

Roll No. ....

**24004**

**B. Tech. 2nd Semester "F Scheme"**

**Examination - May, 2010**

**BASICS OF ELECTRONICS**

**Paper : ECE-101-F**

**Time : Three hours ] [ Maximum Marks : 100**

*Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note : Attempt any five questions.**

- |  |   |
|--|---|
| 1. (a) What is knee voltage ?  | 3 |
| (b) What is cas code amplifier ?                                     | 3 |
| (c) What is barkausen criteria ?                                     | 3 |
| (d) What is C M R R ?  | 3 |
| (e) Define datch and flip flop.                                      | 3 |
| (f) Advantages of L E D over L C D.                                  | 3 |
| (g) What is gsaticule ?  | 2 |
| 2. (a) Differentiate between entrinsic and intrinsic semiconductors. | 6 |

24004-8,900-(P-3)(Q-9)(10)

P. T. O.

- (b) Draw and explain the V-I characteristics of a diode with the help of current of diode. 7
- (c) Explain I/O (v-I) characteristics of C E amplifiers. 7
3. (a) Draw and explain the frequency response curve of RC coupled amplifier and derive expressions for upper and lower cut off frequencies. 10
- (b) Explain the working of feed back networks. Why these are required? What are their advantages? 10
4. (a) Draw and explain the circuit and working of crystal oscillator. 10
- (b) Draw and explain the circuit and working of wein bridge oscillator. 10
5. (a) Draw the basic block diagram of op-amp. 6
- (b) Explain op-amp as differential amplifier. 6
- (c) Explain : (i) slew rate (ii) o/p offset voltage (iii) PS RR. 8
6. Write short notes on : 20
- (a) SMPS.
- (b) Master slave flip flop.
- (c) Johnson counter.
7. (a) Draw the basic block diagram of CRT and explain its working. 10
- (b) Explain the working of function generator. 10

24004-8,900-(P-3)(Q-9)(10) (2)

8. Write short notes on : 20
- (a) Seven segment display
  - (b) Electronic displays.
9. Briefly describes : 20
- (a) Types of liquid crystal cells.
  - (b) Multimeter.
-