

Roll No.

24004

B. Tech. 1st Semester

Examination – December, 2013

BASICS OF ELECTRONICS

'F' Scheme

Paper : ECE-101-F

Time : Three hours]

[Maximum Marks : 100

Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt five questions in all, selecting *one* question from each Section Question No. 1 is *compulsory*.

1. (a) Explain the necessity of doping. 2
- (b) Why is silicon more widely used for semiconductor material ? 2
- (c) What is positive feedback ? Where is it used ? 2
- (d) What is slew rate ? 2

- (e) What is Race-around condition ? 3
- (f) Why is the efficiency of SMPS high ? 3
- (g) Convert $(FF3B)_{16}$ to equivalent decimal. 3
- (h) What is the function of "delay line" in an oscilloscope ? 3

SECTION - A

2. (a) What is meant by biasing of a p-n junction diode ?

Why is it necessary ? Also explain the V-I characteristics of junction diode. 10

- (b) Explain R-C coupled amplifier draw its frequency response curve at different frequencies. 10

3. (a) Explain the concept of cascaded amplifier. Why cascading is required ? 10

- (b) Discuss the advantages and disadvantages of negative feedback. 10

SECTION – B

4. (a) What is crystal oscillator ? Draw its equivalent circuit and derive result for impedance and resonant frequency. 10
- (b) Explain the block diagram of Op-amp. 10
5. (a) Compare the working of Inverter and UPS. 10
- (b) Explain voltage regulator with the help of block diagram. 10

SECTION – C

6. (a) What are universal gates ? Realize all the gates using universal gates. 10
- (b) Explain the working of J-K flipflop. 10
7. (a) Discuss role, importance and application of test instruments. 10
- (b) Explain the working of function generator. 10

SECTION – D

8. (a) Explain the type of liquid crystal cells. 10

Download All Btech Stuff From StudentSuvudha.com

(b) Discuss the advantages and disadvantages of LCD display. 10

9. (a) How fourteen segment display works ? Design a circuit for it. 10

(b) What is LED ? Why LED's emit light of different colours ? Give its advantages and disadvantages. 10