

1987

B.E. 2nd Semester Examination,

May–2013


ELECTRICAL TECHNOLOGY

Paper–EE–101 E

Time allowed : 3 hours] [Maximum marks : 100

- Note :** (i) Attempt any five questions.
(ii) Use of non programmable calculator is allowed.

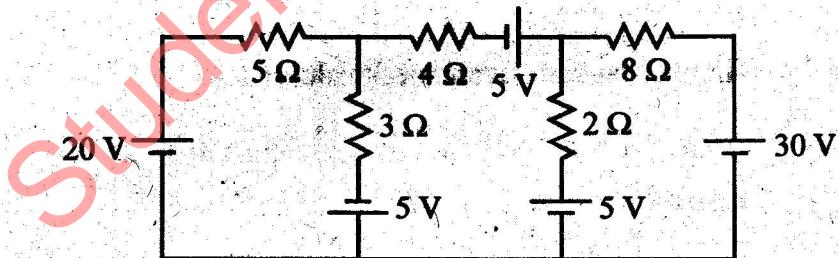- 1. (a)** Determine current in each branch of the network shown in fig. 1.



15

Fig. 1

- (b)** Explain current division and voltage rule with a suitable example. **5**


1987–P–4–Q–8 (13)

[P.T.O.]

(2)

1987

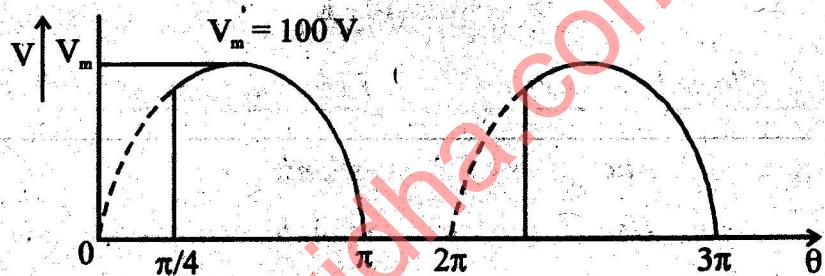2. (a) Find average and effective value of voltage for sinusoidal waveform given below:



10

- (b) Explain the following terms :

(i) RMS Value

(ii) Phase angle

(iii) Instantaneous and peak value.

10

3. (a) Using Norton theorem calculate current in 2Ω resistor in the network shown in fig. 3.

10

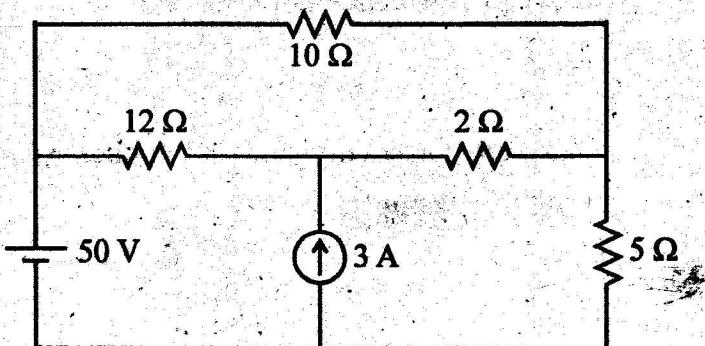


Fig. 3

1987

(3)

1987

- (b) State and explain maximum power transfer theorem. 10

4. (a) Define (i) Q-factor of a coil (ii) Power factor (iii) active and reactive power and their significance. 10

- (b) What is meant by resonance in series a.c. circuit ? Also discuss effect of series resonance. 10

5. (a) Explain two wattmeter method of power measurement in three phase A.C. system at balanced load. 10

- (b) Establish relation between line voltage and phase voltage and between line current and phase current if the three phase load is connected - (i) In star fashion and (ii) In delta fashion. 10

6. (a) Explain working principle and constructional details of single phase transformer. 10

- (b) Derive the equation for voltage regulation of single phase transformer at capacitive load by drawing the phasor diagram. 10

1987

[P.T.O.]

(4)

1987

7. Explain the comparison of working principle and construction of D.C. motor with Induction motor and synchronous motor. 20
8. Explain construction and working of:
(i) Wattmeter
(ii) Energy meter. 20

1987