

24007

**B.Tech. 1st Semester Examination,  
December-2012**

**ELECTRICAL TECHNOLOGY**

**Paper-EE-101-F**

*Time allowed : 3 hours]*

*[Maximum marks : 100*

- Note :** (i) *Question No. 1 is compulsory from Section-A.*  
(ii) *Attempt four questions from remaining four sections selecting one question from each section.*  
(iii) *Use of non programmable calculator is allowed.*

**Section-A**


1. (i) Distinguish between unilateral and bilateral Network. 4  
(ii) How the rotor of DC Motor rotate ? 4  
(iii) Derive the e.m.f. equation for 1-phase transformer. 4  
(iv) Write short note on deflecting torque in measuring instruments. 4  
(v) Explain the significance of power triangle in AC system. 4

24007-P-4-Q-9


[P.T.O.

## Section-B

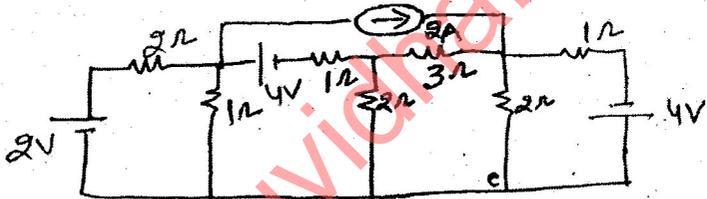2. (a) Explain the Kirchoffs voltage law and current law with some suitable example. 10
- (b) Find the value of current flowing through 3 ohm resistance in the given circuit by using Nodal Analysis. 10



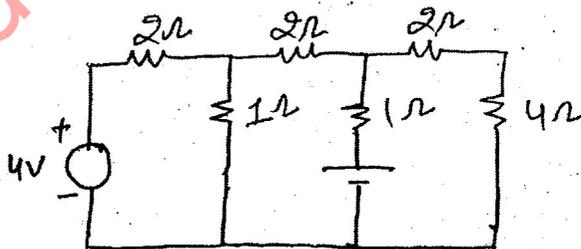3. (a) Find the value of current flowing through 4 ohm resistance in the given circuit by using Thevenin's theorem. 10



- (b) State and explain maximum power transfer theorem with some suitable example. 10

**Section-C**

4. (a) Define and explain the terms given below : 10  
(i) RMS values and  
(ii) Average values of an AC sinusoidal signal.
- (b) An inductive ckt of resistance  $3\Omega$ , and inductance  $0.02\text{H}$  is connected to a  $230\text{V}$ ,  $50\text{Hz}$  supply. What value of capacitance be placed in parallel with the inductive ckt will produce resonance ? Also find current taken from supply at resonance. 10
5. A coil which has  $6\text{ ohm}$  and  $25.5\text{ mH}$  inductance is energized from a  $220\text{ V}$ ,  $50\text{ Hz}$  supply. (i) Calculate the current (ii) A capacitor is then connected in parallel with the coil so that the overall power factor is raised to unity. Calculate the capacitance of the capacitor. 20

**Section-D**

6. (a) Explain two wattmeter method of power measurement in 3-phase AC system at balanced load. 10
- (b) Derive the relation between Line voltage and phase voltage, Line current and phase current for star connection in 3-phase system. 10

7. Draw and explain the Circuit diagram and Phasor diagram of single Phase Practical transformer diagram at resistive load. 20

### Section-E

8. (a) Explain how the revolving flux is produced in the stator of 3-phase induction motor. 10
- (b) Prove that 1-phase induction is not self starting. Explain the starting methods. 10
9. (a) Explain the construction and working of Energy Meter. 10
- (b) A 240 V single phase energy meter has a constant load current of 10 A at unity power factor. If the meter disc makes 1155 revolution during 3 hours, calculate the meter constant. If the power factor were 0.85, what would be the number of revolutions made by the disc in that time ? 10