

Roll No. ....

**2104**

**B. E. 4th Sem. (ECE)**

**Examination – May, 2011**

**DIGITAL ELECTRONICS**

**Paper : EE-204-E**

**Time : Three hours ]**

**[ Maximum Marks : 100**

*Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** Attempt any **five** questions. All questions carry equal marks.

1. (a) Why NAND and NOR gate are called universal gate. Derive basic gates from these gates. 10
- (b) (i) Multiply  $(110.10)_2$  by  $(11.01)_2$ . 3
- (ii) Convert  $(10101011)_2$  to its gray code. 2
- (iii) Convert  $(12)_{10}$  to the number system whose base is 3. 5

2104- 3,350-(P-3)(Q-8)(11)

P. T. O.

2. (a) Seven bit Hamming code is received as 1011001. Locate the error position and find the correct code, if even parity is used. 10
- (b) What are main disadvantages of Boolean algebra Reduction Method ? Give advantages of K-Map. Reduce the function  $Y(ABCD) = \sum(0, 2, 4, 6, 8, 9, 12)$  using K-map. 10
3. (a) Implement the following function using  $4 \times 1$  Multiplexer. 10
- $$y = \sum(0, 1, 2, 5, 9, 11, 13, 15)$$
- (b) Design a code converter, which convert Binary code to grey code. 10
4. (a) What is race around condition in J-K Flip Flop ? How it can be eliminated by different method ? 10
- (b) Design Mod 6 UP/Down counter using T-type Flip Flop. 10
5. (a) What is the advantages of ECL logic family ? Explain how ECL gate works. 10
- (b) What do you mean by interfacing ? Explain the need. How will you interface TTL to C-MOS. 10
6. (a) What is magnitude comparator ? Draw a circuit for u bit comparator. 10

- (b) Draw and explain the circuit for bi-directional shift register. 10
7. (a) Explain the R-2-R ladder type D/A converter. 10  
(b) Explain SAR A/D converter. 10
8. Write short note on : 20  
(i) PLD's and CPLD's  
(ii) ROM and FPQA
-