

24043

B.Tech. 3rd Semester Information Technology

(Branch-VI) Examination, December-2013

DIGITAL ELECTRONICS

Paper-EE-204-F

Time allowed : 3 hours] [Maximum marks : 100

Note : Question No. 1 is compulsory. Attempt any one question from each section.

1. (a) Realize three basic gates (AND, OR and NOT) using NAND gates only. 5
- (b) Differentiate between Serial and Parallel Adder. 5
- (c) Differentiate between Synchronous and Asynchronous Counters. 5
- (d) Explain PLA in brief. 5

Section-A

2. (a) Convert the following :
 - (i) $(885)_{16} = (\text{-----})_2$
 - (ii) $(111\ 111\ 000\ 101101001)_2 = (\text{-----})_{16}$
 - (iii) $(10\ 111\ 111)_2 = (\text{-----})_8$
 - (iv) $(5624.37)_8 = (\text{-----})_2$
 - (v) $(1010010)_2 = (\text{-----})_{10}$

10

- (b) Minimize the following expression using K-Map and realize it using basic gates.

$$Y = \sum m (1, 2, 9, 10, 11, 14, 15) \quad 10$$

3. (a) Simplify the given expression using the Quine-McCluskey minimisation technique and realize it using basic gates.

$$Y(A, B, C, D) = \sum m (0, 1, 3, 7, 8, 9, 11, 15) \quad 15$$

- (b) Explain Error detecting and Error Correcting Codes with an example of each. 5

Section-B

4. (a) Describe the half-Adder circuit with its truth table and realize it using basic gates. 10

- (b) What do you mean by Multiplexer? Realize 32:1 Multiplexer using two 16:1 Multiplexers. 10

5. (a) Implement the given expression using 8:1 Multiplexer.

$$f(A, B, C, D) = \sum m (0, 2, 3, 6, 8, 9, 12, 14) \quad 10$$

- (b) Explain the function of Demultiplexer in detail with its circuit diagram. 10

Section-C

6. (a) Explain the working of a Master-Slave J-K Flip-Flop with neat and clean diagram. 10
- (b) Design a 2-bit Asynchronous UP counter and explain it using timing diagram. 10
7. (a) What do you mean by Race-Around Condition? How will it be removed? 10
- (b) Design a Mod-5 Synchronous counter using J-K flip-flop and draw its state diagram. 10

Section-D

8. (a) Differentiate between RAM and ROM including their advantages, disadvantages and applications. 10
- (b) What is PLA? Explain various blocks of PLA. 10
9. (a) What is PAL? Explain in detail. 10
- (b) Explain different types of Hazards in combinational circuits. 10