

Roll No.

24143

**B. Tech 4th Semester (E. E.)
Examination – May, 2013**

DIGITAL ELECTRONICS

Paper : EE-204-F

Time : Three hours]

[Maximum Marks : 100

Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions. Question No. 1 is *compulsory* and *one* question from each of *four* Section.

1. (a) Realize the following using NOR gate : $5 \times 4 = 20$
 - (i) OR gate
 - (ii) AND gate
- (b) Give Boolean expression and Truth Table for following :
 - (i) AND gate
 - (ii) Half Adder
 - (iii) Subtractor
 - (iv) 4 : 1 Multiplexer

(c) Differentiate between :

- (i) Latch and Flip Flop
- (ii) Decoder and demultiplexer
- (iii) Ripple and synchronous counter

(d) What are hazards ?

SECTION - A

2. (a) Use K-map to simplify : 10

$$(i) F = \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + \overline{A}BCD \\ + \overline{A}B\overline{C}D + \overline{A}BC\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}CD$$

$$(ii) F = (AC + A\overline{C}D)(AD + AC + BC)$$

(b) Write short notes on : 10

- (i) Quine MC- Clusky Method
- (ii) Error detecting and correcting codes

3. (a) Convert : 10

- (i) 212_8 to decimal
- (ii) 399_{10} to octal
- (iii) -200_{10} to hexadecimal
- (iv) 101101.1_2 to decimal
- (v) ABH to binary

(b) Get simplified expression of : 10

$$Y = F(A, B, C, D) = \sum m(1, 2, 8, 9, 10, 12, 13, 14)$$

using Quine -MC Qusky method

SECTION - B

4. (a) Design 16 to 1 multiplexer using 4 to 1 multiplexer. 10
- (b) Draw block diagram, Truth table and Circuit diagram for 1-bit comparator. 10
5. (a) Implement Full adder using two half adders. 10
- (b) Realize $y = \bar{A}B + \bar{B}\bar{C} + ABC$ using an 8 to 1 multiplexer. Can it be realized with 4 to 1 multiplexer. 10


SECTION - C

6. (a) Design a MOD-10 down counter using J - K Flip-Flop. 10
- (b) Convert : 10
- (i) J-K Flip - Flop to D Flip Flop
- (ii) S-R Flip - Flop to J-K Flip Flop
7. (a) What is a shift register ? Draw circuit diagram for : 10
- (i) Serial in/Serial out
- (ii) Parallel in/parallel out Shift registers using J - K Flip - Flops
- (b) Give excitation tables for : 10
- (i) J - K Flip - Flop
- (ii) D Flip - Flop
- (iii) T Flip - Flop

SECTION - D

8. Reduce state transition diagram of Figure by : 20

 - (i) Row eliminator method
- (ii) Implication Table method



9. Write short notes on :

10, 10

- (i) ROM and PLA,
- (ii) ASM.