

SECTION-D

Binary Subtractor

- half

- full Subtractor

- half Subtractor


| | B | 0 | 1 |
|---|---|------------|------------|
| A | 0 | 0 m_0 | 1 m_1 |
| | 1 | 1 m_2 | 0 m_3 |

$$\text{Diff} = AB + A\bar{B} = A \oplus B$$

| A | B | Diff | Borrow |
|---|---|---------|--------|
| 0 | 0 | m_0 0 | 0 |
| 0 | 1 | m_1 1 | 0 |
| 1 | 0 | m_2 1 | 0 |
| 1 | 1 | m_3 0 | 1 |


| | B | 0 | 1 |
|---|---|---|---|
| A | 0 | 0 | 1 |
| | 1 | 0 | 0 |

$$\text{Borrow} = B_0 = \bar{A}B$$

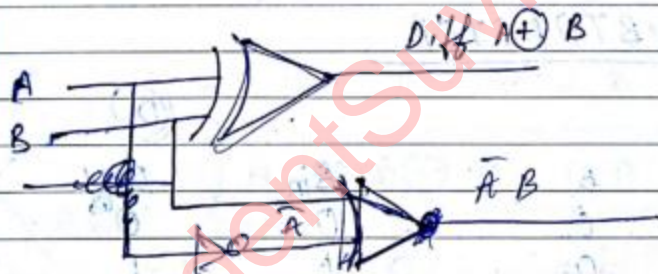


NAND

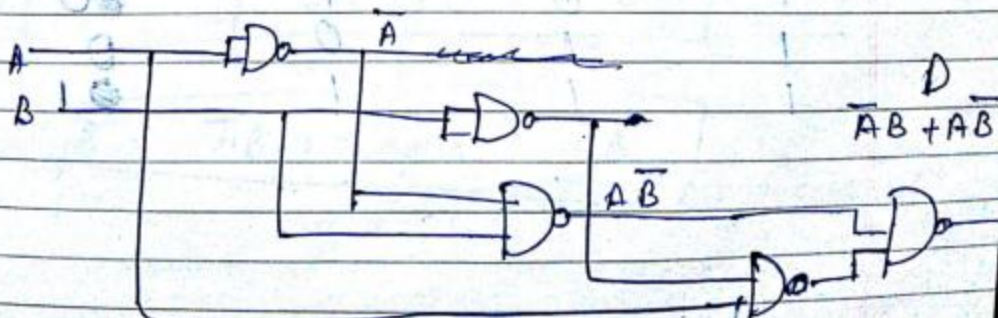Difference $\bar{A}B + A\bar{B} = D$
 $\bar{A}B \cdot \bar{A}B = D$



Borrow NAND

$$\overline{\overline{A}B}$$

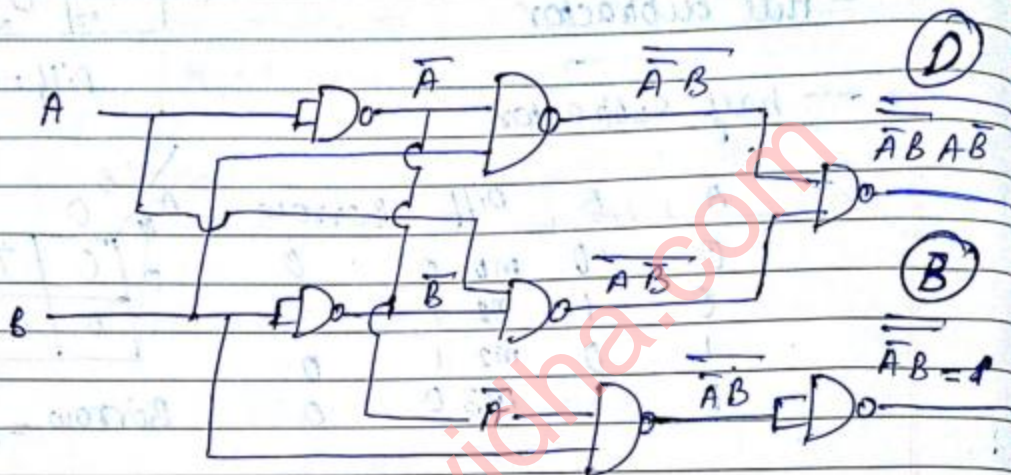

FULL SUBTRACTOR

| A | B | Bin | Diff | Borrow |
|---|---|-----|------|--------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

XOR - XNOR

classmate

Date

Page

| B Bin | | 00 | 01 | 11 | 10 |
|-------|---|----|----|----|----|
| A | 0 | 0 | 1 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 0 |

$$D = \bar{A}\bar{B}Bin + A\bar{B}Bin + A\bar{B}Bin + ABBin$$

$$B \cdot \bar{A} (\bar{B}Bin + B\bar{B}in) + A (\bar{B}Bin + B\bar{B}in)$$

$$\bar{A} (B \oplus Bin) + A (\bar{B} \oplus Bin)$$

$$\text{Assume } B \oplus Bin = X$$

$$\bar{A}X + A\bar{X} = A \oplus X$$

$$A \oplus B \oplus Bin = D$$

| B Bin | | 00 | 01 | 11 | 10 |
|-------|---|----|----|----|----|
| A | 0 | 0 | 1 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 0 |

$$B = \bar{A}Bin + BinB + \bar{A}B$$

| B Bin | | 00 | 01 | 11 | 10 |
|-------|---|----|----|----|----|
| A | 0 | 0 | 1 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 0 |

$$D = \bar{A}\bar{B}Bin + AB\bar{Bin} + A\bar{B}\bar{Bin} + AB\bar{Bin}$$

$$B \cdot \bar{A} (\bar{B}Bin + B\bar{Bin}) + A (\bar{B}\bar{Bin} + B\bar{Bin})$$

$$\bar{A} (B \oplus Bin) + A (\bar{B} \oplus \bar{Bin})$$

$$\text{Assume } B \oplus Bin = X$$


$$\bar{A}X + A\bar{X} = A \oplus X$$

$$A \oplus B \oplus Bin = D$$


| B Bin | | 00 | 01 | 11 | 10 |
|-------|---|----|----|----|----|
| A | 0 | 0 | 1 | 0 | 1 |
| | 1 | 0 | 0 | 1 | 0 |


$$B = \bar{A}Bin + BinB + \bar{A}\bar{B}$$

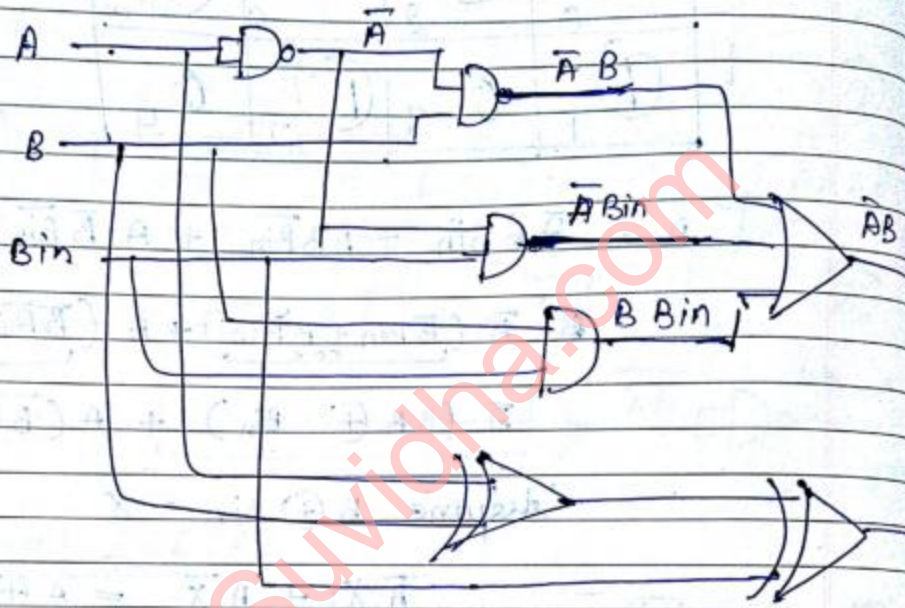B $\bar{A}B_{in} + B\bar{A}_{in} + \bar{A}B$



FULL SUBTRACTOR USING HALF SUBTRACTOR

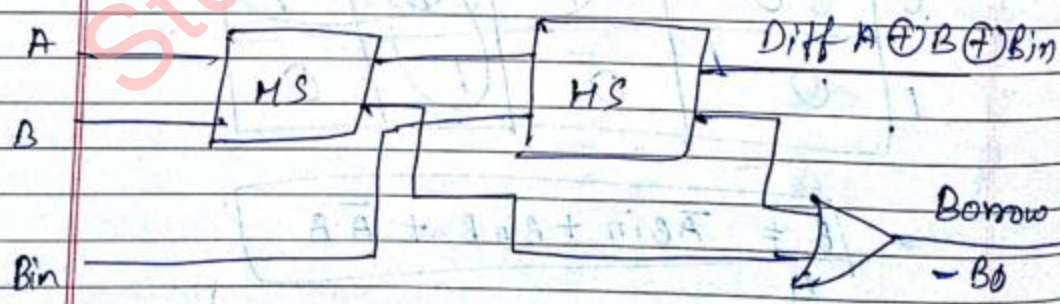

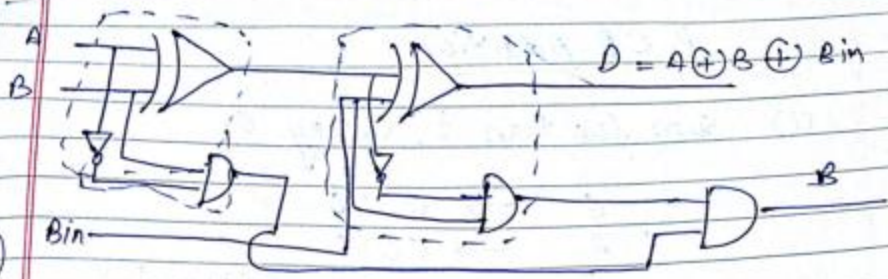

(B)

$$AB + B\text{in} + \bar{A}B$$

$$(A \oplus B) \text{Bin} + \bar{A}B = \bar{A}B + AB\text{in} + BB\text{in}$$

(C)

$$A \oplus B \oplus \text{Bin}$$

$$(\bar{A}\bar{B} + AB) \text{Bin} + \bar{A}B$$

$$\bar{A}\bar{B}\text{Bin} + AB\text{Bin} + \bar{A}\bar{B}(1 + B\text{in})$$

$$\bar{A}\bar{B}\text{Bin} + AB\text{Bin} + \bar{A}\bar{B} + \bar{A}\bar{B}B\text{in}$$

$$\bar{A}\text{Bin}(\bar{B} + B) + AB\text{Bin} + \bar{A}\bar{B}$$

$$\bar{A}\text{Bin} + AB\text{Bin} + \bar{A}\bar{B}(1 + B\text{in})$$

$$\bar{A}\text{Bin} + AB\text{Bin} + \bar{A}\bar{B} + \bar{A}\bar{B}B\text{in}$$

$$\boxed{\bar{A}\text{Bin} + AB\text{Bin} + \bar{A}\bar{B}}$$

B C D Addition

(1) Sum less than 9, Carry 0

$$\begin{array}{r} 6 \rightarrow 0110 \\ + 2 \rightarrow 0010 \\ \hline 8 \quad \underline{1000} \end{array} \begin{array}{l} \text{(Binary)} \\ \downarrow \\ \text{BCD} \end{array}$$

(2) Sum greater than or equal to 9, carry 0

$$\begin{array}{r} 9 \\ + 4 \\ \hline 13 \end{array} \quad \begin{array}{r} 1001 \\ 0100 \\ \hline 1101 \end{array} \rightarrow \text{Binary addition}$$

$$\begin{array}{r} 1101 \\ + 0110 \\ \hline 00010011 \end{array} \rightarrow \text{Add 6}$$

$$\begin{array}{r} 00010011 \\ \hline 00010111 \end{array} \rightarrow \text{BCD}$$


(Note: The diagram shows a carry of 1 from the 4th bit to the 5th bit, resulting in 1 0111, which is 13 in BCD.)

(3) Sum greater than 9 but carry is equivalent to 1

$$\begin{array}{r} 9 \\ + 8 \\ \hline 17 \end{array} \quad \begin{array}{r} 1001 \\ + 1000 \\ \hline 10001 \end{array} \rightarrow \text{Binary addition}$$

$$\begin{array}{r} 10001 \\ + 0110 \\ \hline 00010111 \end{array} \rightarrow \text{BCD}$$

(Note: The diagram shows a carry of 1 from the 5th bit to the 6th bit, resulting in 1 0111, which is 17 in BCD.)

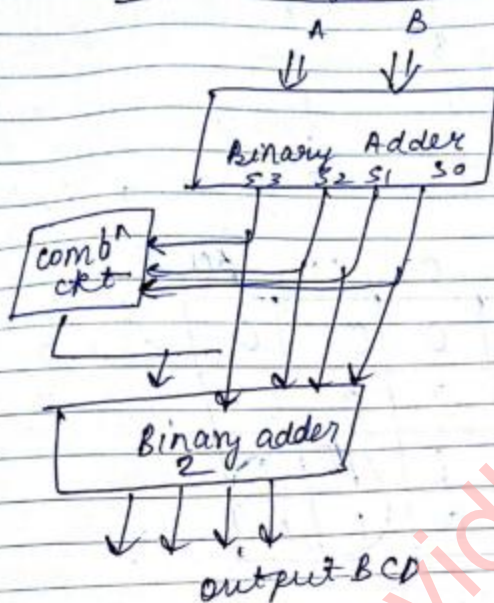Block Diagram of BCD AdderDesign Combinational Skt of BCD Adder

(1) if $sum > 9$, carry

| s_3 | s_2 | s_1 | s_0 | Y |
|-------|-------|-------|-------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |

| | | | | |
|---|---|---|---|---|
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |

$S_3 S_2$ $S_1 S_0$

| | | | | |
|----|----|----|----|----|
| | 00 | 01 | 11 | 00 |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |


$S_3 = A$


$S_2 = B$

$S_1 = C$

$S_0 = D$

$$Y = S_2 S_3 + S_3 S_1$$

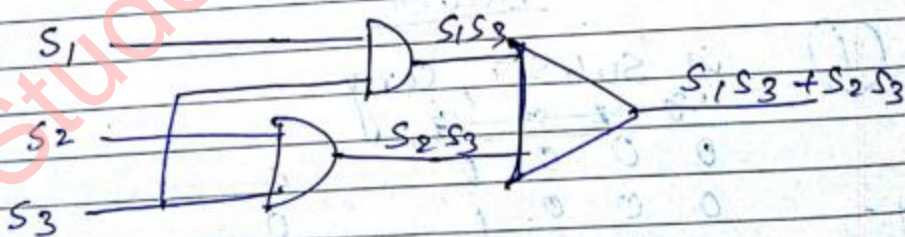

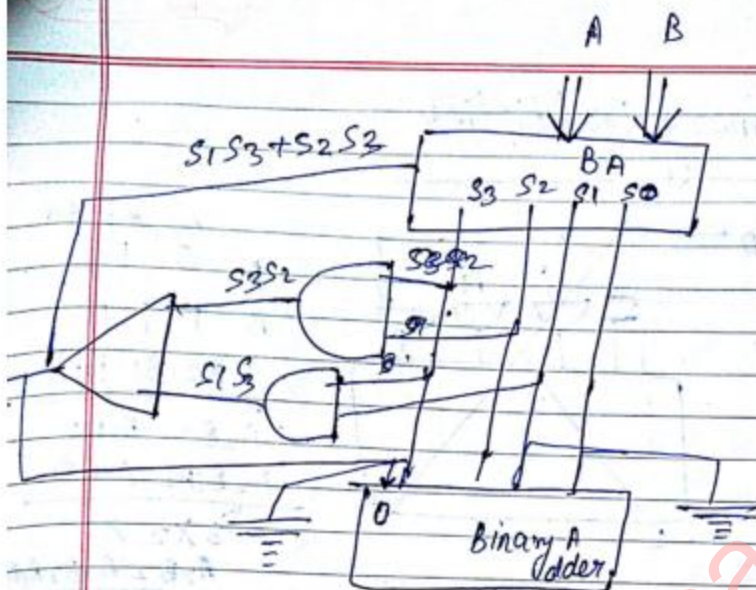

BCD SUBTRACTOR

10's Complement



9's Complement + 1

Q (4) no.

9's complement = 9

4

5 — 9's

+ 1

6 — 10's


8 — 1000

+ 6 — 0110


14 — 1110 + 6

0110

Binary Multiplier

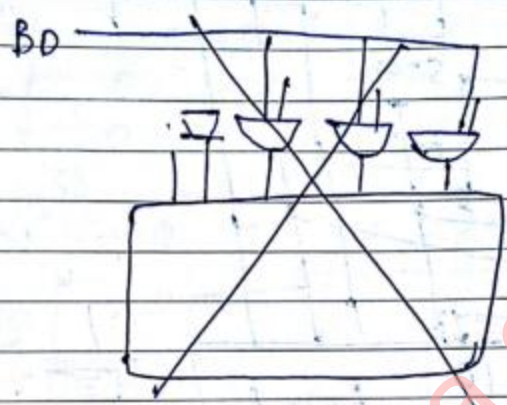
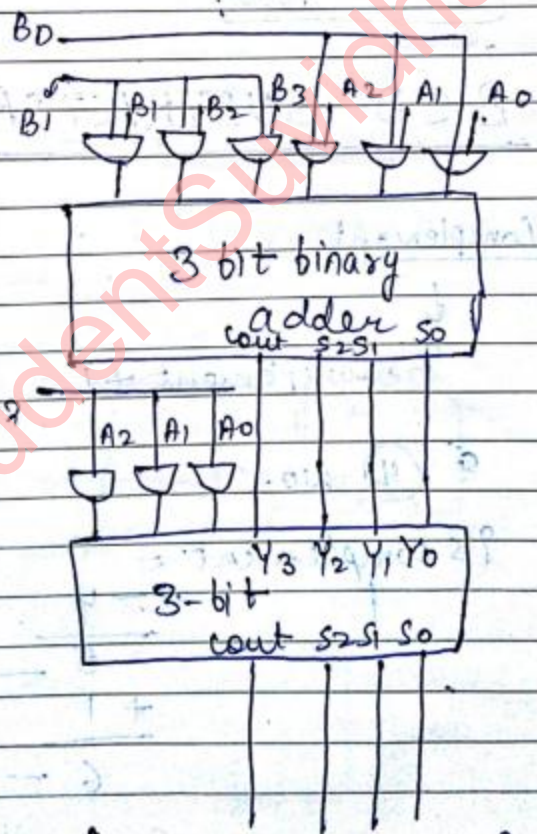
$$\begin{array}{r}
 A_2 \ A_1 \ A_0 \\
 A \quad 0 \ 1 \ 1 \\
 B \quad 1 \ 1 \ 1 \\
 \hline
 B_2 \ B_1 \ B_0 \\
 A_2 B_0 \ A_1 B_0 \\
 A_2 B_1 A_1 \ A_0 B_1 \\
 \hline
 A_3 \times 2 \ A_1 \\
 A_2 B_2 \ A_1 B_2 \ A_0 \\
 \hline
 \times
 \end{array}$$



(Block diagram of Binary Model)

Binary to BCD Conversion

| | | | | BCD | | | |
|---|---|---|---|-------|-------|-------|-------|
| A | B | C | D | D_4 | D_3 | D_2 | D_1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 1 | 1 | 0 |
| 01 | 0 | 1 | 1 | 0 |
| 11 | 0 | 1 | 1 | 0 |
| 10 | 0 | 1 | 1 | 0 |

| AB \ CD | 00 | 01 | 11 |
|---------|----|----|----|
| 00 | 0 | 0 | 1 |
| 01 | 0 | 0 | 1 |
| 11 | 1 | 1 | 0 |
| 10 | 0 | 0 | 0 |

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 1 | 1 | 1 | 1 |
| 11 | 0 | 0 | 1 | 1 |
| 10 | 0 | 0 | 0 | 0 |

$$\overline{AB} + D_2$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 1 | 1 | 0 | 1 |

$$D_3 \overline{A} B \overline{C}$$

| AB \ CD | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |

$$D_4$$

$$A C + A D$$

A

B

BCD to Excess 3 Converter

| BCD | | | | | | | | Excess 3 | | | |
|-----|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A | B | C | D | B ₃ | B ₂ | B ₁ | B ₀ | E ₃ | E ₂ | E ₁ | E ₀ |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |

1 0 1 0

1 0 1 1

1 1 0 0

1 1 0 1

1 1 1 0

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

1 1 1 1

| B ₀ B ₁ B ₂ B ₃ | 00 | 01 | 11 | 10 | B ₀ B ₁ B ₂ B ₃ | 00 | 01 | 11 | 10 |
|---|----|----|----|----|---|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 | 00 | 1 | 0 | 1 | 0 |
| 01 | 1 | 0 | 0 | 1 | 01 | 1 | 0 | 1 | 0 |
| 11 | x | x | x | x | 11 | x | x | x | x |
| 10 | 1 | 0 | x | x | 10 | 1 | 0 | x | x |

E₀B₃E₁B₂B₁B₀

| B ₂ B ₁ | | 00 01 11 10 | | | | B ₂ B ₁ | | 00 01 11 10 | | | |
|-------------------------------|----|-------------|---|---|---|-------------------------------|----|-------------|---|---|---|
| B ₀ B ₀ | 00 | 0 | 1 | 1 | 1 | B ₀ B ₁ | 00 | 0 | 0 | 0 | 0 |
| | 01 | 1 | 0 | 0 | 0 | | 01 | 0 | 1 | 1 | 1 |
| | 11 | X | X | X | X | | 11 | X | X | X | X |
| | 10 | 0 | 1 | X | X | | 10 | 1 | 1 | X | X |

Binary to Gray Code

$$G_3 = B_3$$

$$G_2 = B_2 \oplus B_3$$

$$G_1 = B_1 \oplus B_2$$

$$G_0 = B_0 \oplus B_1$$

| B ₃ | B ₂ | B ₁ | B ₀ | G ₃ =B ₃ | G ₂ | G ₁ | G ₀ |
|----------------|----------------|----------------|----------------|--------------------------------|----------------|----------------|----------------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |

~~Exercise 3.2~~Bob₁ 00 01 11 10

Q3

| B ₂ B ₃ | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | 0 | 0 | 1 | 1 |
| 01 | 0 | 0 | 1 | 1 |
| 11 | 0 | 0 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |

Bob₁ 00 01 11 10

Q2

| B ₂ B ₃ | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | 0 | 1 | 1 | 1 |
| 01 | 0 | 1 | 0 | 1 |
| 11 | 0 | 1 | 0 | 1 |
| 10 | 0 | 1 | 0 | 1 |

Bob₁ 00 01 11 10

Q1

| B ₂ B ₃ | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

Bob₁ 00 01 11 10

Q0

| B ₂ B ₃ | 00 | 01 | 11 | 10 |
|-------------------------------|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

Gray to Binary

$$B_3 = G_3$$

$$B_2 = G_2 \oplus G_3$$

$$B_1 = G_1 \oplus G_2 \oplus G_3$$

$$B_0 = G_0 \oplus G_1 \oplus G_2 \oplus G_3$$

000

011


101

110

| G_3 | G_2 | G_1 | G_0 | B_3 | B_2 | B_1 | B_0 |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 |

Multiplexer

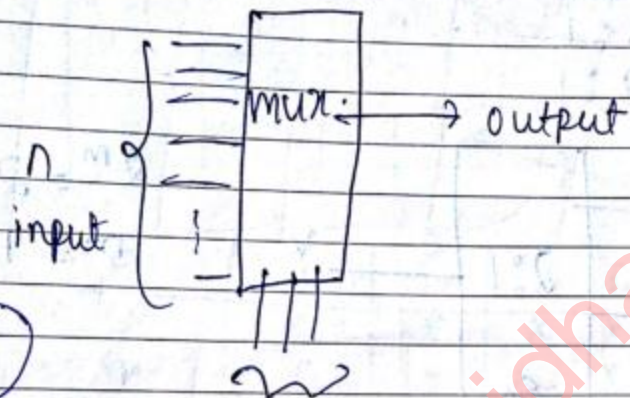is a combinational ~~circuit~~ ~~circuit~~ ~~circuit~~ circuit, it has n input and 1 output and n data select inputs.



$E = 0$
active mode
 $E = 1$
Inactive mode

m - Selected \rightarrow n no. of select inputs.
 $n \rightarrow$ inputs.

- 1) A mux. is a digital circuit which select one of n data inputs and routes it to the output.
- 2) E is called as Enable input which is useful for cascading. It is generally an active low terminal that means it will be required open when it is low.

Advantage of Mux

- It reduce no. of wires.
- It simplify logic design.
- It reduce circuit complexity & cost.

mux types :-


- 2 : 1

- 4 : 1


- 8 : 1

- 16 : 1

- 32 : 1

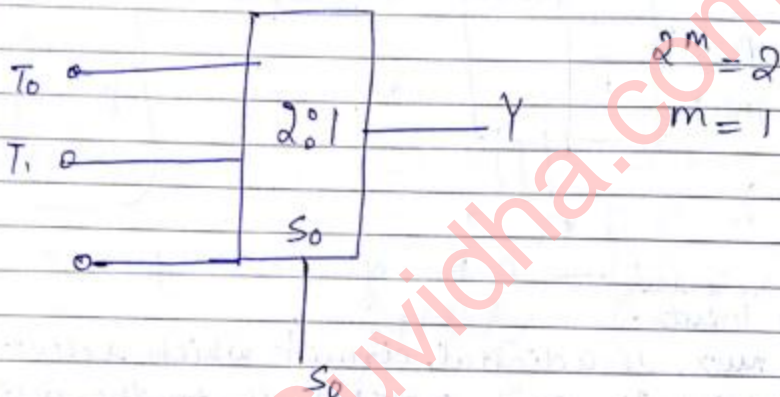

| T_0 | T_1 | S_0 | F | S_0 | Y |
|-------|-------|-------|-----|-------|-------|
| 0 | 0 | 0 | 0 | x | x |
| 0 | 1 | 0 | 1 | 0 | D_0 |
| 1 | 0 | 1 | 1 | 1 | D_1 |

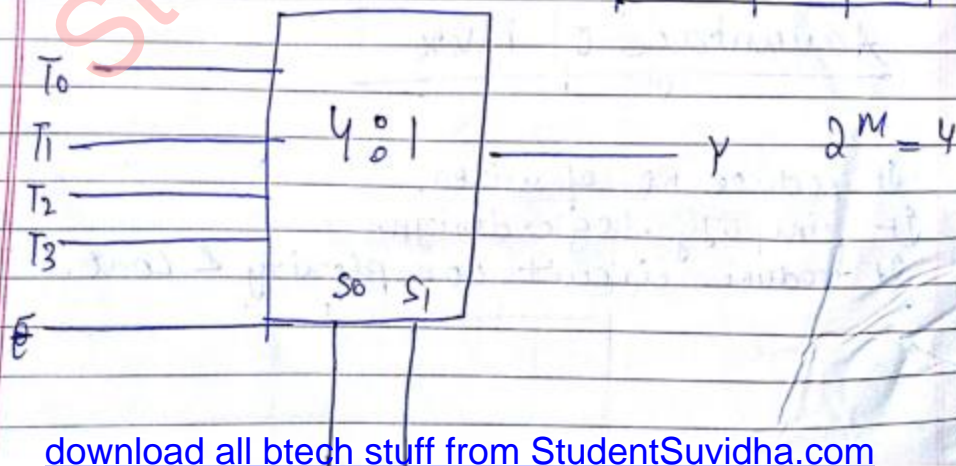

| E | S ₀ | S ₁ | D₀ | D ₁ | Y |
|---|----------------|----------------|--------------------------|----------------|---|
| 0 | X | X | X | X | X |
| 1 | 0 | 0 | 0 | X | 0 |
| 1 | 0 | 0 | 1 | X | 1 |
| 1 | 1 | 0 | | | |
| 1 | 1 | 1 | | | |

| E | S ₀ | S ₁ | Y | A | S ₁ | S ₀ | D ₀ | X |
|---|----------------|----------------|----------------|---|----------------|----------------|----------------|---|
| 0 | X | X | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | D ₀ | X | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | D ₁ | 0 | 0 | 1 | X | 0 |
| 1 | 0 | 0 | D ₂ | 1 | 0 | 1 | X | 1 |
| 1 | 1 | 1 | D ₃ | X | 1 | 0 | X | 0 |

| S₀ | 0 | 1 | X |
|--------------------------|---|----------------|----------------|
| S₁ | 0 | D ₀ | D ₂ |
| | | D ₁ | D ₃ |

S₁ S₀ D₀

| | 0 | 1 | X | X |
|-----|-----|-----|-----|---|
| E | 001 | 011 | 010 | |
| X | X | X | X | X |
| 100 | 101 | 111 | 110 | |

$\overline{S_1} \overline{S_0} X$

D_1

| | | | | | |
|---|-------|----|----|----|----|
| | S_0 | | | | |
| | S_1 | 00 | 01 | 11 | 10 |
| 0 | | X | X | X | 1 |
| 1 | | X | X | X | X |


$$D_1 = \overline{S_1} S_0 \overline{X}$$

$$D_2 = S_1 \overline{S_0} \overline{X}$$

$$D_3 = S_1 S_0 \overline{X}$$

$$Y = \overline{S_1} \overline{S_0} \overline{X} + \overline{S_1} S_0 \overline{X} + S_1 \overline{S_0} \overline{X} + S_1 S_0 \overline{X}$$

Design 8:1 Mux

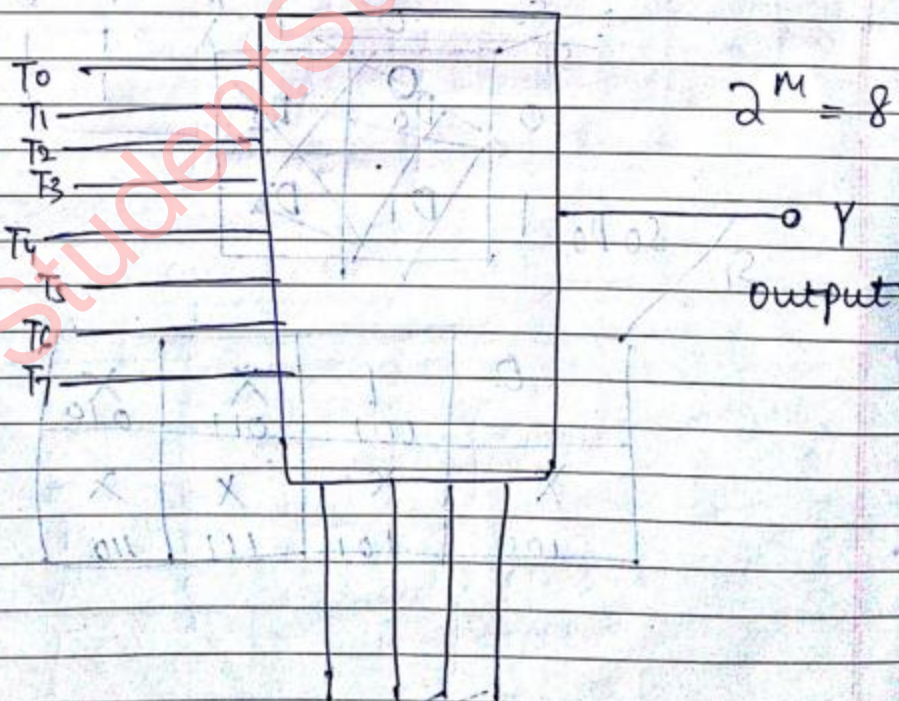

Truth Table

| E | S ₂ | S ₁ | S ₀ | Y |
|---|----------------|----------------|----------------|----------------|
| 0 | X | X | X | 0 |
| 1 | 0 | 0 | 0 | D ₀ |
| 1 | 0 | 0 | 1 | D ₁ |
| 1 | 0 | 1 | 0 | D ₂ |
| 1 | 0 | 1 | 1 | D ₃ |
| 1 | 1 | 0 | 0 | D ₄ |
| 1 | 1 | 0 | 1 | D ₅ |
| 1 | 1 | 1 | 0 | D ₆ |
| 1 | 1 | 1 | 1 | D ₇ |

$$E = \overline{S_2} \overline{S_1} \overline{S_0} D_0 + \overline{S_2} \overline{S_1} S_0 D_1 + \overline{S_2} S_1 \overline{S_0} D_2 + \overline{S_2} S_1 S_0 D_3 \\ + S_2 \overline{S_1} \overline{S_0} D_4 + S_2 \overline{S_1} S_0 D_5 + S_2 S_1 \overline{S_0} D_6$$


Application Of Mux

another name of Mux is data-selector

Mux Tree

The mux having more no. of inputs can be ~~not~~ obtained by cascading two or more multiplexers with less no. of input is called mux. Tree.

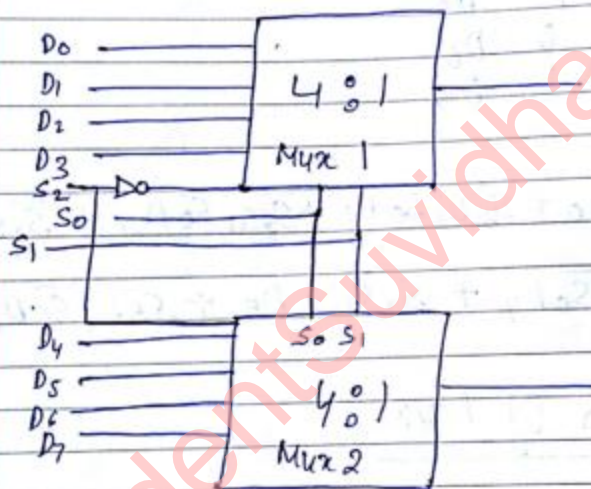Ques obtain 8:1 mux using ~~2:4:1~~ two 4:1 muxes.




Truth Table

| S ₂ | S ₁ | S ₀ | Y | |
|----------------|----------------|----------------|----------------|-----------------|
| 0 | 0 | 0 | D ₀ | Mux 1 enable |
| 0 | 0 | 1 | D ₁ | |
| 0 | 1 | 0 | D ₂ | |
| 0 | 1 | 1 | D ₃ | |
| 1 | 0 | 0 | D ₄ | Mux 2 enable |
| 1 | 0 | 1 | D ₅ | |
| 1 | 1 | 0 | D ₆ | |
| 1 | 1 | 1 | D ₇ | |

Ques Implement the following exprⁿ using Muxs.
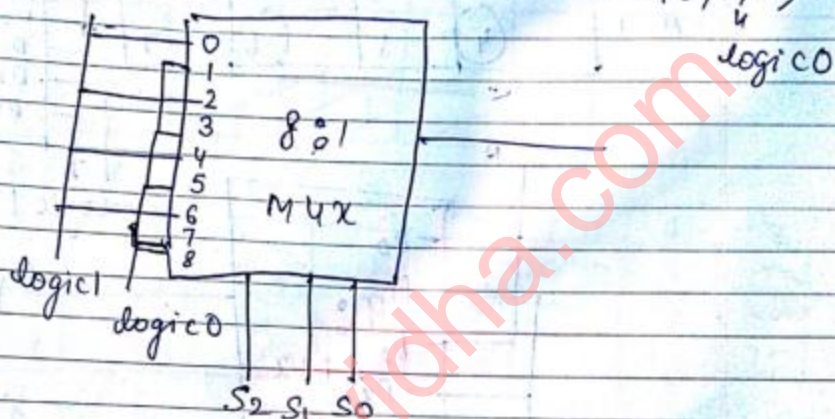
$$F(A, B, C) = \sum m(0, 2, 4, 6) = \text{logic 1} \\ \text{or } \pi(1, 3, 5, 7)$$




Ques Implement the logic function using 4-to-1 mux.

$$F(A, B, C) = \sum m(1, 3, 4, 6)$$




folding Table

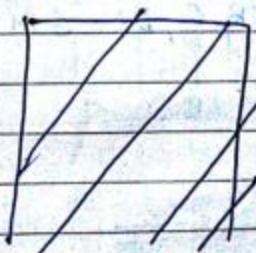

| | D_0 | D_1 | D_2 | D_3 |
|-----------------|-------|-------|-------|-------|
| \overline{BC} | 00 | 01 | 11 | 10 |
| $A=0$ | 0 | 1 | 2 | 3 |
| $A=1$ | 4 | 5 | 6 | 7 |


if it is the

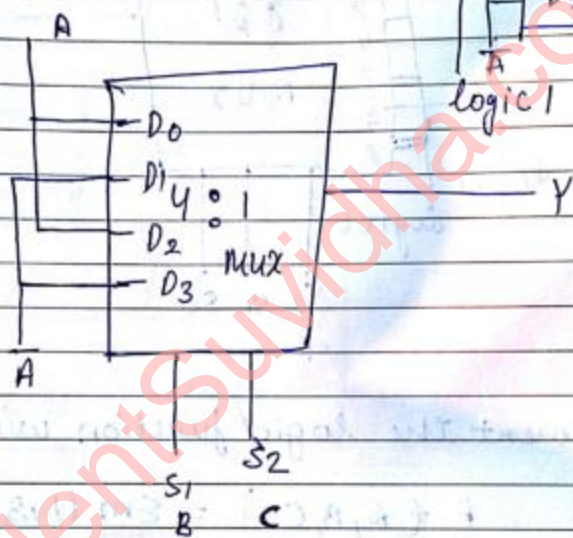


$$A + \overline{A} = 1$$

Ques Implement the following Boolean function
8-to-1 MUX
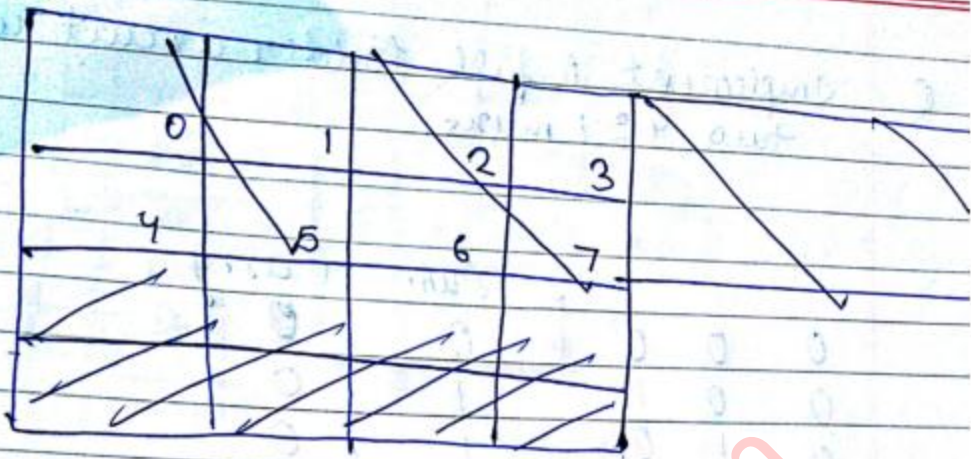
$$f(A, B, C, D) = \sum m(2, 4, 7, 5, 10, 14)$$



| | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| A | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |

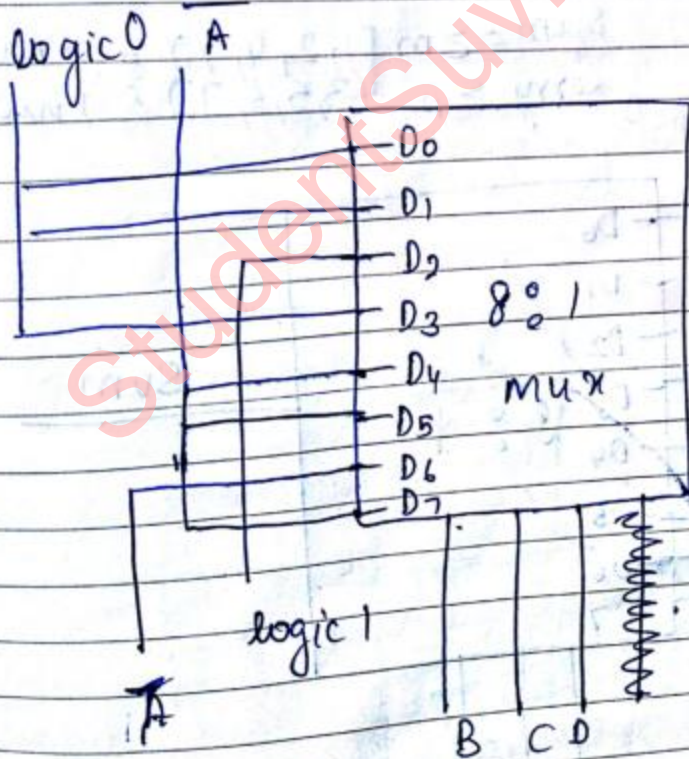



Q Implement A full adder circuit using two 4:1 muxs.

| | | | Sum | Carry |
|---|---|---|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Sum = $\Sigma m(1, 2, 4, 7)$ 4:1 mux


Carry = $\Sigma m(3, 5, 6, 7)$ 4:1 mux

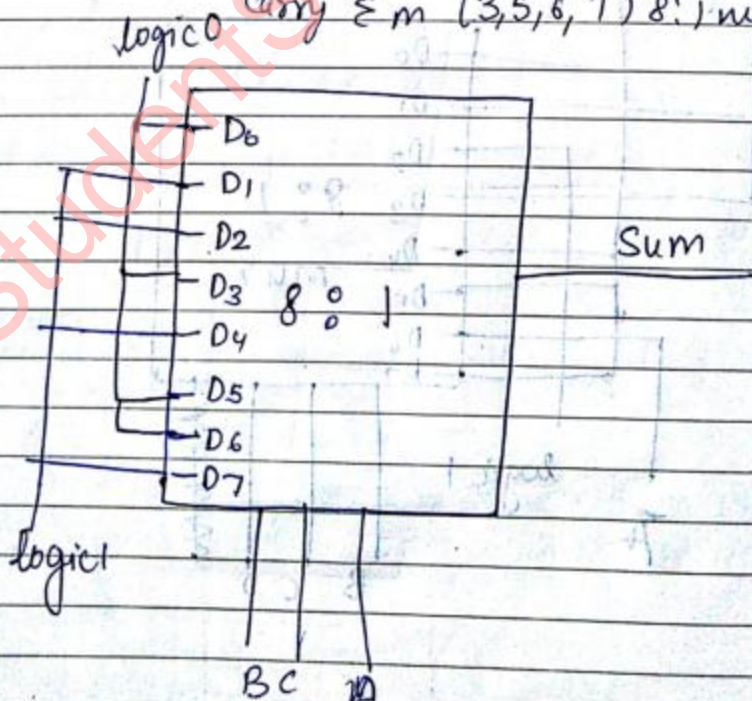

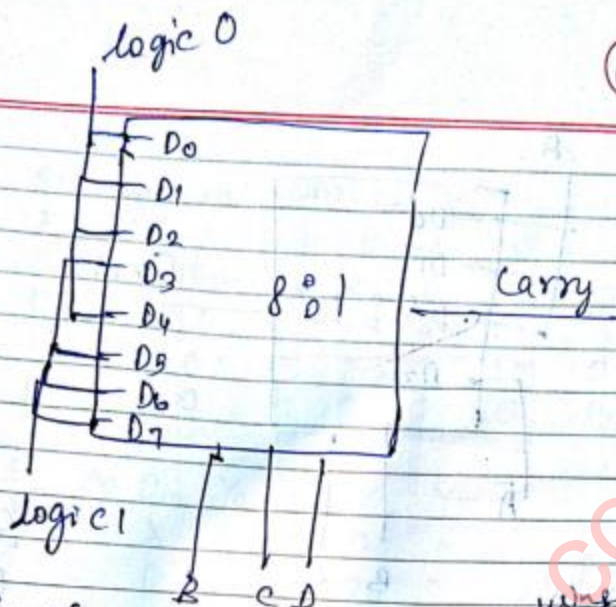


Implementing full adder using 4 to 1 mux.


| | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| A | 4 | 5 | 6 | 7 | 0 | 1 | 2 | 3 |

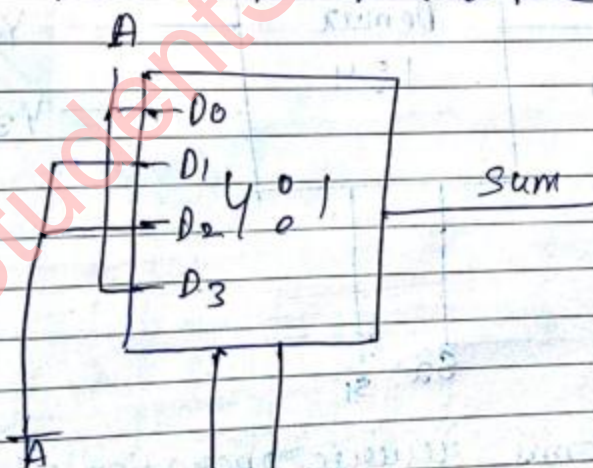

| | D ₀ | D ₁ | D ₂ | D ₃ |
|---|----------------|----------------|----------------|----------------|
| A | 0 | 1 | 2 | 3 |
| A | 0 | 1 | 2 | 3 |

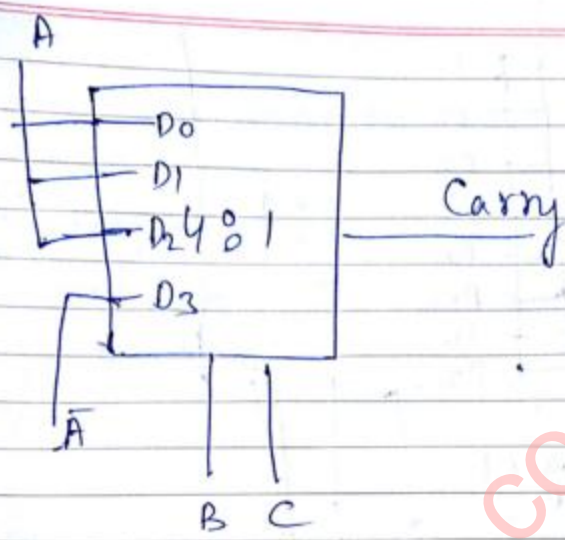

Demux

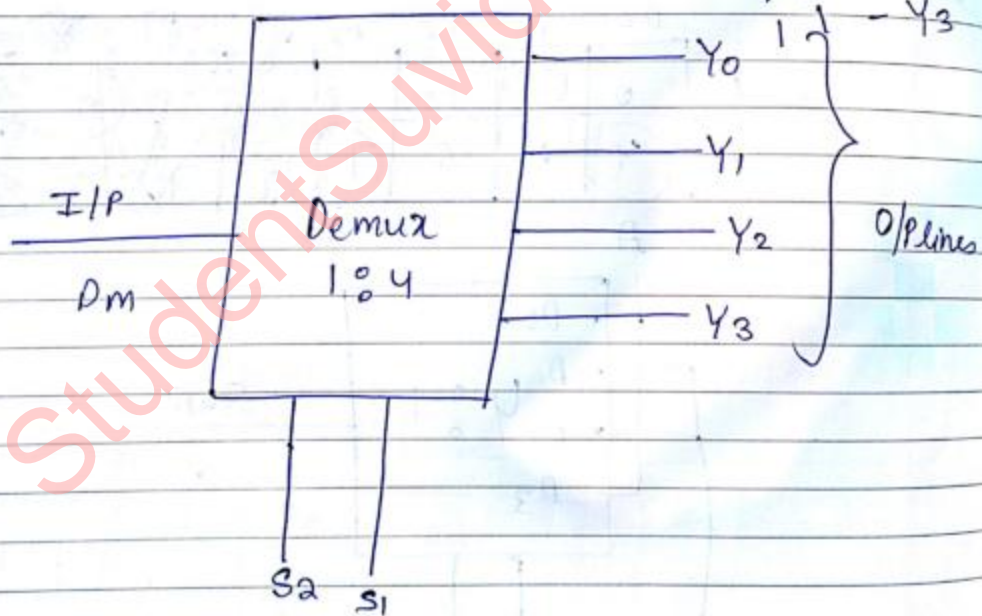

| S_0 | S_1 | |
|-------|-------|--------|
| 0 | 0 | $-Y_0$ |
| 0 | 1 | $-Y_1$ |
| 1 | 0 | $-Y_2$ |
| 1 | 1 | $-Y_3$ |

It performs reverse operation of mux.

| E | S ₁ | S ₀ | Y ₀ | Dm | Y ₀ | Y ₁ | Y ₂ | Y ₃ |
|---|----------------|----------------|----------------|----|----------------|----------------|----------------|----------------|
| 0 | X | X | 0 | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | Dm | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | Dm | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | Dm | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | Dm |

| | E | S ₁ | S ₀ | Dm | Y ₀ | Y ₁ | Y ₂ | Y ₃ |
|----|---|----------------|----------------|----|----------------|----------------|----------------|----------------|
| 8 | 0 | X | X | X | 0 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 10 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 11 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 12 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 13 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 14 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 15 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 16 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

| ES ₁ | S ₀ Dm | 00 | 01 | 11 | 10 |
|-----------------|-------------------|----|----|----|----|
| 00 | | 0 | 0 | 0 | 0 |
| 01 | | 0 | 0 | 0 | 0 |
| 11 | | 0 | 0 | 0 | 0 |
| 10 | | 0 | 0 | 0 | 0 |

$$Y_1 = \overline{S_0} Dm E S_1$$

$$E \overline{S_1} S_0 \overline{Dm}$$

| ES ₁ | S ₀ Dm | 00 | 01 | 11 | 10 |
|-----------------|-------------------|----|----|----|----|
| 00 | | 0 | 0 | 0 | 0 |
| 01 | | 0 | 0 | 0 | 0 |
| 11 | | 0 | 0 | 0 | 0 |
| 10 | | 0 | 1 | 0 | 0 |

$$Y_0 = \overline{S_0} Dm E \overline{S_1}$$

$$Y_0 = S_0 Dm E \overline{S_1}$$


| $S_0 D_m$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| ES_1 | | | | |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 1 | 0 | 0 |
| 10 | 0 | 0 | 0 | 0 |

$$Y_2 = \overline{S_0 D_m} ES_1$$


| $S_0 D_m$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| ES_1 | | | | |
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 0 | 0 | 1 |
| 10 | 0 | 0 | 0 | 0 |

$$Y_3 = \overline{S_0 D_m} ES_1$$
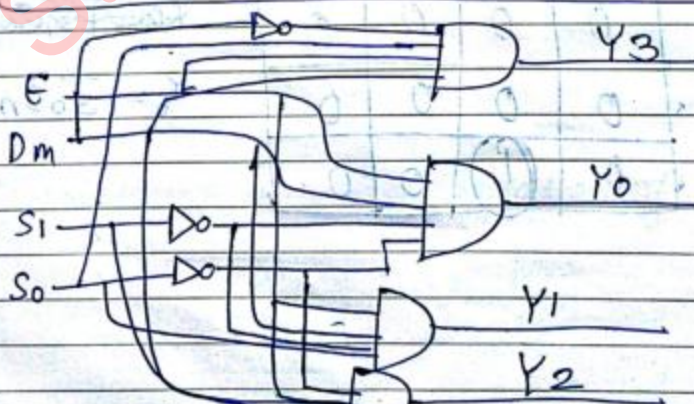
$$Y = \overline{S_0 D_m} ES_1 + E \overline{S_1} S_0 \overline{D_m} + \overline{S_0 D_m} ES_1 + S_0 \overline{D_m} ES_1$$




Demux Tree

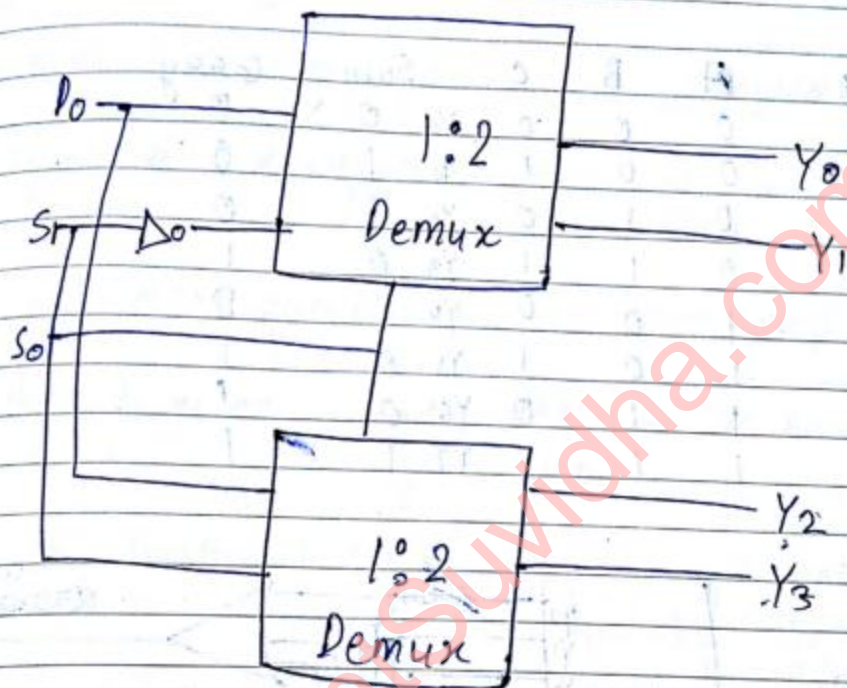

Implement full adder using Demux

| A | B | C | Sum | Carry |
|---|---|---|---------|-------|
| 0 | 0 | 0 | Y_0 0 | 0 |
| 0 | 0 | 1 | Y_1 1 | 0 |
| 0 | 1 | 0 | Y_2 1 | 0 |
| 0 | 1 | 1 | Y_3 0 | 1 |
| 1 | 0 | 0 | Y_4 1 | 0 |
| 1 | 0 | 1 | Y_5 0 | 1 |
| 1 | 1 | 0 | Y_6 0 | 1 |
| 1 | 1 | 1 | Y_7 1 | 1 |

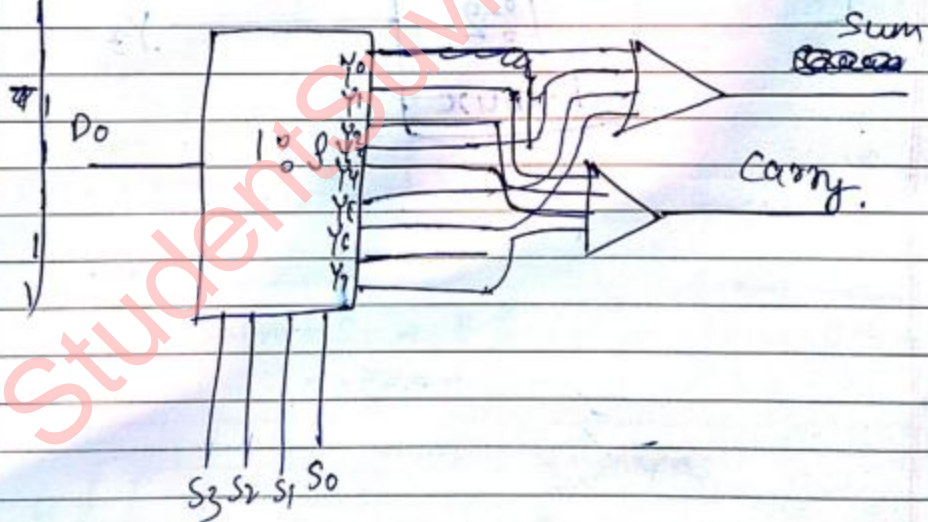

EncoderComparison of Mux and demux

| <u>Mux</u> | <u>demux</u> |
|---|---|
| there is n no. of data input | there is one input. |
| one data output | n data outputs |
| there is m no. of select lines. | there is m no. of select lines |
| combinational logic circuit | It is also a combinational logic circuit. |
| the relation b/w input & output & select lines is $n = 2^m$ | the relation b/w input, output & select line is $n = 2^m$ |
| Its operating principle is many to one. | Its operating principle is one to many. |
| It is also known as <u>data selector</u> | It is known as <u>data distributor</u> . |
| Mux is used in communication system | demux is also used in communication systems. |

Encoder

is a combinational circuit which is design to perform inverse operation of the decoder.




there is no selector in encoder and decoder.

Types of Encoder

- Priority Encoder
- Decimal to BCD n
- ~~Decimal~~ Decimal to Binary n
- hexa decimal to n

Priority Encoder

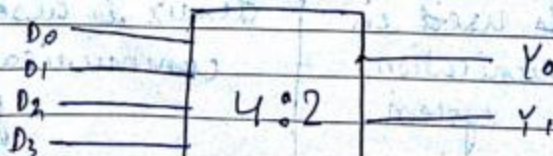


Truth Table

| D_3 | D_2 | D_1 | D_0 | Y_0 | Y_1 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |

| A | 00 | 01 | 10 | 11 |
|----|----|----|----|----|
| 00 | | | | |
| 01 | | | | |
| 11 | | | | |
| 10 | | | | |

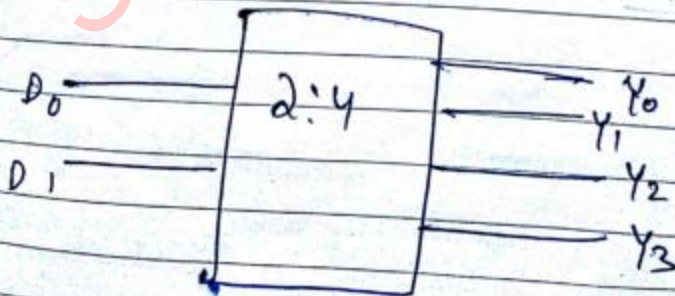
Decoder is a combinational circuit it has n no. of input and 2^n output



| D_0 | D_1 | Y_0 | Y_1 | Y_2 | Y_3 |
|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |

$$D_0 \bar{D}_1 \quad \bar{D}_0 D_1 \quad D_0 \bar{D}_1 \quad D_0 D_1$$
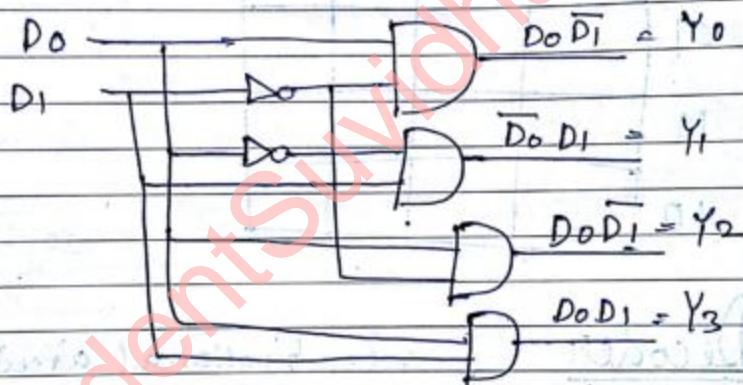
$$Y = D_0 \bar{D}_1 + \bar{D}_0 D_1 + D_0 \bar{D}_1 + D_0 D_1$$



K-Map

$$F(A, B, C, D) = \sum m(1, 5, 6, 12, 13, 14) \\ + d(2, 4)$$

Step 1

| grp | Minterm | Representation | | | |
|-----|--------------|----------------|---|---|---|
| | | A | B | C | D |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 2. | 5 | 0 | 1 | 0 | 1 |
| | 6 | 0 | 1 | 1 | 0 |
| | 12 | 1 | 1 | 0 | 0 |
| 3. | 13 | 1 | 1 | 0 | 1 |
| | 14 | 1 | 1 | 1 | 0 |

StudentSuvidha.com