

B.Tech.  
First Semester Examination, December-2009  
**Electrical Technology (EE-101-F)**

**Note :** Attempt any five questions.

**Q. 1. (a) State Kirchoff's laws of current and voltage.**

**Ans.** For complex circuit computations, the following two laws first stated by Gustav R. Kirchoff are indispensable :


**(i) First Law (Point or Current Law) :** "The sum of currents entering a junction is equal to the sum of the currents leaving the junction."

If the currents towards a junction are considered positive and those away from the same junction negative then this law states that the algebraic sum of all currents meeting at a common junction is zero.

$$\Sigma \text{ current entering} = \Sigma \text{ current leaving}$$

$$I_1 + I_3 = I_2 + I_4 + I_5$$

Or  $I_1 + I_3 - I_2 - I_4 - I_5 = 0$

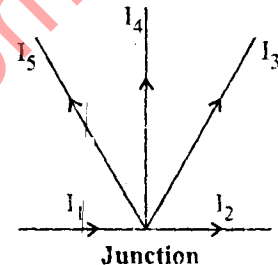

**(ii) Second Law (Mesh or Voltage Law) :** The sum of the emf around any closed loop of a circuit equal the sum of potential drops in that loop. Considering a rise of potential as positive (+) and a drop of potential as negative, (-) the algebraic sum of potential difference around a closed loop of a circuit is zero—


$$\Sigma E - \Sigma IR \text{ drops} = 0 \text{ (around closed loop)}$$

$$\Sigma E = \Sigma IR$$

$$\Sigma \text{ Potential rises} = \Sigma \text{ Potential drops}$$

In tracing through any single circuit whether it is by itself or a part of a network, the following rules must be applied :

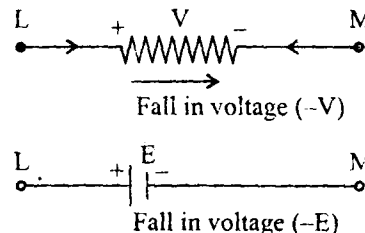(i) A voltage drop exists when tracing through a resistance with or in the same direction as the current or through a battery or generator against their voltage the is from (+ve) to (-ve), refer figure



(ii) A voltage rise exist when tracing through a resistance against or in opposite direction to the current or through a battery or a generator with their voltage that is from (-ve) to (+ve).

**Q. 1. (b) State maximum power transfer theorem.**

**Ans. Maximum Power Transfer Theorem :** This theorem is particularly useful for analyzing communication networks.

"Maximum power output is obtained from a network when the load resistance is equal to the output resistance of the network as seen from the terminals of the load."

Any network can be converted into a single voltage source by the use Thevenin's theorem. The maximum power transfer theorem axis at finding  $R_L$  such that the power dissipated in  $R_L$  is maximum.

$$P = I^2 R_L$$

$$= \left( \frac{E_{th}}{R_{th} + R_L} \right)^2 R_L \dots (i)$$

For  $P$  to be maximum

$$\frac{dP}{dR_L} = 0$$

Differentiating equation, we have

$$\frac{dP}{dR_L} = \frac{E_{th}^2 [(R_{th} + R_L)^2 - 2R_L (R_{th} + R_L)]}{(R_{th} + R_L)^4}$$

$$\frac{E_{th}^2 [(R_{th} + R_L)^2 - 2R_L (R_{th} + R_L)]}{(R_{th} + R_L)^4} = 0$$

From which

$$R_L = R_{th}$$

It is worth noting that under these conditions the voltage across the load is half the open circuit voltage at the terminals  $L$  &  $M$

$$\text{Maximum power } P_{\max} = \left[ \frac{E_{th}}{R_L + R_L} \right]^2 R_L = \frac{E_{th}^2}{4R_L}$$

**Q. 1. (c) What are crest and peak factor?**

**Ans. Crest & Peak Factor :** The a.c. voltage and current wavelength completes a certain no. of cycles in one second, each cycle comprising an identical positive and negative half cycle. The value of the quantities varies from instant to instant peaking at a certain instant only. The rms voltage of the a.c. voltage or current is often used in practice to specify the quantity. It is also called effective or virtual value of alternative quantity. General expression for calculating of rms val: :

$$I_{eff} = I_{rms} = \sqrt{\text{avg } i^2(t)} = \sqrt{\frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}}$$

General expression for the average value of current wave  $T_x$

$$I_{avg} = \frac{i_1 + i_2 + \dots + i_n}{n}$$

Consider an alternating current of sinusoidal waveform flowing through resistance  $R$

$$i = I_m \cos \omega t = I_m \frac{\cos 2\pi}{T} t$$

Instantaneous power dissipation  $p = i^2 R$

Average power dissipation over one cycle

$$P = \left( \frac{1}{T} \int_0^T i^2 dt \right) R = I^2 R$$

Where,

$$I = \left[ \frac{1}{T} \int_0^T i^2 dt \right]^{1/2}$$

$$= \left[ \left( \frac{1}{T} \int_0^T I_m^2 \cos^2 \frac{2\pi}{T} t dt \right) \right]^{1/2}$$

$$= \frac{I_m}{\sqrt{2}}$$

$$I_{avg} = \frac{2I_m}{\pi}$$

The form factor

$$= \frac{I_{(rms)}}{I_{avg}}$$

$$= \frac{\pi}{2\sqrt{2}} = 1.11 \text{ for sinusoidal current and voltage}$$

$$\text{Peak factor} = \frac{I_m}{I_{(rms)}} = \sqrt{2} \text{ for sinusoidal current/voltage}$$

This is also called crest factor or amplitude factor.


**Q. 1. (d) What are cut-off frequencies?**

**Ans. Cut-off Frequency :** The frequency response of an amplifier is mainly presented in the form of a graph that shows output amplitude plotted Vs frequency. Phase angle variation is sometime plotted on the same graph. Figure shows a typical plot of voltage gain of an a.c. amplifier Vs frequency. Notice that the gain is 0 at dc then rises as frequency increases levels off for further increases in frequency, and then begins to drop again at high frequency.

The frequency range over which the gain is more or less constant is called midband range and the gain in that range is designated  $A_m$ . As shown in figure the low frequency at which the gain equals  $(\sqrt{2}/2)A_m = 0.707A_m$  is called lower cut off frequency and designated  $f_1$ . The high frequency at which the gain once again drop to  $0.707A_m$  is called upper cut off frequency and designated  $f_2$ . The bandwidth of the amplifier is defined to be the difference between the upper and lower cut-off frequencies

$$\text{Bandwidth} = BW = f_2 - f_1$$

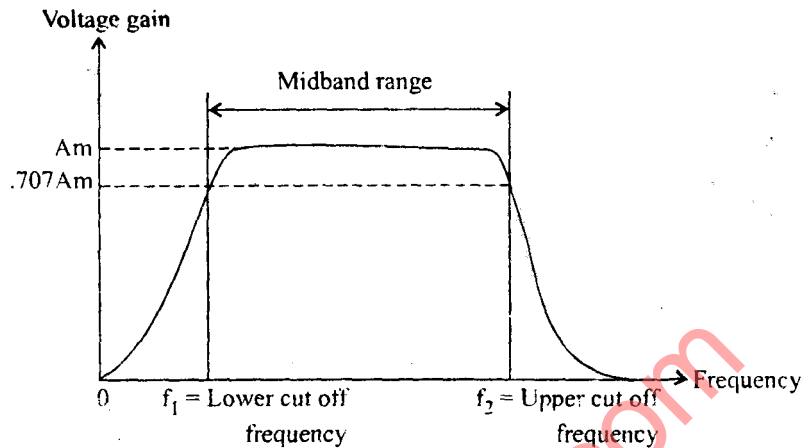The points on the graph in figure where the gain is  $0.707A_m$  are called half power points and cut off frequencies is called half power frequencies.




**Q. 1. (e) What are unbalanced circuits?**

**Ans. Unbalanced Circuit :** Much of the simplifying symmetry goes out the window when a three phase circuit is unbalanced. A circuit sometimes become unbalanced because the generator voltages do not form a symmetrical three phase set. But the unbalanced state often results from loads with unequal impedances.

An unbalance exist in a circuit when the impedances in one or more phases differ from the impedances of the other phases. In such a case, line or phase current are different and are displaced from one another by unequal cycles. We have considered balance loads connected to balanced systems. It is enough to solve problems, considering one phase only on balance loads, the conditions on other two plane being similiar. Problems on unbalanced three phase loads are difficult to handle because conditions in the three phases are different

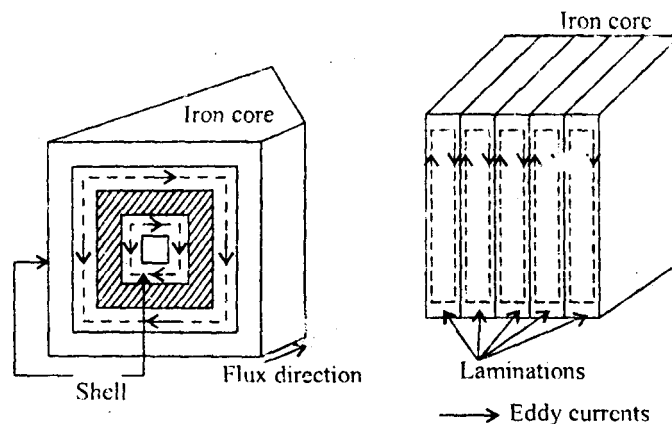**Q. 1. (f) What are eddy currents?**

**Ans. Eddy Current :** When a magnetic core carries a time varying flux, voltage is induced in all possible paths enclosing the flux. The result is the production of circulating currents in the core (all magnetic material are conductors). These currents are known as eddy current and have power loss ( $I^2R$ ) associated with them called eddy current loss



The eddy current loss depend upon the resistivity of the material and lengths of the paths of circulating currents for a given cross section.

**Applications of Utilization of Eddy Current :**

- (i) In induction energy meters eddy current braking is used.
- (ii) Eddy current heating is used for heating materials.
- (iii) Eddy current damping is used in PMMC instruments.

**Q. 1. (g) Explain, what is slip?**

**Ans. Slip :** The rotor speed must always remain less than the synchronous speed. The difference between the synchronous speed and the rotor speed is known as slip. It usually expressed as a fraction of the synchronous speed.

Thus, slip is 
$$S = \frac{N_s - N}{N_s}$$

$$N = N_s (1 - S)$$

$N_s$  = Synchronous speed (r.p.m)

$N$  = Motor speed (r.p.m)

In practice the value of slip is very small. At no load slip is around 1% or so and at full load it is around 3%. For large efficient machines the slip at full load may be around 1% only. The induction motor is therefore a motor with substantially constant speed and fills the same role as d.c. shunt motor :

(i) When the rotor is stationary its speed is zero and  $S = 1$ . The rotor cannot run at synchronous speed because then there will be no rotor emf and no rotor current and torque. If the rotor is to run at synchronous speed an external torque is necessary. If the rotor is driven such that  $N > N_s$ , the slip become negative, the rotor torque opposes external driving torque and the machine acts as induction generator.

(ii) The induction motor derives, its name from the fact that the current in the rotor circuit is induced from the stator. There is no external connection to the rotor except for some special purposes.

**Q. 2. (a) Derive expressions for converting Delta circuit to star circuit.**

**Ans. Derive Expression for Converting Delta to Star ( $\Delta$  to  $Y$ ) :** Consider the two networks, if these are to be identical, then the resistance between any pair of lines should be the same when the third line is kept open.

**In Case of  $\Delta$  Connection :**

**In Case of  $Y$  Connection :**

Therefore

$$R_{AB} = R_{ab} || (R_{bc} + R_{ca}) = R_a + R_b$$

$$R_{BC} = R_{bc} || (R_{ab} + R_{ca}) = R_b + R_c$$

$$R_{CA} = R_{ca} || (R_{bc} + R_{ab}) = R_c + R_a$$

Or

$$R_a + R_b = \frac{R_{ab} (R_{bc} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}}$$

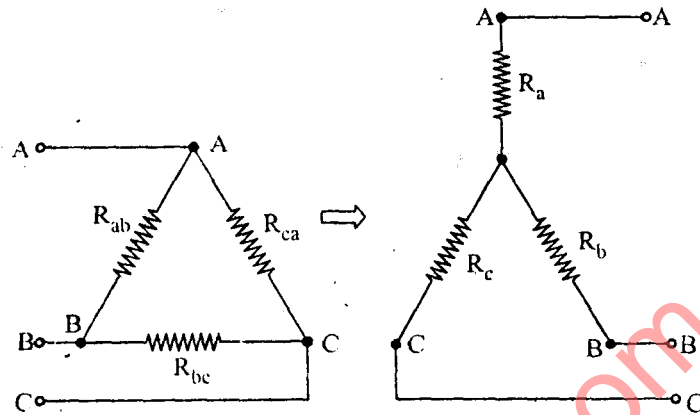


Fig. Delta to Star conversion

On solving parallel combination of  $\{R_{ab} || (R_{bc} + R_{ca})\}$  ..... (i)

$$R_b + R_c = \frac{R_{bc}(R_{ab} + R_{ca})}{R_{ab} + R_{bc} + R_{ca}} \quad \text{..... (ii)}$$

$$R_c + R_a = \frac{R_{ca}(R_{bc} + R_{ab})}{R_{ab} + R_{bc} + R_{ca}} \quad \text{..... (iii)}$$

Solving these three equations for  $R_a, R_b, R_c$  in terms of  $R_{ab}, R_{bc}, R_{ca}$ , we get

$$R_a = \frac{R_{ab} \cdot R_{ca}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ab} \cdot R_{ca}}{\Sigma R_{ab}} \quad \text{.... (a)}$$

$$R_b = \frac{R_{ab} \cdot R_{bc}}{R_{ab} + R_{bc} + R_{ca}} = \frac{R_{ab} \cdot R_{bc}}{\Sigma R_{ab}} \quad \text{.... (b)}$$

$$R_c = \frac{R_{bc} \cdot R_{ca}}{R_{ab} + R_{bc} + R_{ca}} + \frac{R_{bc} \cdot R_{ca}}{\Sigma R_{ab}} \quad \text{.... (c)}$$

Equations (a), (b) & (c) are the required solution.

**Q. 2. (b) Differentiate between :**


**(i) Lumped parameter & distributed parameters**

**(ii) Mesh & Loop**

**(iii) Active and passive components & sources**

**Ans. (i) Lumped Parameter :** "The parameters in the network which are physically separable one known as lumped parameters."

**Example :**

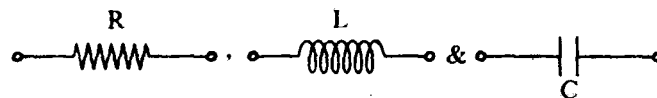

**Distributed Parameters :** "The parameters in the network like R, L etc. equation not be physically separable for analysing purpose."

**Example :** Transmission line

**(ii) Mesh & Loop :**


**Mesh :** It is the most elementary form of loop i.e., which cannot be further divided in other loops. (Mesh is the smallest close path).

**Example :** In figure, only ABEFA & BCDEB qualify the criteria of mesh. But ABCDEFA cannot because it encloses the ABEFA & BCDEB loops.

**Note :** All the meshes are loops but all the loops are not meshes.

**Loop :** It is any closed path of the network.

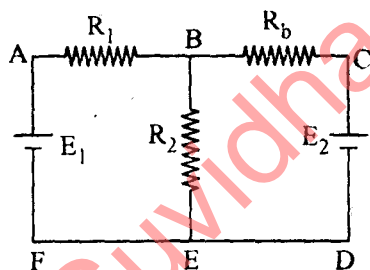**Example :** In figure, there are three (3) possible closed path in loop—ABEFA, BCDEA & ABCDEFA.



**(iii) Active & Passive Component :** "The components which supplies the electrical energy to the circuit, are known as active components or elements."

**Example :** Current force, voltage forces, battery, cell etc.

"The components which receives electrical energy and then either converts it into heat (resistance) or stores in magnetic field (inductance) or electric field (capacitance)."

**Example :** R(resistance), L(inductance), C(capacitance).


**Q. 3. (a) State and explain Thevenin's theorem.**

**Ans. Thevenin's Theorem :** It states that for the purpose of determining the current in a resistor,  $R_L$ , connected across two terminals of a network which contains sources of e.m.f. and resistors, the network can be replaced by a single source of e.m.f. and a series resistor  $R_{th}$ . This e.m.f.,  $E_{th}$  is equal to potential difference between the terminals of the network when the resistor,  $R$  is removed; the resistance of series resistor,  $R_{th}$  is equal to the equivalent resistance of the network with the resistor,  $R$  removed C or it is sometimes called, "the resistance of the network when viewed from the terminals under consideration."

Hence

$$I = \frac{E}{R_L + R_{th}} \quad \dots (i)$$

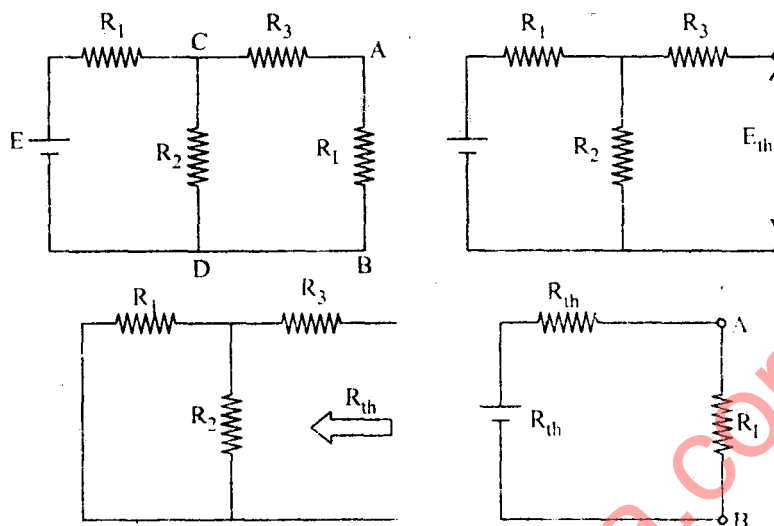**Explanation :** Let us consider the circuit



The following steps are required to find current through the load resistance  $R_L$  :

(i) Remove  $R_L$  from the circuit terminals  $A$  &  $B$  and redraw the circuit obviously the terminals have been open circuited.

(ii) Calculate the open circuit voltage ( $V_{oc} = E_{th}$ ) which appears across terminals  $A$  &  $B$ , when they are open i.e., when  $R_L$  is removed. This voltage is  $E_{th}$ . A little thought will reveal that

$$E_{th} = \frac{ER_2}{R_1 + R_2} \quad \dots (ii)$$

$$\left[ \because I = \frac{E}{R_1 + R_2} \text{ \& } E_{th} = IR_2 = \frac{ER_2}{R_1 + R_2} \right]$$

(iii) Short circuit the battery and find the thevenin resistance  $R_{th}$  of the network as seen from the terminals  $A$  &  $B$ .

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} + R_3 \quad \dots (iii)$$


(iv) Connect  $R_L$  back across the terminals  $A$  &  $B$  from where it was temporarily removed earlier.

$$\text{Current through } R_L \text{ is given by } I = \frac{E_{th}}{R_{th} + R_L} \quad \dots (iv)$$
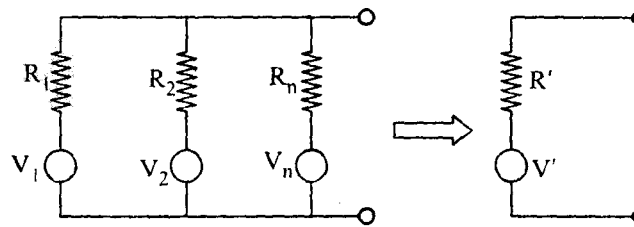
### Q. 3. (b) State and explain Millman's theorem.

Ans. Millman's theorem states that in any network, if the voltage sources  $V_1, V_2, \dots, V_n$  in series with internal resistances  $R_1, R_2, \dots, R_n$  respectively, are in parallel then these sources may be replaced by a single voltage source  $V$  in series with  $R$  as shown in figure.





Where,


$$V = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

Here,  $G_n$  is the conductance of the  $n^{\text{th}}$  branch

&

$$R' = \frac{1}{G_1 + G_2 + \dots + G_n}$$

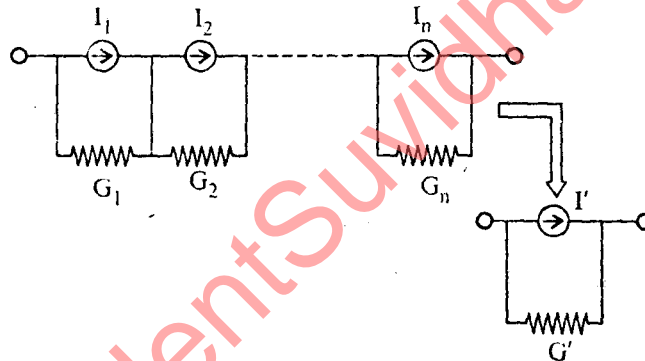As similar theorem can be stated for  $n$ -current sources having internal conductances which can be replaced by a single current source  $I'$  in parallel with an equivalent conductance.



Where,

$$I' = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

&


$$G' = \frac{1}{R_1 + R_2 + \dots + R_n}$$

**Q. 4. (a) Explain the behaviour of R-C circuits to step response.**

**Ans. Response (Step response) of R.C. Circuit :** The figure shows a series RC circuit. It is assumed that the initial energy in the network is zero, and the step input is shown by  $u(t)$ .

If the excitation is a step voltage, the physical analogy is that of a switch-closing at time  $t = 0$ , which connects a low voltage battery to the circuit.

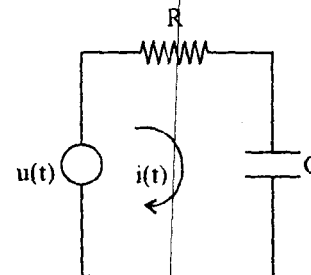Consider the circuit of figure (i). The voltage equation can be written as



$$u(t) = Ri(t) + \frac{1}{C} \int_0^t i(t) dt \quad \dots (i)$$


By laplace transform method equation (i) can be written in S-domain as

$$1 = RI(s) + \frac{1}{C} \left[ \frac{I(s)}{s} \right]$$

$$I(s) = \frac{1/R}{s - 1/RC}$$

Changing above equation to time domain

$$i(t) = \frac{1}{R} e^{\frac{1}{RC}t}$$

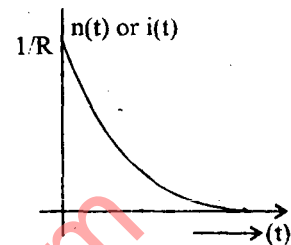

.... (ii)

The time response of equation (ii) is drawn here under

**Q. 4. (b) Explain the concept of voltage and current in RL, RC & RLC circuits with the help of phasor diagrams.**

**Ans. Series R-L Circuit :**

Let  $V$  = Supply voltage

$I$  = Circuit current

$V_R$  = Voltage drop across  $R$

$$V_R = I \cdot R$$

$V_L$  = Voltage drop across  $L$

$$V_L = I \cdot X_L$$

$$X_L = 2\pi fL$$

$$V_L = I \cdot 2\pi fL$$

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$= \sqrt{I^2 R^2 + I^2 X_L^2}$$



$$V = I \sqrt{R^2 + X_L^2}$$

$$\frac{V}{I} = \sqrt{R^2 + X_L^2}$$


Let

$$Z_L = \sqrt{R^2 + X_L^2}$$

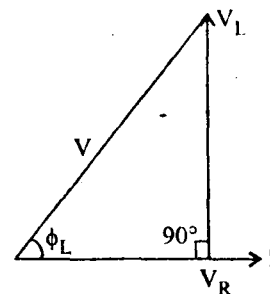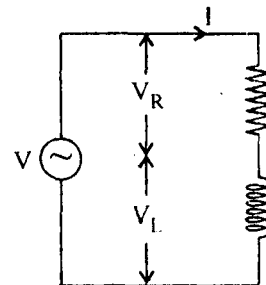The quantity  $Z_L$  is called the impedance of a series R-L circuit



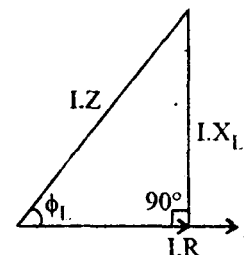Since  $I$  is common to both element  $R$  &  $L$ , this is used as reference phasor. The voltage is in phase with  $I$  &  $V_L$  leads by  $90^\circ$



$$\frac{V}{I} = Z_L$$

From impedance  $\Delta$ ,

$$\tan \phi_L = \frac{X_L}{R}$$

$$\cos \phi_L = \frac{R}{Z}$$

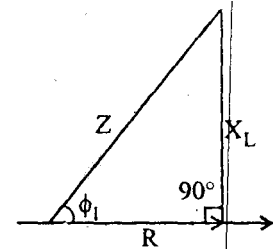


Fig. Impedance triangle for a series R-L circuit

### Series R-C Circuit :

Let

$V$  = Supply voltage

$I$  = Supply current

$V_R$  = Voltage across  $R$

$$V_R = I \cdot R$$

$V_C$  = Voltage across  $C$

$$V_C = I \cdot X_C$$

$$X_C = \frac{1}{2\pi f c}$$

$$V_C = \frac{I}{2\pi f c}$$

$$\vec{V} = \vec{V}_R + \vec{V}_C$$

$$V = \sqrt{V_R^2 + V_C^2}$$

$$= \sqrt{I^2 R^2 + I^2 X_C^2}$$

$$V = I \sqrt{R^2 + X_C^2}$$

$$\frac{V}{I} = \sqrt{R^2 + X_C^2}$$

Let

$$Z_C = \sqrt{R^2 + X_C^2}$$


The quantity  $Z_C$  is called the impedance of series R-C circuit

$$\frac{V}{I} = Z_C$$

From impedance  $\Delta$ ,

$$\tan \phi_c = \frac{X_C}{R}$$

$$\cos \phi_c = \frac{R}{Z}$$

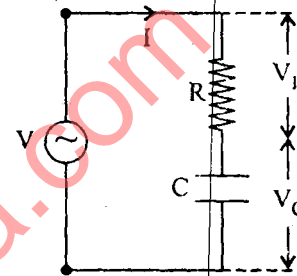

$I$  is common to takes as a reference

$I$  leads  $V$  by an angle  $90^\circ$

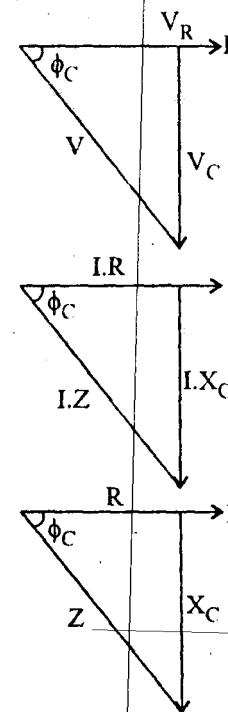


Fig. Impedance triangle of series R-C circuit

**Series R-L-C Circuit :** There are four voltages in the circuit,

$V_R$  in phase with  $I$

$V_L$  leads  $I$  by  $90^\circ$

$V_C$  lags  $I$  by  $90^\circ$

$V$  in the phasor sum of  $V_R$ ,  $V_L$  &  $V_C$

$$V = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

Thus,  $V_L$  &  $V_C$  are in opposite directions. The resultant of  $V_L$  &  $V_C$  is therefore the arithmetical difference between them.

There are three possible cases of the series RLC circuit

(a)  $V_L > V_C$  i.e.,  $X_L > X_C$

(b)  $V_L < V_C$  i.e.,  $X_L < X_C$

(c)  $V_L = V_C$  i.e.,  $X_L = X_C$

**Case I :**  $V_L > V_C$

When  $X_L > X_C$ , the circuit is predominantly inductive

$$V^2 = V_R^2 + (V_L - V_C)^2$$

$$= (I.R)^2 + \{(IX_L) - (IX_C)\}^2$$

$$= I^2 R^2 + I^2 [(X_L - X_C)^2]$$

$$V^2 = I^2 [R^2 + (X_L - X_C)^2]$$

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$\frac{V}{I} = \sqrt{R^2 + (X_L - X_C)^2}$$



Let  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$Z$  is the impedance of series RLC circuit

$$\boxed{\frac{V}{I} = Z}$$

From impedance  $\Delta$

$$\tan \phi = \frac{(X_L - X_C)}{R}$$

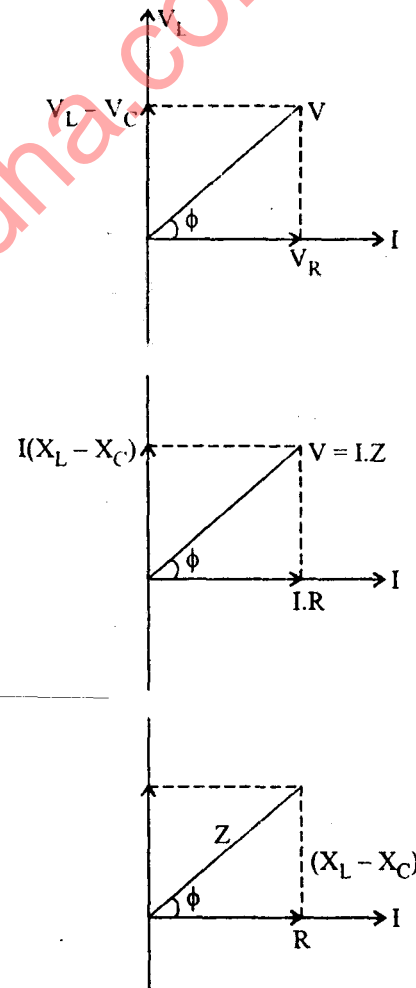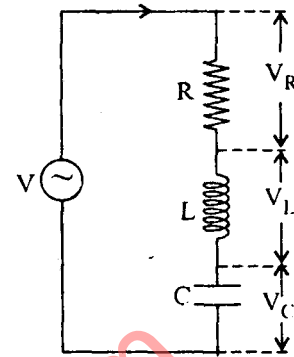

**Fig. Impedance  $\Delta$  of series RLC circuit**

$$\cos \phi = \frac{R}{Z}$$

Case II :  $V_L < V_C$

When  $X_C > X_L$ , the circuit is predominantly capacitive

$$\begin{aligned} V^2 &= V_R^2 + (V_C - V_L)^2 \\ &= I^2 R^2 + [IX_C - IX_L]^2 \\ &= I^2 R^2 + [I(X_C - X_L)]^2 \\ V^2 &= I^2 [R^2 + (X_C - X_L)^2] \end{aligned}$$

$$V = I \sqrt{R^2 + (X_C - X_L)^2}$$


Let 
$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

The quantity  $Z$  is called the impedance of series RLC circuit.

From impedance  $\Delta$ ,


$$\tan \phi = \frac{(X_C - X_L)}{R}$$

$$\cos \phi = \frac{R}{Z}$$

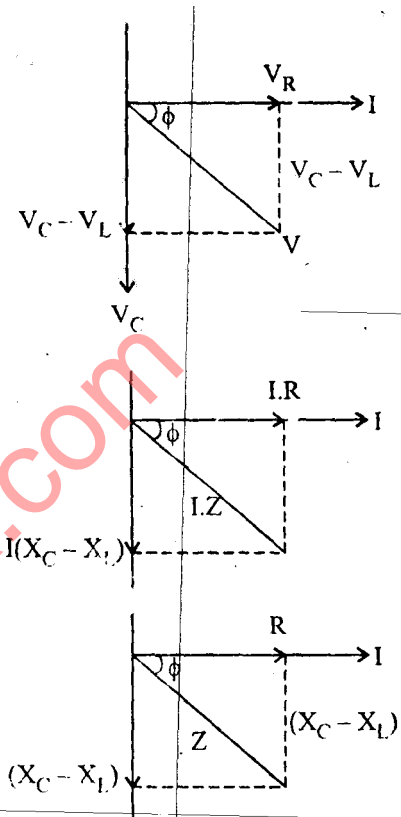

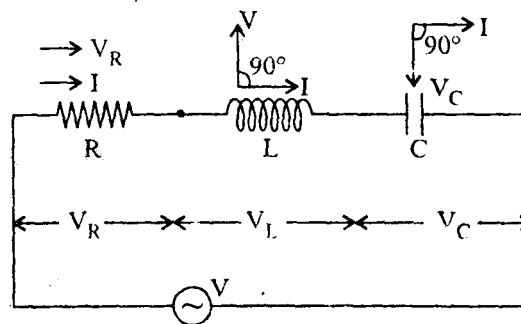**Q. 5. (a) Derive results of resonant frequency, bandwidth and impedance in case of series RLC circuits.**

**Ans.** Consider a circuit containing a resistance  $R$ , and inductance  $L$  and a capacitance  $C$  connected in series as shown in the figure.



$V_R$  = Voltage drop across  $R$  &  $I$  &  $V$  are in phase

$V_L$  = Voltage drop across  $L$  &  $V$  leads  $I$  by an angle  $90^\circ$

$V_C$  = Voltage drop across  $C$  &  $I$  leads  $V$  by an angle  $90^\circ$

(Under the condition of resonance, the inductive reaction ( $X_L$ ) and the capacitive reactance ( $X_C$ ) should be made equal and voltage and the current are in phase i.e., the power factor becomes unity and network is purely resistive) and the frequency at which it occurs is known as resonant frequency for

$$X_L = X_C$$

(i) Net reactance  $X = X_L - X_C = 0$

(ii) Impedance of the circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$Z = \sqrt{R^2 + 0} \Rightarrow \boxed{Z = R}$$

If resonant frequency is denoted by  $f_r$ , then

$$X_L = \omega L = 2\pi f_r L$$

&

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f_r C}$$

For resonance

$$X_L = X_C$$


$\therefore$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

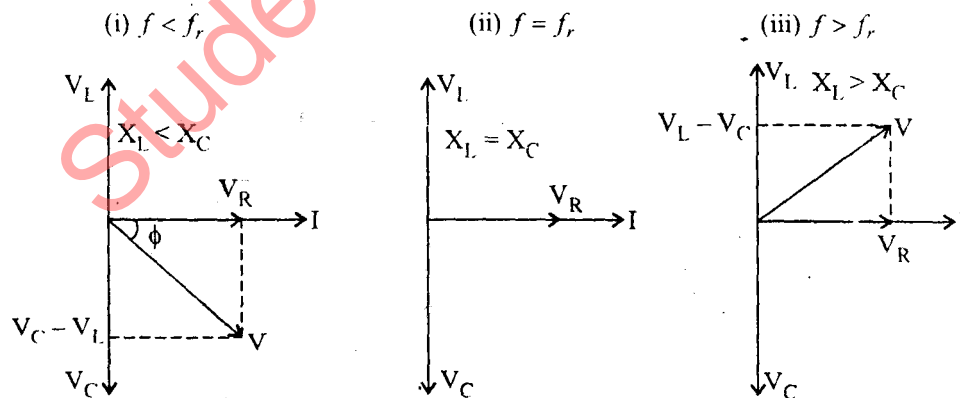**Resonant Frequencies in Series :**

$$\boxed{f_r = \frac{1}{2\pi\sqrt{LC}}} \text{ or } \omega_r = \sqrt{1/LC}$$

Phasor diagrams for series  $RLC$  circuit shown in figure at three different frequencies with  $L$  and  $C$  kept constant.




**Note :** Since in this resonance the voltage is maximum. It is called voltage resonance. The series resonance is also called acceptor circuit. Such a circuit accepts current at one particular frequency but rejects current of other frequencies.

**Bandwidth Determination :** The bands of frequencies while lie between points on either side of the resonant frequency where current is  $1/\sqrt{2}$  times of max current  $I_{\max}$ .

Bandwidth  $\Delta f = f_2 - f_1$  and  $f_1$  &  $f_2$  at the limits of the bandwidth are called half power points on the frequency scale.

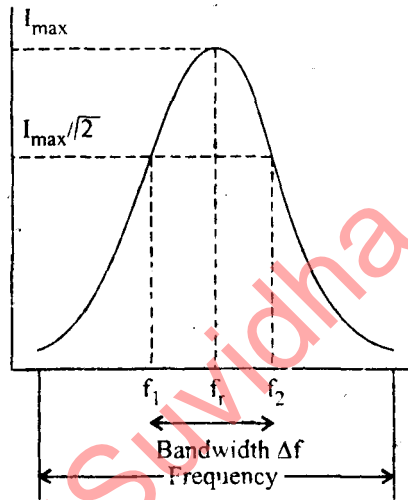The impedance of the tuned circuit must be  $\sqrt{2}$  times its impedance at resonance so that the current is  $I_{\max}/\sqrt{2}$ . But the impedance at resonance  $Z = R$  so at half power points the impedance is  $\sqrt{2}R$ , since  $Z = \sqrt{R^2 + X^2}$ , therefore  $\sqrt{2}R = \sqrt{R^2 + X^2}$  or  $X = R$ . Now this information cannot be used to obtain an expression for the bandwidth.



The reactance at linear half power frequency  $X_1$

$$X_1 = \omega_1 L - \frac{1}{\omega_1 C} = -R$$

(Minus sign appears on the right hand side of the equation because below resonance the capacitance reactance exceeds the  $X_L$ .)

$$\omega_1^2 + \frac{R}{L} \omega_1 - \frac{1}{LC} = 0$$

**Example :**

$$\begin{aligned} \omega_1 &= -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ &= -\alpha \pm \sqrt{\alpha^2 + \omega_r^2} \end{aligned}$$

Where,  $\alpha = \frac{R}{2L}$  &  $\omega_r = \sqrt{1/LC}$

On solving, we get

Lower half power frequency  $\omega_1 = -\alpha + \sqrt{\alpha^2 + \omega_r^2}$  .... (i)

Similarly the upper half power frequency

$$X_2 = \omega_2 L - \frac{1}{\omega_r C} = +R$$

Or  $\omega_2^2 - \frac{R}{L} \omega_r - \frac{1}{LC} = 0$

Or  $\omega_2 = \alpha + \sqrt{\alpha^2 + \omega_r^2}$

So the equation for the bandwidth becomes

$$\begin{aligned} \omega_{bw} &= \omega_2 - \omega_1 = \alpha + \sqrt{\alpha^2 + \omega_r^2} - \left[ -\alpha + \sqrt{\alpha^2 + \omega_r^2} \right] \\ &= 2\alpha = \frac{R}{L} \end{aligned}$$

& bandwidth

$$\Delta f = f_2 - f_1 = \frac{\omega_2 - \omega_1}{2\pi}$$

$$\Delta f = \frac{R}{2\pi L} \text{ Hz}$$

Lower half power frequency


$$f_1 = f_r - \frac{\Delta f}{2} = f_r - \frac{R}{4\pi^2} \text{ Hz}$$

Upper half power frequency


$$f_2 = f_r + \frac{\Delta f}{2} = f_r + \frac{R}{4\pi^2} \text{ Hz}$$

Q. 5. (b) Derive relation between  $I_c$  &  $I_{ph}$ ,  $V_c$  &  $V_{ph}$  in case of star connected three phase circuit.

Ans.

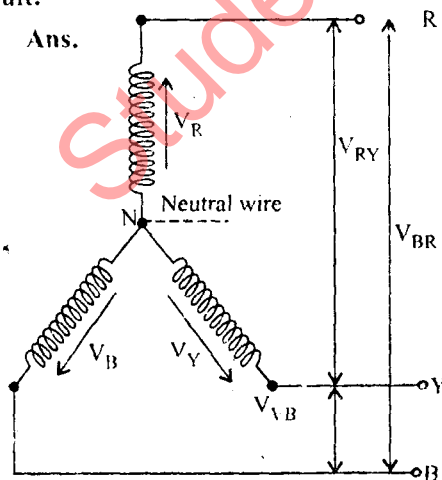

(a) Connection diagram

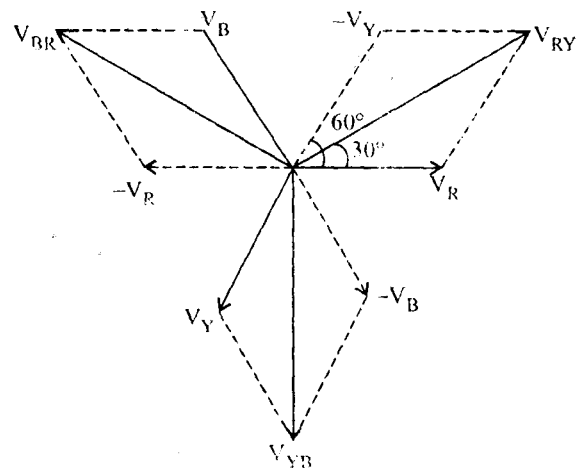

(b) Phase diagram of line & phase voltage

Fig. Three phase star connected system



The three phase 4 wire star connected system is shown in figure (a). The voltage between any line and the neutral point i.e., voltage across the phase winding is called phase voltage ( $V_{ph}$ ) while the voltage between two line is called the line voltage ( $V_L$ ).

The neutral point is usually earth connected.

In figure (a) the three phase are numbered as usually done  $R$ ,  $Y$  &  $B$  indicate the three neutral columns red, yellow and blue respectively.

In figure (b), the emf induced in 3 phase are shown by the phases.

From the phasors, potential difference between line  $R$  &  $Y$ .

$$V_{RY} = V_R - V_Y \text{ (phasor difference)}$$

Or 
$$V_{RY} = V_R + (-V_Y) \text{ (phasor sum)}$$

Since angle between  $V_R$  and  $(-V_Y)$  is  $60^\circ$

$\therefore$  From phasor diagram 
$$V_{RY} = \sqrt{V_R^2 + V_Y^2 + 2V_R V_Y \cos 60^\circ} \quad \dots (a)$$

Let 
$$V_R = V_Y = V_B = V_P \text{ (all are phase voltage)}$$

Then from equation (a) 
$$V_{RY} = \sqrt{V_P^2 + V_P^2 + 2V_P V_P \times \frac{1}{2}} = \sqrt{3}V_{ph}$$

In balanced star connected system  $V_{RY}$ ,  $V_{YB}$ ,  $V_{BR}$  are equal in magnitude and are known line voltage

$$V_{RY} = V_{YB} = V_{BR} = V_L$$

Similarly potential difference between line  $Y$  and  $B$  &  $B$ ,  $R$

Or 
$$V_{YB} = V_Y - V_B = \sqrt{3}V_{ph}$$

$$V_{BR} = V_B - V_R = \sqrt{3}V_{ph}$$

Is 
$$V_L = \sqrt{3}V_{ph} \quad \dots (i)$$

Since in star connected system each line conductor is connected to separate phase, so current through the lines and phase are same i.e., line current = phase current

$$I_L = I_{ph}$$

**Q. 6. (a) Explain how three phase power can be measured by two wattmeter method?**

**Ans. Two Wattmeter Method :** Balanced or unbalanced load figure show connection diagram for star connected and delta connected loads respectively. In this method the current coils of the two wattmeters are inserted in any two lines and the pressure coil of earth joined to the third line.

It can be proved that the sum of the instantaneous powers indicated by  $W_1$  &  $W_2$  gives the instantaneous power absorbed by the three loads  $L_1$ ,  $L_2$  &  $L_3$ . Let us consider a star connected load.

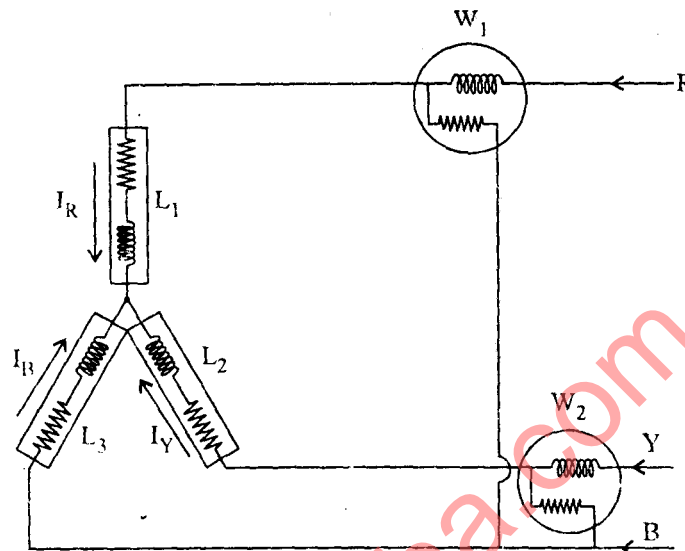


Fig. Star connected load

Keeping in mind that it is important to take the direction of the voltage though the circuit the same as that taken for the current which establishing the reading of the two wattmeters.

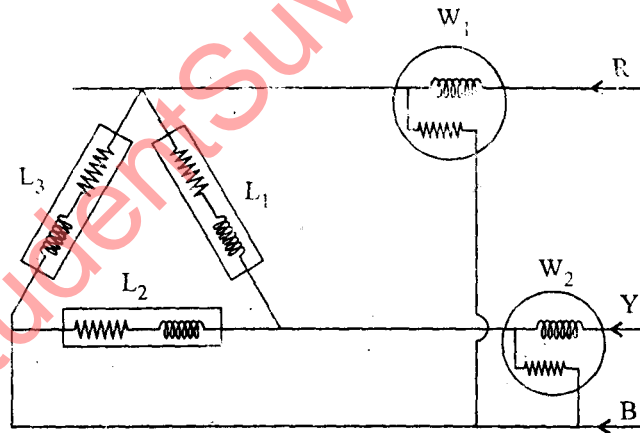


Fig. Delta connected load

Instantaneous current through  $W_1 = i_R$

Instantaneous potential difference across

$$\begin{aligned} W_1 &= e_{RB} \\ &= e_R - e_B \end{aligned}$$

Instantaneous power read by  $W_1 = i_R (e_R - e_B)$

Instantaneous current through  $W_2 = i_Y$

Instantaneous potential difference across

$$W_2 = e_{YB} = e_Y - e_B$$

Instantaneous power read by  $W_2 = i_Y (e_Y - e_B)$

$$\begin{aligned} W_1 + W_2 &= i_R (e_R - e_B) + i_Y (e_Y - e_B) \\ &= i_R e_R + i_Y e_Y - e_B (i_R + i_Y) \end{aligned}$$

Now according to Kirchhoff law

$$i_R + i_Y + i_B = 0$$

$$i_R + i_Y = -i_B$$

$$\begin{aligned} W_1 + W_2 &= i_R e_Y + i_Y e_Y + i_B e_B \\ &= P_1 + P_2 + P_3 \end{aligned}$$

Where,  $P_1$  = Power absorbed by load  $L_1$

$P_2$  = Power absorbed by load  $L_2$

$P_3$  = Power absorbed by load  $L_3$

$W_1 + W_2$  = Total power absorbed

This proof is true whether the load is balanced or unbalanced.

In case, the load is star-connected then it should have no neutral connection and if it has a neutral connection that it should be exactly balance so that in each case there is no neutral current in otherwise Kirchhoff law will give.

$$i_P + i_Y + i_R + i_N = 0$$

In the above derivation we have considered the instantaneous reading. In fact the moving system wattmeter due to its inertia, cannot quickly follow the variations taking place in cycle, hence it indicates the average power.

$$\begin{aligned} \text{Total power} &= W_1 + W_2 \\ &= \frac{1}{T} \int_0^T i_R e_{RR} dt + \frac{1}{T} \int_0^T i_Y e_{BB} dt \end{aligned}$$

**Q. 6. (b) Draw and explain the construction of transformer and derive emf. equation.**

**Ans. Transformer Construction :** All transformer have the following essential elements :

- (i) Two or more electrical windings insulated from each other and from the core.
- (ii) A core which in case of a single phase distribution transformers usually comprises cold rolled silicon steel strip.

**Other Necessary Parts :** (i) A suitable container for the assembled core and winding.


(ii) A suitable medium for insulating the core and its winding from each other and from container.

(iii) Suitable bushing for insulating and bringing the terminals of the windings out of case.

The two types of transformers are :

[Download all btech stuff from StudentSuvidha.com](http://StudentSuvidha.com)

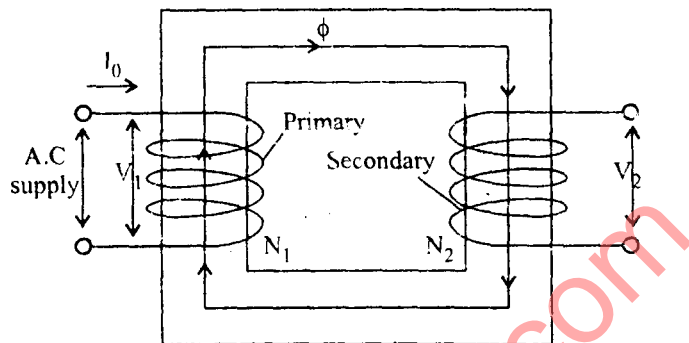
**(i) Core Type Transformer :** The complete magnetic circuit of the core type transformer is in the shape of the hollow rectangle as shown in which  $I_0$  is the no load current and  $\phi$  is the flux produced by it.  $N_1$  &  $N_2$  be the no. of turns on primary and secondary sides respectively.



The core is made up of silicon steel laminations which are either rectangular or L-shaped. In order to provide maximum linkage between windings, the group on each leg is made up of both high tension and low tension coils.

By placing the high voltage winding around the low voltage winding, only one layer of high voltage insulation is required, that between the two coils. If high voltage coils were adjacent to the core, an additional high voltage insulation layer would be necessary between the coil and iron core.

**(ii) Shell Type Transformer :**

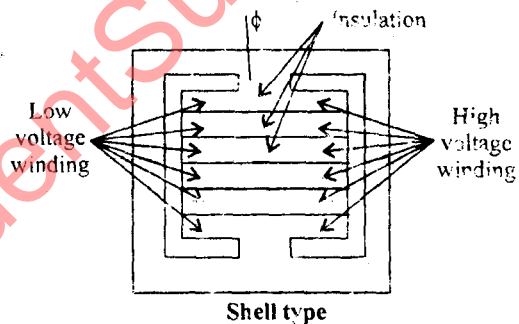

In the shell type construction the iron almost entirely surrounds the copper. The core is made up of E-shaped or F-shaped laminations which are stacked to give a rectangular figure eight. All the windings are placed on the central leg and in order to reduce leakage, each high side coil is adjacent to a low coil. The coil actually occupy the entire space of both windows are flat or pancake in shape and are auxiliary constructed of strip copper again to reduce the account the high voltage insulation required, the low voltage coils are placed adjacent to the iron core.

**Emf Equation of a Transformer :**

$N_1$  = No. of turns in primary

$N_2$  = No. of turns in secondary

$\phi_m$  = Maximum flux in the core

$$= B_m \times A$$

$B_m$  = Maximum flux density

$A$  = Area

$f$  = Frequency of ac input

Refer figure since the flux increase from its zero value to maximum value  $\phi_m$  in one quarter of the cycle in  $T/4$  sec.

$$\text{Average rate of change of flux} = \frac{\phi_m}{1/4 T} = 4 f \phi_m \text{ Wb/s or volt}$$

If flux varies sinusoidally then r.m.s. value of emf is obtained by multiplying the average value with form factor.

But form factor

$$= \frac{\text{r.m.s. value}}{\text{Average value}} = 1.11$$

r.m.s. value of emf

$$= 1.11 \times 4 f \phi_m = 4.44 f \phi_m$$

Now r.m.s. value of induced emf in the whole of primary winding

$$E_1 = 4.44 f \phi_m N_1$$

Similarly r.m.s. value of induced emf in the secondary is


$$E_2 = 4.44 f \phi_m N_2$$

In an ideal transformer on no load

$$V_1 = E_1 \text{ \& } V_2 = E_2$$

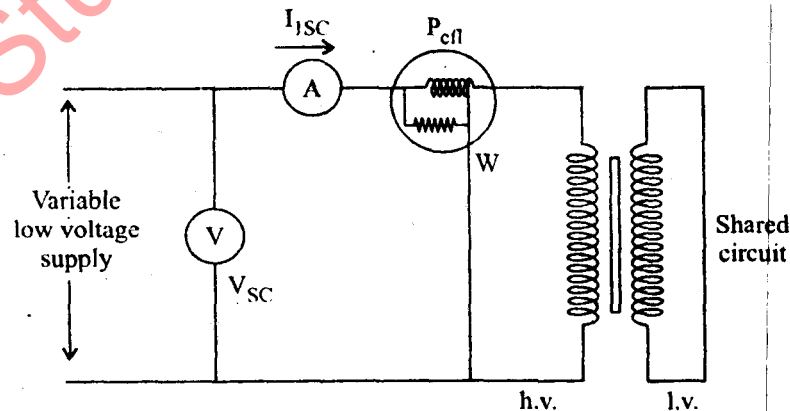**Q. 7. (a) Explain how S.C. test is performed and why?**

**Ans. SC Test or Impedance Test :** In the SC test, usually the low voltage side is short circuited by a thick conductor.



An ammeter, a voltmeter and a wattmeter are connected on the high voltage (h.v.) side.

The reasons for short circuiting the l.v. side and taking measurement on the hv side are as follows :

(i) The rated current on hv side is lower than that on lv side, this current can be safely measured with the available laboratory ammeter.

(ii) Since the applied voltage is less than 5% of the rated voltage of the winding, greater accuracy in the reading of the voltmeter is possible when the hv side is used as a primary.

The high voltage winding is supplied at the reduced voltage from a variable supply. The supply voltage is gradually increased until full load primary current flows, when the rated full load current flows in the primary winding rated full load current will flow in the secondary winding by transformer action.

Readings of the ammeter, voltmeter and wattmeter are noted.

The readings of the instruments in a SC test are as follows :

(i) Ammeter reading = Full load primary current,  $I_{1SC}$

(ii) Voltmeter reading = Short circuit voltage  $V_{1SC}$

**Wattmeter Reading :** Full load copper loss of the transformer (since the applied voltage is low (usually 5 to 10% of normal rated supply voltage). The flux  $\phi$  produced is low, also, core loss is nearly proportional to flux<sup>2</sup>, the core loss is so small that it can be neglected. However, the windings are carrying normal full load currents and therefore input is supplying the normal full load copper losses. Thus, the wattmeter gives the full load copper loss,  $P_{eff}$ , the output voltage  $V_2$  is zero because of is short circuit.

Consequently whole of the primary voltage is used in supplying the voltage drop in the total impedance  $Z_{1e}$  referred to the primary.

$$V_{1SC} = I_{1SC} Z_{1e}$$

From this test, the following calculation can be made :

(i) Equivalent resistance,  $R_{eq} = \frac{P_{eff}}{I_{1SC}^2}$

(ii) Equivalent impedance,  $Z_{eq} = \frac{V_{1SC}}{I_{1SC}}$

(iii) Equivalent reactance,  $X_{eq} = \sqrt{Z_{eq}^2 - R_{eq}^2}$

&  $\cos \phi_{SC} = \frac{R_{eq}}{Z_{eq}}$


The above values are referred to the hv side in above case, if desired, the values could be easily calculated referred to other side also.

The purpose of this test is to determine full load copper loss and equivalent resistance and equivalent reactance referred to metering side (hv side).

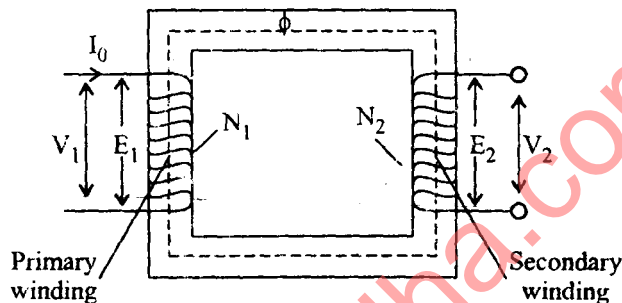**Q. 7. (b) Draw and explain the phasor diagram of transformer with no load and full load.**

**Ans. Transformer on No Load :** A transformer is said to be on no load when the secondary winding is open circuited. The secondary current is thus zero. (There is no load on secondary).

When an alternating voltage is applied to the primary, a small current  $I_0$  i.e., no load current of the transformer flows in the primary. It is made up of two components  $I_\mu$  &  $I_w$ . The component  $I_\mu$  is called the magnetizing component which magnetizes the core. In other words, it sets up a flux in the core and therefore  $I_\mu$  is in the phase with  $\phi_M$ . The current  $I_w$  is also called reactive or wattless components of no load current.



The component  $I_w$  supplies the hysteresis and eddy current losses in the core and the negligible  $I^2 R$  loss in the primary winding. The current  $I_w$  is called active component or wattful component of no load current and it is in phase with the applied voltage  $V_1$ .

For a transformer on no load, we have

$$\phi = \phi_m \sin \omega t$$

$$e_1 = E_{1m} \sin(\omega t - \pi/2)$$

$$e_2 = E_{2m} \sin(\omega t - \pi/2)$$

Since  $E_1$  &  $E_2$  are induced by the same flux  $\phi_1$  they will be in phase with each other.  $E_2$  differs in magnitude from  $E_1$  because

$$E_2 = E_1 \frac{T_2}{T_1} = \frac{E_1}{a}$$

If the voltage drops in the primary winding are neglected,  $E_1$  will be equal and opposite to the applied voltage  $V_1$ .

$I_\mu$  is in phase with  $\phi_m$  and

$I_w$  is in phase with  $V_1$


The phasor sum of  $I_\mu$  &  $I_w$  is  $I_0$ .

Angle  $\phi_0$  is called the no load power factor angle. So that the power factor on no load is  $\cos \phi_0$ .

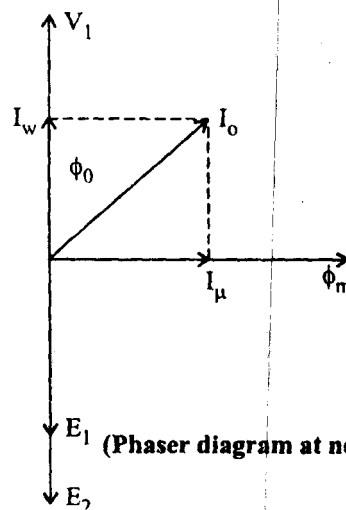**From the Phasor Diagram :**

$$I_w = I_0 \cos \phi_0 \quad \dots (i)$$

$$I_\mu = I_0 \sin \phi_0 \quad \dots (ii)$$




$$I_0 = \sqrt{I_w^2 + I_\mu^2} \quad \dots \text{(iii)}$$

$$\cos \phi_0 = \frac{I_w}{I_0} \quad \dots \text{(iv)}$$

$$\text{Also core loss} = V_1 I_0 \cos \phi_0 = V_1 I_w \quad \dots \text{(v)}$$

$$\text{Magnetizing (reactive) voltameters} = V_1 I_0 \sin \phi_0 = V_1 I_\mu \quad \dots \text{(vi)}$$

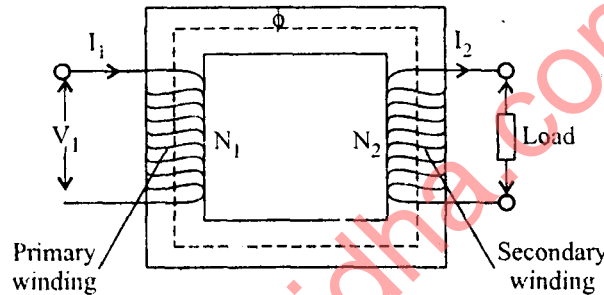**Transformer On Load :** When there is a load connected to secondary side of transformer, then transformer is said to be on load.



When the transformer is on load (i.e., an impedance or load is connected across the secondary terminals).

Current  $I_2$  flows through the secondary windings, the secondary current  $I_2$  set up its own mmf and hence creates a secondary flux  $\phi_2$ , the secondary flux  $\phi_2$  opposes the main flux  $\phi$  set up by the exciting current.  $I_0$  the opposing secondary flux  $\phi_2$  weakens the main flux  $\phi$  momentarily.

So primary back emf  $E_1$  tends to be reduced, so difference of applied voltage  $V_1$  &  $E_1$  increases.

Therefore, more current is drawn from the source of supply flowing through the primary winding until original value of flux  $\phi$  is obtained and it again causes increase in back emf  $E_1$ .

Let the additional primary current be  $I'_1$ .

The  $I'_1$  is in phase opposition with secondary current  $I_2$  and is called the counter balancing current.

The additional current  $I'_1$  set up an mmf  $N_1 I'_1$  producing flux  $\phi'_1$  in the same direction as that of the main flux  $\phi$  and cancels the flux  $\phi_2$  produced by secondary mmf  $N_2 I_2$ .

$$\text{So} \quad N_1 I'_1 = N_2 I_2 \quad \text{or} \quad I'_1 = \frac{N_2}{N_1} I_2 \quad \dots \text{(a)}$$

The total primary current  $I_1$  is therefore, phasor sum of primary counter balancing current  $I'_1$  and no load current  $I_0$ .

$$I_0 \text{ is very small so} \quad I_1 = I'_1$$

$$I_1 = I'_1 = N_2 / N_1 \cdot I_2 \quad \text{or} \quad \frac{I_1}{I_2} = \frac{N_2}{N_1} = K$$



Since the secondary flux  $\phi_2$  produced in secondary mmf  $N_2 I_2$  is neutralized by the flux  $\phi_1'$  produced by mmf  $N_1 I_1'$  set up counter balancing current  $I_1'$ . The flux in the transformer core remains constant from no load to full load.

Since the voltage drop in both of the winding of the transformer are assumed to be negligible.

Therefore,  $V_2 = E_2$  &  $V_1 = -E_1$

Resistive Load	Inductive Load	Capacitive Load
Current $I_2$ will be in phase with $V_2$ , the current $I_1'$ will be in phase with $V_1$ and equal to $I_2$ in magnitude. The current $I_1$ is made up of $I_0$ and $I_1'$ so lags behind $V_1$ by an angle $\phi_1$ .	The secondary current $I_2$ lags behind the secondary terminal voltage $V_2$ by an angle $\phi_2$ . The induced primary current $I_1'$ is always in opposition of $I_2$ .	The secondary current $I_2$ leads the secondary terminal voltage $V_2$ by an angle $\phi_2$ . The current $I_1$ is the vector sum of the current $I_0$ and $I_1'$ which will be lagging behind $V_1$ by an angle $\phi_1$ .

Phasor diagram for the ideal transformer on load


**Q. 8. (a) Explain the construction and working of synchronous motor.**

**Ans. Construction of Synchronous Motor :** It consist of following essential parts :


- A laminated stator core with three phase armature winding.
- Revolving field complete with amortisseur inding and slip rings.
- Brushes and brush holders.
- Two end shields to house the bearings that support the shaft.

The stator core and windings of a synchronous motor are similiar to those of 3-phase squirrel cage induction motor. The rotor is generally a salient pole rotor. In order to eliminate hunting and to develop the necessary starting torque when a.c. voltage is applied to stator, the rotor poles contain pole phase conductors which are short circuited at their ends as shown. The field circuit leads are brought out of two

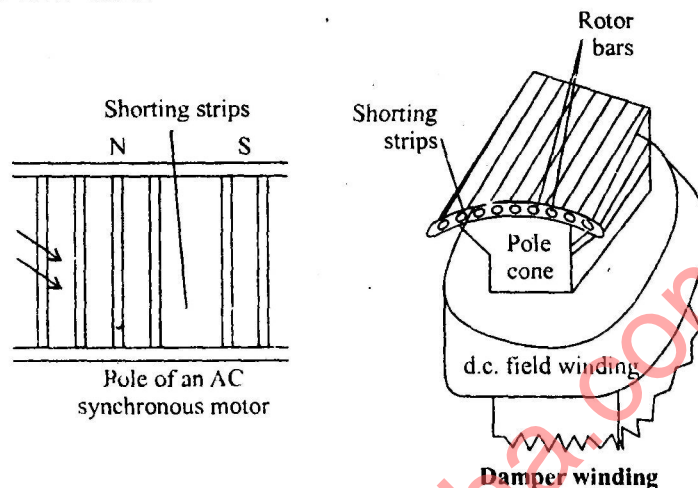slip rings mounted on the rotor shaft. Carbon brushes mounted in brush holders make contact with the two slip rings the terminal of the field circuit are brought out from the brush holders to a second terminal box mounted on the rotor frame.



**Principle of Operation :** Where the stator winding of a 3-phase synchronous motor are supplied with rated 3-phase. Voltage a rotating field travelling at synchronous field is set up. The synchronous speed is found from the relation  $N_s = \frac{120f}{P}$  where  $N_s$  (rpm),  $f$  and  $P$  are synchronous  $P$  speed, frequency and no. of poles respectively. This rotating magnetic field cuts across the squirrel cage winding of rotor and induces voltage and current in the bass of this winding. The resultant magnetic field of squirrel cage winding embedded in the rotor field poles reacts with the rotor field in such a manner as to cause the rotation of motor. The rotor will increase its speed to a point slightly below the synchronous speed of the stator field. The field circuit is now existed from an outside source of d.c. and magnetic poles of fixed polarity are set up in the rotor field cores. The fixed magnetic poles of the rotor are attracted to unlike poles of the rotating magnetic field set up by the stator winding.

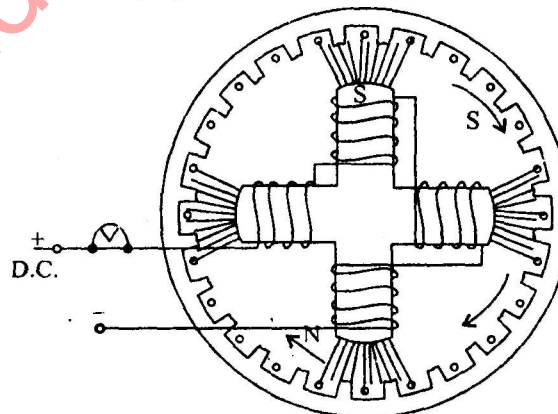

**Application :** Power houses and substations, factories, 18/13 industries, constant speed equipment (fans, blowers, centrifugal pumps, motor generator sets) etc.

**Q. 8. (b) Explain the working principle of D.C. machine and derive emf. equation for it.**

**Ans. Working Principle :** It is a machine which convert electrical power into mechanical power. It is used to operate pumps, lathe etc.

When a current carrying conductor is placed in a magnetic field then it experiences a mechanical force tending to rotate and the direction of the force experienced is given by the flowing left hand rule. The magnitude of this mechanical force ( $F$ ) is experienced by the conductor is given by

$$F = Bil \text{ newton}$$

$l$  = Length of conductor (in meter)

$i$  = Current in the conductor (in amp)


$B$  = Magnetic flux density (in  $\text{wb/m}^2$ )

(i) Suppose a conductor is placed in a magnetic field as shown and here magnetic field passes the airgap from N-pole to S-pole.

(ii) Now the figure, conductor carries the current but no magnetic effect of the main right hand, S thumb rule or work screw rule.

(iii) Again in figure, the current carrying conductor is placed in a magnetic field. Here magnetic field of conductor supports main field upon the conductor and opposes main field under the conductor in other words the flux density increased in one side and decrease in other side. Here a force is developed on the conductor for high density flux to low density flux.

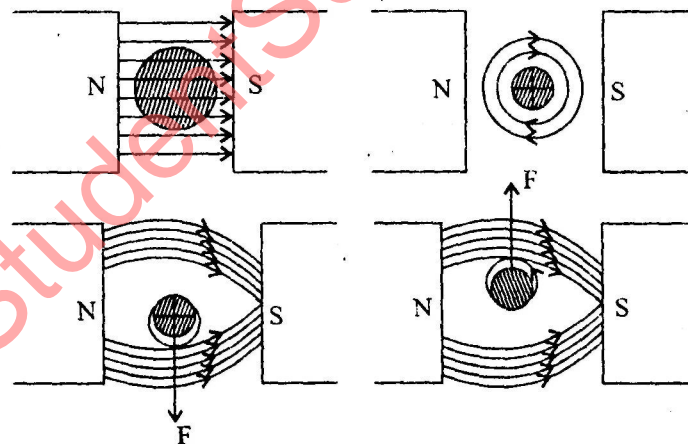(iv) If we change the direction of current in conductor, the direction of force is also changed as shown.



**E.M.F Equation :** Let in a d.c. machine

$P$  = No. of poles

$\phi$  = Flux generated per pole (in  $\text{wb/m}$ )

$Z$  = Total conductor in armature

$N$  = Speed of armature (r.p.m.)

$A$  = Parallel paths (in armature)

According to Faraday's law,

In one conductor

Induced average e.m.f.  $E = \frac{d\phi}{dt}$  volt

Flux cut in one revolution  $d\phi = \text{No. of poles} \times \text{Flux/pole}$   
 $= p \times \phi$

Time taken in one revolution  $dt = \frac{60}{N} \text{ sec.}$

Here induced average emf in one conductor

$$E = \frac{d\phi}{dt} = \frac{P\phi}{60/N} = \frac{P\phi N}{60} \text{ volt}$$

When conductor are  $Z$ , total induced e.m.f.

$$E = \frac{P\phi N}{60} \times Z \text{ volt}$$

But conductor in one parallel path  $= \frac{Z}{A}$

So induced e.m.f.  $E = \frac{\phi Z N P}{60 \times A} \text{ volt}$

$$A = \begin{cases} Z & \text{for wave winding} \\ P & \text{for loop winding} \end{cases}$$

**Q. 9. Write short notes on :**

**(a) Induction type voltmeter**



**(b) Energy meter**

**Ans. (a) Induction Type voltmeter :** Here the deflecting torque is produced due to the reaction between the flux of an a.c. magnet and the eddy currents induced by this flux.

**Principle of Operation :** It consist of thin aluminium disc  $D$  free to rotate about an axis passing through its centre. Two a.c. magnetic poles  $P_1$  &  $P_2$  produce alternating fluxes  $\phi_1$  &  $\phi_2$  respectively which cut this disc. Consider any annular portion of the disc around  $P_1$  with centre on the axis of  $P_1$  this portion will be linked by flux  $\phi_1$  and so on alternating emf  $e_1$  be induced in it. This emf will circulate an eddy current  $i_1$  which will pass under  $P_2$ . Similarly  $\phi_2$  will induced an emf  $e_2$  which will further induce an eddy current  $i_2$  in an annular portion of the disc around  $P_2$ .

This eddy current  $i_2$  flows under pole  $P_1$ .

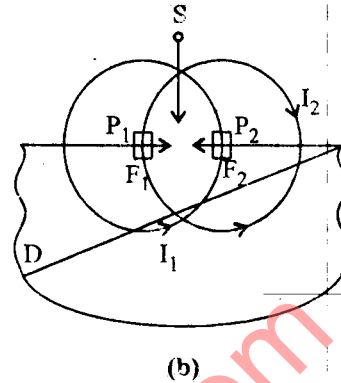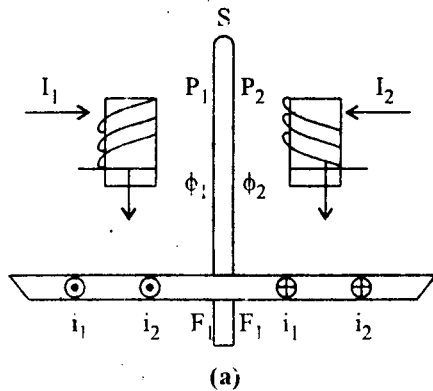The portion of the disc which is traversed by flux  $\phi_1$  and carries eddy current  $i_2$  experience a force  $F_1$  along the direction as indicated. As  $F = Bil$ , force  $F_1 \propto \phi_1 i_2$ . Similarly the portion of the disc are leging in flux  $\phi_2$  and carrying eddy current  $i_1$  experiences a force  $F_2 \propto \phi_2 i_1$  or  $F_2 = K\phi_2 i_1$



$$F_1 \propto \phi_1 i_2 = K \phi_1 i_2$$

Let  $R$  be the effective radius at which these force act. The torque  $T$  acting on the disc being equal to the difference of the two torque. A given by

$$\begin{aligned} T &= R(K\phi_1 i_2 - K\phi_2 i_1) \\ &= K_1 (\phi_1 i_2 - \phi_2 i_1) \quad K_1 = RK \end{aligned}$$

The value of eddy current

$$i_1 = \frac{e_1}{R} = \left( \frac{d\phi_1}{dt} \right) / R$$

$$i_1 = \frac{d(\phi_{1m} \sin \omega t)}{dt} / R$$

$$i_1 = \frac{\omega \phi_{1m} \cos \omega t}{R}$$

Similarly

$$i_2 = \frac{\omega \phi_{2m} (\cos \omega t - \alpha)}{R}$$

Where,  $\phi_1 = \phi_m \sin \omega t$

$$\phi_2 = \phi_{2m} \sin(\omega t - \alpha)$$

After putting the value of  $i_1$  &  $i_2$  in equation (i), we have

$$T = \frac{K_1 \omega}{R} \phi_{1m} \phi_{2m} \sin \alpha$$

From above it is clear that : (i) If  $\alpha = 0$  if two fluxes are in plane the net torque is zero.

(ii) If  $\sin \alpha = 1$ ,  $\alpha = 90^\circ$  the net torque is max. for given values of  $\phi_{1m}$  &  $\phi_{2m}$ .


(iii) The net torque is in such a direction so as to rotate the disc from the pole with leading flux towards the pole with lagging flux.

(iv) The value of  $T$  does not depend upon  $t$ . So we can say that it has a steady value at all times

**(b) Energy Meter :** An instrument which measures electrical energy is called an energy meter or wathours (wh) meter. Since the electrical energy consumed by a load adds up as the time goes on, an energy meter is an integrating meter. There are several types of energy meters. Single phase induction type energy meters are very commonly used to measure electrical energy consumed in domestic, commercial, and industrial installation.

**Construction :** A single phase induction type energy meter consists of the following parts :

- (i) Driving system
- (ii) Moving system
- (iii) Braking system
- (iv) Registering system

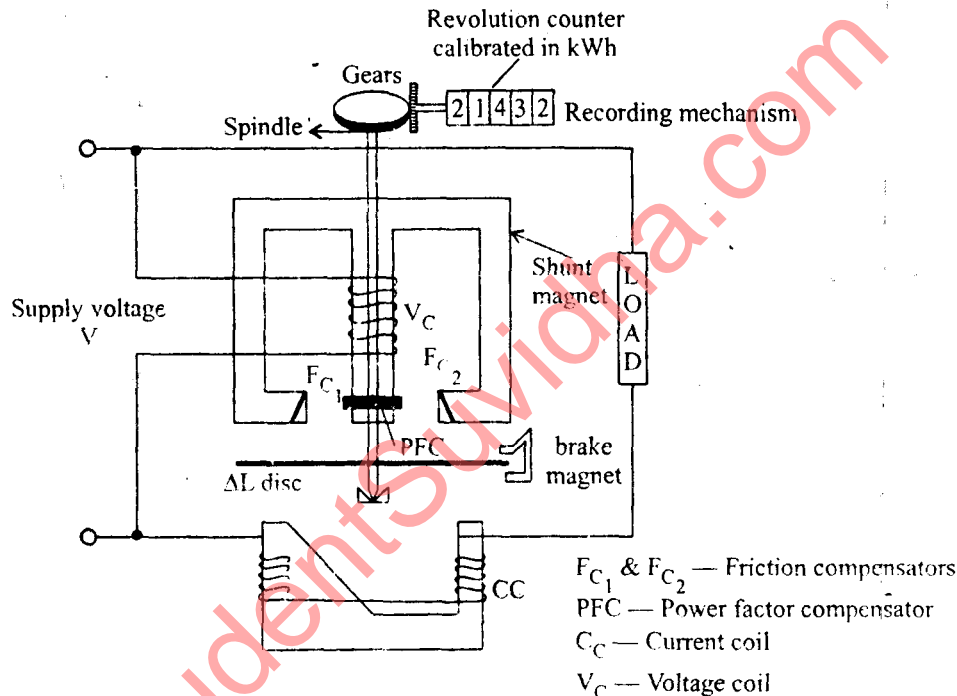

**Fig. Single phase energy meter**

**(i) Driving System :** The driving system of the energy meter consists of two silicon steel laminated electromagnets  $M_1$  &  $M_2$ . The magnet  $M_1$  is called the series magnet and the magnet  $M_2$  is called the shunt magnet. The series magnet  $M_1$  carries a coil consisting of few turns of thick wire and carries the load current. This coil is called the current coil (CC) and is connected in series with the circuit. The shunt magnet  $M_2$  carries a coil consisting of many turns of thin wire.

This coil is called the voltage coil (VC) and is connected across the supply. The voltage coil carries a current proportional to the supply voltage.

Short-circuited (copper shading bands) are provided on the lower part of the central limb of the shunt magnet. These bands are also called power factor compensators.

**(ii) Moving System :** The moving system consists of a thin aluminium disc (rotor) mounted on a spindle. The disc is placed in the air gap between the series and shunt magnets so that it acts the fluxes of both the magnets.

(iii) **Braking System** : The braking system consists of a permanent magnet known as brake magnet. It is placed near the edge of the aluminium disc. When the disc rotates in the field of the brake magnet, eddy currents are induced in it. These eddy currents react with the flux and exert a braking or retarding torque.

(iv) **Registering System** : The disc spindle is connected, through a set of gears to a counting mechanism. This mechanism records a number which is proportional to the number of revolutions of the disc and indicates the energy consumed directly in kilowattheours (kWh).

**Theory** : When the energy meter is connected in the circuit, the current coil carries a current equal to the load current  $I$  and the voltage coil carries a current proportional to the supply voltage.

Let,  $V$  = Supply voltage

$I$  = Load current lagging behind  $V$  by  $\phi$

$\therefore \cos \phi$  = Load power factor

$I_{sh}$  = Current through the shunt coil VC

$I_{sc}$  = Current through the series coils CC.

The flux  $\phi_{sh}$  of the shunt coil (VC) is made to lag behind  $V$  by  $90^\circ$  with the adjustment of copper shading bands. The flux  $\phi_{sc}$  of the series coil (CC) is taken to be in phase with current  $I$ . Let  $e_{sh}$  and  $e_{sc}$  be the induced emfs in the disc due to fluxes  $\phi_{sh}$  and  $\phi_{sc}$ . The emfs  $\phi_{sh}$  lags behind  $\phi_{sh}$  by  $90^\circ$  and  $e_{sc}$  lags behind  $\phi_{sc}$  by  $90^\circ$ . Eddy currents  $i_{sh}$  and  $i_{se}$  are set up in the disc by  $e_{sh}$  and  $e_{sc}$  respectively. Since the inductance of the eddy current path in the disc is negligible,  $i_{sh}$  is in phase with  $e_{sh}$  and  $i_{sh}$  is in phase with  $e_{sc}$ . The phasor diagram is shown below.

The instantaneous torque acting upon the disc will be due to the two oppositely directed torques proportional to  $\phi_{sh} i_{se}$  and  $\phi_{sc} i_{sh}$ .

$\tau_{inst} \propto \phi_{sh} i_{se} - \phi_{sc} i_{sh}$  : Let supply voltage be,

$$v = V_m \sin \omega t$$

Then the load current is  $i = I_m \sin(\omega t - \phi)$

The fluxes are  $\phi_{sc} = K_1 I_m \sin(\omega t - \phi)$

Where,  $K_1$  = Constant


$$\phi_{sh} = K_2 \int v dt$$

Where,  $v = \frac{1}{K_2} \frac{d\phi_{sh}}{dt}$ , being in phase opposition to the induced voltage

$$\phi_{sh} = -K_2 \frac{V_m}{\omega} \cos \omega t$$

Where,  $K_2$  is another constant.

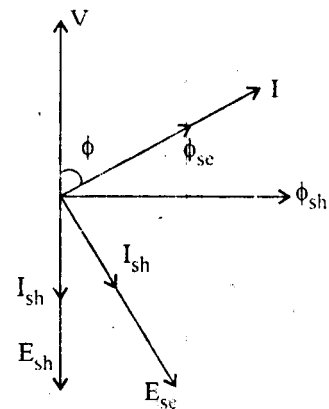The eddy emf induced by the flux  $\phi_{sc}$  is





$$e_{se} = \frac{-d\phi_{se}}{dt} = -K_1 I_m \omega \cos(\omega t - \phi)$$

If the eddy current path is assumed to be purely resistance of value  $R$ .

$$i_{se} = \frac{e_{se}}{R} = \frac{-K_1 I_m \omega}{R} \cos(\omega t - \phi)$$

$$e_{sh} = \frac{-d\phi_{sh}}{dt} = -K_2 V_m \sin \omega t$$

$$i_{sh} = \frac{e_{sh}}{R} = \frac{-K_2 V_m}{R} \sin \omega t$$

The instantaneous torque in the disc is then

$$\begin{aligned} T_{inst.} &\propto \phi_{sh} i_{se} - \phi_{se} i_{sh} \\ &\propto \frac{K_2 V_m}{\omega} \cdot \frac{K_1 I_m \omega}{R} \cos \omega t \cdot \cos(\omega t - \phi) + \frac{K_1 I_m K_2 V_m}{R} \sin(\omega t - \phi) \sin \omega t \\ &\propto \frac{K_1 K_2}{R} V_m I_m [\cos \omega t \cos(\omega t - \phi) + \sin \omega t \sin(\omega t - \phi)] \\ &\propto \frac{K_1 K_2}{R} V_m I_m [\cos \omega t - \omega t - \phi] \\ &\propto \frac{K_1 K_2}{R} V_m I_m \cos \phi \end{aligned}$$

The average deflecting torque upon the disc is

$$T_d \propto VI \cos \phi$$

Thus, the average deflecting torque on the disc is proportional to the active power in the circuit.

Neglecting friction in the meter, and assuming that the shunt magnet flux lags behind the supply voltage by exactly  $90^\circ$ , the driving torque is proportional to the power consumed in the circuit, that is,

$$T_d \propto P, \quad T_d = K_3 P$$

The braking torque is due to eddy currents induced in the disc. Since the magnitude of eddy currents is proportional to the disc speed.

$$T_b \propto N, \quad T_d = K_4 N$$

The disc will prove with steady speed when

$$\boxed{T_b = T_d}$$