

1987

B.E./B.Tech. 1st Semester Examination,

December-2013


ELECTRICAL TECHNOLOGY

Paper-EE-101-E

Time allowed : 3 hours] [Maximum marks : 100

Note : Attempt any five questions out of eight.

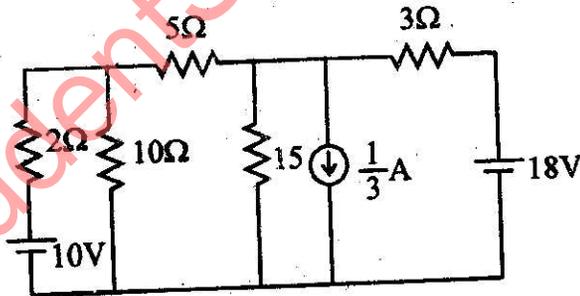
1. (a) Define Ohm's law and also explain its limitations. 10
- (b) Find current through 2Ω and 3Ω resistances using nodal analysis in the following Ckt. 10



2. (a) Explain and prove Tellegen's theorem. 10
- (b) Explain star to Delta and Delta to star conversion. 10
3. (a) Define RMS voltage and average voltage. 10

Download All Btech Stuff From StudentSuvudha.com

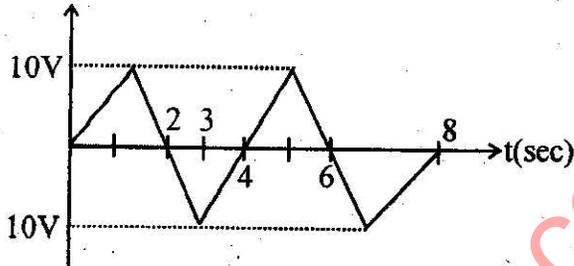- (b) Determine the form factor of voltage waveform. 10



4. (a) Define apparent power, True power, Power factor and imaginary power. 10
- (b) Discuss the concept of impedance triangle and power triangle. 10
5. (a) Explain Transient response of R-L Ckt. 10
- (b) Explain Series resonance in detail. 10
6. (a) Explain different losses that exist in transformer. 10
- (b) Compare shell type and core type transformers. 10
7. (a) Explain two wattmeter method for the measurement of three phase power. 10
- (b) Compare single phase and three phase systems. 10
8. (a) Explain working principle of D.C machine. 10
- (b) Explain construction and principle of energy meter. 10