

Roll No.

2013

**B. E. 3rd Semester (I.T.)
Examination – December, 2009**

DIGITAL ELECTRONICS

Paper : EE-204-E

Time : Three hours]

[Maximum Marks : 100

Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt any five questions. All questions carry equal marks.

1. (a) Implement Boolean expression for EX-OR gate using NAND gates. 10
- (b) Determine the single error correcting code for the BCD number 1001 using even parity. 10
2. (a) Simplify and design the given Boolean function using K-map

$$y = \sum m (0, 4, 8, 12, 16, 18, 20, 22) + \sum d (24, 26, 28, 30, 31)$$

10

2013-12,600-(P-3)(Q-8)(09)

P. T. O.

- (b) Simplify the following Boolean function by using tabulation method.

$$F(A, B, C, D) = \sum m(0, 2, 3, 6, 7, 8, 10, 12, 13) \quad 10$$

3. (a) Implement the following Boolean function with 8 : 1 multiplexer.

$$F(A, B, C, D) = \pi m(0, 3, 5, 6, 8, 9, 10, 12, 14) \quad 10$$

- (b) Design a full adder using 8 : 1 multiplexer Ic's. 10

4. (a) Convert the given D flip-flop to T flip-flop. 10

- (b) Design MOD4 counter using JK flip-flops and implement it. 10

5. (a) Draw a TTL circuit with totem pole output and explain its working. Why should it not be used for wired AND connection ? 10

- (b) Explain the working of ECL logic with suitable diagram. 10

6. (a) What are the specification of A/D converters ? Also explain the working of Dual-slope A/D converter with diagram. 10

- (b) Explain sample and hold circuit with suitable diagram. 10

