

Roll No.

24143

**B. Tech. 4th Sem. (E.E/E.E.E/E.C.E./E.I.E./
I.C.E.) (Common to all these Branches)**

Examination – May, 2011

DIGITAL ELECTRONICS

Paper EE-204-F

Time : Three hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination

Note : Attempt five questions. Q. No. 1 is compulsory and one questions from each of four Section.

1. (a) Realize the following using Nand Gate :

- (i) AND gate,
- (ii) EX-OR gate,

(b) Simply :

- (i) $F = \overline{A} (\overline{B} + \overline{C}) + BC + A\overline{C}$
- (ii) $F = \overline{A(B+C)} + \overline{AB} + \overline{C(A+B)}$

(c) Give truth table for :

- (i) S-R Flip-Flop,
- (ii) J-K Flip Flop.

(d) Differentiate between :

(i) Latch and Flip-Flop,

(ii) Ripple counter and Synchronous counter.

5 × 4

SECTION – A

2. (a) (i) Multiply 4.75_2 by 3.625_2 .

(ii) Divide 50_{10} by 5_2 .

(iii) Convert 2004_{10} to octal

(iv) Convert 7325_8 to binary.

(v) Add $+112_{10}$ and $+65_{10}$ using 2s complement arithmetic. 10

(b) Use K-map to simplify :

(i) $F = \overline{A}B\overline{C} + A\overline{C}D + BC + \overline{A}B\overline{D} + A\overline{B}CD$

(iii) $F = (AC + A\overline{C}D)(AD + AC + BC)$

3. (a) Write short notes on :

(i) Error detecting and correcting codes,

(ii) Excess-3 code and gray code. 10

(b) Give simplified large equation of Table 1 by Quine-McClusky Method. 10

Table 1

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

SECTION – B


4. (a) Show how 1,6 to 1 multiplexes can be obtained using 4 to 1 multiplexes 10
- (b) Draw and explain :
- (i) Block diagram,
 - (ii) Truth Table,
 - (iii) Circuit for 1-bit comparator. 10
5. (a) Give truth table, Boolean equation and circuit diagram for :
- (i) Full Adder,
 - (ii) Substrater.
- (b) What is a demultiplexer. Explain with help of suitable block diagram and logic circuit of 1 to 16 demultiplexer. 10

SECTION – C

6. Design : 20
- (i) MOD-8 ripple counter
 - (ii) Decode synchronous counter using J-K Flip-Flops.
7. (a) What is a shift register. Draw circuit diagram for :
- (i) Serial in/parallel out
 - (ii) Parallel in / serial out shift registers using J-K Flip-Flops. 15
- (b) Convert J-K Flip-Flop into D Flip-Flop. 5

SECTION – D

 8. (a) Design an asynchronous sequential logic circuit for state transition diagram shown in Figure : 10



- (b) Implement a full adder using PLA. 10
9. Write short notes on : 10, 10
- (i) RAM and ROM.
 - (ii) Algorithm State Machine (ASM).