

Roll No.

24043

**B. Tech. 3rd Sem.
(Information Technology)
Examination – December, 2012**

DIGITAL ELECTRONICS

Paper : EE-204-F

Time : Three Hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions. Question No. 1 is *compulsory* and *one* question from each of four Sections.

1. (a) Draw and give truth table of :

(i) Ex-OR gate

(ii) Nor gate

(b) Draw and explain 4 : 1 multiplexer

24043-7,450-(P-4)(Q-9)(12)

P. T. O.

(c) Give truth table of :

(i) S-R Flip Flop

(ii) J-K Flip Flop

(d) Differentiate between ASLC and SSLC. 5×4

SECTION – A

2. (a) Simplify the logic function using Quin Mc-Clusby method : 15

$$f(A, B, C, D) = \sum_m(1, 3, 7, 11, 15) + d(0, 2, 5).$$

(b) Simplify : $\overline{A}B + B\overline{C} + BC + A\overline{B}\overline{C}$ 5

3. (a) 7-bit Hamming code is received as 1101101. Locate the error position and find the correct code. 5

(b) Write in brief about cyclic code. 5

(c) Use K-map to simplify : 10

(i) $F = \sum_m(1, 2, 3, 4, 9, 11, 12, 13, 15)$

(ii) $F = \pi(3, 4, 6, 7, 11, 12, 13, 14, 15)$

SECTION – B

4. (a) Draw and explain BCD adder using IC 7483. 10

- (b) Give truth table, Boolean equation and circuit for full subtractor. 10

5. (a) Design a 16 : 1 multiplexer using 8 : 1 multiplexer. 10

- (b) Draw block diagram, truth table and circuit for 1-bit comparator. 10

SECTION – C

6. (a) Design a 3 bit synchronous counter using J-K flip flop. 15

- (b) Differentiate between synchronous and asynchronous counter. 5

7. (a) What is a shift register ? Draw circuit diagram for : 15


(i) Serial in parallel out

(ii) Parallel in serial out shift registers using J-K Flip-Flop.

- (b) Convert J-K Flip-Flop into S-R Flip-Flop. 5

SECTION – D

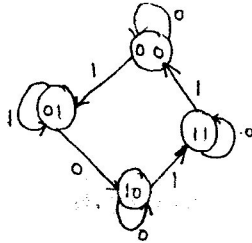8. (a) For state diagram shown in figure, obtain the state table and design the circuit using minimum no. of J-K Flip-Flop. 15



- (b) Define primitive flow table and non-primitive flow table. 5

9. Write short notes on the following : 2 × 10

- (i) Hazards,
- (ii) PLA and PAL.