

2013

B.Tech. 3rd Semester (I.T.) Examination,

December-2013

DIGITALELECTRONICS

Paper-EE-204-E

*Time allowed : 3 hours ]*

*[ Maximum marks : 100*

*Note : (i) Attempt any five questions.*

*(ii) Use of non-programmable calculator is allowed.*

1. Explain the following : 20
  - (a) Universal Gates
  - (b) Error detecting codes
  - (c) Latches
  - (d) Registers
  - (e) Digital Multivibrators
  
2. (a) Simplify the function using tabular method : 10  
 $F(A, B, C, D) = 1, 5, 6, 7, 8, 9, 11, 12, 13, 15.$   
  
(b) Write the Hamming code for the following BCD Code (11001) for odd parity. 10
  
3. (a) What are binary address ? Explain with diagram & Truth Table. 10

- (b) Explain the following :
- (i) Decoder
  - (ii) Demultiplexers. 10
4. (a) Explain the parallel in parallel out shift registers. Also explain the applications. 10
- (b) Explain Ring Counter with Four flip flops. 10
5. (a) What are Flip Flops ? Differentiate between Flip Flops & Latches. 10
- (b) Explain the working of JK Flip Flop with neat and clean diagram and truth table. 10
6. Simplify the given function using k-map method :
- $F(A, B, C, D) = (0, 1, 2, 5, 6, 8, 9, 11, 13, 14)$  using minterms values only. 20
7. (a) What is the difference between synchronous and asynchronous circuits ? 10
- (b) Explain the working of JOHNSON counter with diagram and truth table. 10
8. Explain the following :
- (a) PAL
  - (b) FPGA
  - (c) ROM 20