

B.E./B.Tech. 4th Semester (AEIE) E-Scheme

Examination, May-2014

DIGITAL ELECTRONICS

Paper-EE-204-E

Time allowed : 3 hours] [Maximum marks : 100*Note : Attempt any five questions. All questions carry equal marks.*

1. (a) Convert the following :

(i) $(1101.01101)_2 = (?)_{16}$

(ii) $(3FA7)_{16} = (?)_8$

(iii) $(32.43)_{10} = (?)_8$

(iv) $(100.11)_2 = (?)_{10}$

(iv) $(8435)_{10} = (?)_{16}$ 10

(b) Prove the following :

(i) $AB + ABC + ABCD + ABCDE + ABCDEF = AB$

(ii) $(A + \bar{B} + \bar{C})(A + \bar{B}C) = A + \bar{B}C$ 10

2. (a) Describe the following :

(i) BCD Code

(ii) Excess - 3 Code

(iii) ASCII Code 10

2104-P-3-Q-8 (14)

[P.T.O.]

(b) Simplify the following functions

(i) $Y = \pi(0, 1, 2, 3, 6, 8, 11, 12, 13, 15)$

(ii) $Y = \pi M(0, 1, 2, 3, 5, 7, 14) + d(6, 9, 11, 12, 13, 15)$ 10

3. (a) Simplify the Boolean function using Quine Mc Cluskey method.

$f(A, B, C, D) = \Sigma m(1, 2, 3, 6, 9, 12, 14, 15)$ 10

(b) Reduce the given equation into POS form and implement using NOR gates

$Y(A, B, C, D, E) = \pi M(2, 3, 5, 7, 11, 13, 15, 19, 21, 24, 25, 30, 31).$ 10

4. (a) Design a 32:1 multiplexer using 8:1 multiplexer. 10

(b) Design a binary to Gray code converter. 10

5. (a) Convert the following :

(i) S-R to T Flip Flop

(ii) J-K to T Flip-Flop. 10

(b) Design MOD - 10 counter using J-K Flip Flop.

10

(b) Simplify the following functions

(i) $Y = \pi(0, 1, 2, 3, 6, 8, 11, 12, 13, 15)$

(ii) $Y = \pi M(0, 1, 2, 3, 5, 7, 14) + d(6, 9, 11, 12, 13, 15)$ 10

3. (a) Simplify the Boolean function using Quine Mc Cluskey method.

$f(A, B, C, D) = \Sigma m(1, 2, 3, 6, 9, 12, 14, 15)$ 10

(b) Reduce the given equation into POS form and implement using NOR gates

$Y(A, B, C, D, E) = \pi M(2, 3, 5, 7, 11, 13, 15, 19, 21, 24, 25, 30, 31)$ 10

4. (a) Design a 32:1 multiplexer using 8:1 multiplexer.

10

(b) Design a binary to Gray code converter. 10

5. (a) Convert the following :

(i) S-R to T Flip Flop

(ii) J-K to T Flip-Flop. 10

(b) Design MOD - 10 counter using J-K Flip Flop.

10

6. (a) Discuss the following TTL output circuit configurations.
- (i) Totem-pole output
 - (ii) Open collector output 10
- (b) Explain the working of dual slope ADC. 10
7. (a) Explain the working of R-2R D/A converter. 10
- (b) Write short notes on :
- (i) Sample and Hold circuit
 - (ii) Resolution
 - (iii) Accuracy 10
8. (a) Compare FPGA with CPLD. 8
- (b) Design the circuit of Half adder using PAL and PLA. 12