

BT-3/D-12

8306

ANALOG COMMUNICATION**Paper—ECE-203E**

Time Allowed : 3 Hours]

[Maximum Marks : 100

Note : Attempt **five** questions in all, selecting at least **one** question from each Unit. All questions carry equal marks.

UNIT-I

1. (a) Determine expression for noise figure of cascaded amplifier and write final expression for multistage amplifier. 10
- (b) Find overall noise figure of a three stage cascaded amplifier, each stage having a power gain of 20 dB and noise figure of 12 dB. 5
- (c) Give classification of external noise. 5
2. (a) Two resistors R_1 and R_2 at absolute temperature T_1 and T_2 are connected in series to form a white noise source. Find the equivalent noise temperature T_{eq} . 10
- (b) Explain noise temperature in detail. 10

UNIT-II

3. (a) Explain, how collector modulation method is used for AM generation. 10
- (b) Explain various methods used for generating SSB-SC signal. 10
4. (a) Explain synchronous detection method for demodulating a DSB-SC signal. 10
- (b) Explain diode detector demodulation technique for AM system. 10

UNIT-III

5. (a) Define modulation index for a FM system and show how it effects the spectrum of FM signal. 10
- (b) Explain Varactor diode method for FM generation. 10
6. (a) Explain preemphasis and deemphasis in a FM system using proper diagram. Also derive expression for SNR improvement using preemphasis. 10
- (b) Explain slope detector method for FM demodulation. 10

UNIT-IV

7. (a) Write note on Armstrong FM transmitter. 10
- (b) Explain in detail sensitivity and selectivity of AM receivers. 10
8. (a) Write note on superheterodyne receiver. 10
- (b) What is image frequency problem related with superheterodyne receiver and how it can be removed? Elaborate. 10