

**GUJARAT TECHNOLOGICAL UNIVERSITY**

B.E. Sem-III Examination December 2009

Subject code: 130701

Subject Name: Digital Logic Design

Date: 21 /12 /2009

Time: 11.00 am – 1.30 pm

Total Marks: 70

**Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) Convert the following numbers to decimal 07  
 (i)  $(10001.101)_2$  (ii)  $(101011.11101)_2$  (iii)  $(0.365)_8$   
 (iv) A3E5 (v) CDA4 (vi)  $(11101.001)_2$  (vii) B2D4
- (b) Perform the operation of subtractions with the following binary numbers using 2' complement 07  
 (i)  $10010 - 10011$  (ii)  $100 - 110000$  (iii)  $11010 - 10000$
- Q.2** (a) Obtain the simplified expressions in sum of products for the following Boolean functions: 07  
 (i)  $F(A,B,C,D,E) = \sum(0,1,4,5,16,17,21,25,29)$   
 (ii)  $A'B'CE' + A'B'CD' + B'D'E' + B'CD'$
- (b) Demonstrate by means of truth tables the validity of the following Theorems of Boolean algebra 07  
 (i) De Morgan's theorems for three variables  
 (ii) The Distributive law of + over-
- OR**
- (b) Implement the following Boolean functions 07  
 (i)  $F = A(B + CD) + BC'$  with NOR gates  
 (ii)  $F = (A + B')(CD + E)$  with NAND gates
- Q.3** (a) Design a combinational circuit that accepts a three bit binary number and generates an output binary number equal to the square of the input number. 07
- (b) Discuss 4-bit magnitude comparator in detail 07
- OR**
- Q.3** (a) With necessary sketch explain full adder in detail 07
- (b) Design a combinational circuit that generates the 9' complement of a BCD digit, 07
- Q.4** (a) Discuss D-type edge- triggered flip-flop in detail 07
- (b) Design a counter with the following binary sequence: 0,4,2,1,6 and repeat (Use JK flip-flop) 07
- OR**
- Q.4** (a) Design a counter with the following binary sequence: 0,1,3,7,6,4, and repeat. (Use T flip-flop) 07
- (b) (i) With neat sketch explain the operation of clocked RS flip 05  
 (ii) Show the logic diagram of clocked D 02
- Q.5** (a) With necessary sketch explain Bidirectional Shift Register with parallel load. 07
- (b) Draw the state diagram of BCD ripple counter, develop its logic diagram, and explain its operation. 07
- OR**
- Q.5** (a) Construct a Johnson counter with Ten timing signals. 07
- (b) Discuss Interregister Transfer in detail 07

\*\*\*\*\*