

GUJARAT TECHNOLOGICAL UNIVERSITY
B. E. - SEMESTER –I • EXAMINATION – WINTER 2012

Subject code: 110005**Date: 24-01-2013****Subject Name: Elements of Electrical Engineering****Time: 10.30 am – 01.00 pm****Total Marks: 70****Instructions:**

1. Attempt any five questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

- Q.1** (a) What is the temperature co-efficient of resistance? Derive equation of resistance at different temperature. Explain the effect of temperature on resistivity on different type of material. **07**
- (b) Derive the equation of Star to Delta and Delta to Star transformation. **07**
- Q.2** (a) Derive the equation of capacitance of parallel plate capacitor with uniform dielectric medium and with composite dielectric medium. **07**
- (b) A parallel plate capacitor has a plate area of 4 cm^2 . The plates are separated by three slabs of different dielectric materials of thickness 0.3 mm, 0.4 mm and 0.3 mm with relative permittivities of 3, 2.5 and 2 respectively. Calculate the capacitance of each material and the voltage across them if the supply voltage is 100 volt. ($\epsilon_0 = 8.854 \times 10^{-12}$) **07**
- Q.3** (a) Give the similarities and dissimilarities between Electrical circuit and magnetic circuit. **07**
- (b) Two coils X and Y are placed close to each other. Coil X has 1000 turns and carries a current 5Amp. The flux produced in this coil is 0.07 mWb. The same 5 Amp. current flows through coil Y having 1300 turns and produces a flux of 1 mWb in it. If 70% of the flux produced by coil X links with coil Y, find
- (a) Self inductances of both coils. **07**
 - (b) Mutual inductance between two coils.
 - (c) Co-efficient of coupling.
- Q.4** (a) Derive the equation of decay of current in inductive circuit with small resistance R connected in series with inductor. **07**
- (b) Define the following term: (1) RMS value (2) Average value (3) Form factor (4) Peak factor regarding a.c. quantity. **04**
- (c) Explain the addition of two vectors by a parallelogram method and by resolution method. **03**
- Q.5** (a) Draw the phasor diagram in R-L circuit. Draw impedance triangle and power triangle. **07**
- (b) Explain series R-L-C circuit with the phasor diagram for $X_L > X_C$; $X_L < X_C$ & $X_L = X_C$. **07**
- Q.6** (a) Derive the voltage and current relationship in delta and star connected load. **07**
- (b) How can we measure the power with the help of two watt meter method in three phase system with star connected load? **07**
- Q.7** (a) What is the need of earthing? Explain the different method of earthing. **07**
- (b) What is the construction of three core cable? Explain each parts and its importance. **07**
