

24007

B. Tech Common for all branches 2nd Semester

F. Scheme Examination,

May-2015

ELECTRICAL TECHNOLOGY

Paper-EE-101-F

Time allowed : 3 hours]


[Maximum marks : 100

Note : Attempt any five questions.


1. (a) State Ohm's Law and Kirchoff's law. 5
- (b) State the differences between series and parallel Resonance 5
- (c) Describe the relationship between phase and line voltages and currents in star connection with neat and clean phasor diagrams and equations. 5
- (d) Define moving iron type Instruments. 5

Section-A

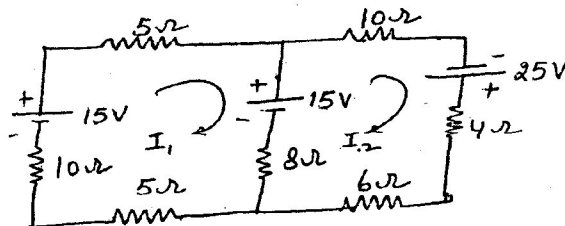2. (a) Solve the network shown below using Loop-current method and find the current in each branch. 10



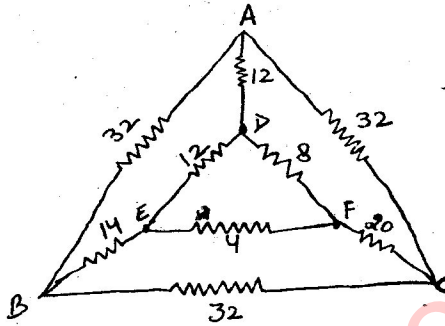
- (b) In the network shown, determine the resistance between A and B. 10



3. (a) Describe superposition and maximum power transfer theorem. 10
- (b) Give the proof of Star to Delta and Delta to Star transformation. 10

Section-B

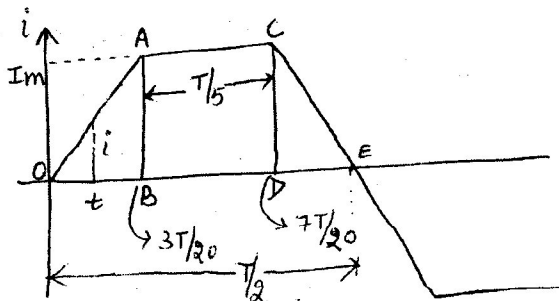4. (a) For the trapezoidal current waveform given below, determine the RMS value of current. 10



(b) The circuits A and B are connected in parallel to a 230 V, 50 Hz supply circuit A consists of resistance 20 ohms in series with an inductive reactance of 20 ohms and circuit B consists of resistance 40 ohms in series with a capacitive reactance of 20 ohms. Determine the

- (i) current drawn by each circuit
- (ii) total current drawn from the mains

Solve this by using phasor method. 10

5. Describe the condition of series resonance in detail. 20

Section-C

6. Describe Two-wattmeter method for power measurement using balanced-load. 20

7. Describe neatly the phasor diagrams of a loaded transformer for resistive, inductive as well as capacitive loads. 20

Section-D

8. (a) Describe constructional features of DC machines. 10
- (b) Describe advantages of Rotating field system over stationary field system. 10
9. Describe the working principles of wattmeter and energy-meter in detail. 20