

END TERM EXAMINATION

SECOND SEMESTER [BCA] MAY-JUNE-2013

Paper Code: BCA106

Subject: Digital Electronics (New)

Time : 3 Hours

Maximum Marks :75

Note: Attempt any five questions including Q.no.1 which is compulsory. Select one question from each unit.

- Q1. (a) Design a Full Adder circuit using only NAND gates only. (5)
- (b) State and explain the DeMorgan's theorem which converts a sum into a product form and vice versa. (5)
- (c) What is Multiplexer? Explain the difference between MUX and DEMUX. (5)
- (d) Explain Binary Multiplier. (5)
- (e) Simplify the following function in Sum of product form using four variable Karnaugh's map. Draw the resulting logic diagram. (5)

$$F(A,B,C,D) = \Sigma (0,1,2,4,5,7,11,15)$$

Unit-I

- Q2. (a) (i) Simplify the Expression $AB + \overline{AC} + \overline{ABC}$ (AB+c) (3)
- (ii) Simplify the given Boolean Expression (3)
- $$Y = \overline{A} \overline{B} \overline{C} + \overline{A} B \overline{C} + A \overline{B} \overline{C} + A B \overline{C}$$
- (b) Explain what is meant by logic family. Describe three major difference between RTL and DTL. (6.5)

- Q3. (a) Explain how the basic gates can be realized using NAND gates. Draw the useful Diagram. (6.5)
- (b) Implement $Y = \overline{AB} + A + \overline{B} + C$ using NAND gates only. (6)

Unit - II

- Q4. (a) Draw a Multiplexer using only NAND gates which selects from four inputs A0 to A3 using two select inputs S0 and S1. (6.5)
- (b) Implement the following function using a Multiplexer

P.T.O.

$$F(A,B,C) = \Sigma(1,2,5,6) \quad (6)$$

- Q5. (a) How does an encoder differ from decoder? Design 3 X 8 decoder. (6.5)
- (b) Design a 4 bit parallel binary adder. (6)

Unit- III

- Q6. (a) Explain in detail the construction and working universal / Bidirectional shift register. (6)
- (b) Explain the operation of Master – slave Flip Flop and show how the race around condition is eliminated in it? (6.5)
- Q7. (a) Explain the function of a D flip flop using a suitable diagram and discuss how it works as a latch? (6)
- (b) How an SR flip flop can be converted into JK flip flop? Give the truth table of JK flip flop Flop. (6.5)

Unit-IV

- Q8. (a) Design a MOD 7 binary counter. Draw its state diagram and circuit. (6)
- (b) What is a modulus counter? Draw the logic diagram of a 4 bit binary ripple counter using flip-flops that trigger on the positive edge transition. (6.5)
- Q.9. (a) What is ROM? Explain the terms volatile memory and non-volatile memory. (6)
- (b) What is a ripple counter? Explain the difference the performance of asynchronous and synchronous counter. (6.5)

* * * * *