

(b) What are Einstein's coefficients ? Derive the relation between them. 4

9. (a) Derive an expression for optical pumping power in lasers. 4

(b) Discuss in brief the principle of He-Ne laser with the help of energy level diagram. 4

Roll No. ....

**91540**

**B. Sc. 2nd Sem. (Chemistry) (Hons.) (New Scheme) Examination – May, 2016**

**PHYSICS - II**

**(Optional)**

*Time : Three Hours ]*

*[ Maximum Marks : 40*

*Before answering the question, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

*Note : Attempt five questions in all selecting at least one question from each Section. Question No. 1 is compulsory.*

1. (a) What is the effect of temperature on the conductivity of a semiconductor ?
- (b) Explain valence and conduction band.
- (c) Do the semiconductor obey Ohm's law as in conductors.
- (d) What is a C.R.O. ?

91540- (P-4)(Q-9)(16) ( 4 )

91540-344-(P-4)(Q-9)(16)

P. T. O.

- (e) What is d. c. load line ?
- (f) What is thermal run of a transistor ?
- (g) Calculate the unit of energy density ?
- (h) Is resonance condition essential for laser action ?

### SECTION - I

2. (a) Explain Band theory of solids. Based on this theory distinguish between insulators, conductors and semiconductors. 4
- (b) What is P-N Junction diode ? How this junction is formed practically ? Explain the formation of potential barrier in a P-N junction. 4
3. (a) What is  $\pi$ -Section filter ? Why it is so called ? Discuss its circuit and working mechanism. 4
- (b) Explain Zener diode as voltage regulator. 4

### SECTION - II

4. (a) A transistor has a base current of  $40\mu A$  and d. c. gain  $\beta_{d.c.} = 100$  and collector current when emitter open ( $I_{CEO}$ ) is  $5\mu A$ . Find its emitter current. 4

91540- (P-4)(Q-9)(16) (2)

- (b) Draw a block diagram of C. R. O. and explain the working of each part. 4

5. (a) A transistor having a voltage gain of 100 is to be used as an oscillator. What type of feedback is to be given to the input circuit and what is its feedback factor ? Find the frequency of oscillation if  $\alpha = 0.1$  mH and  $C = 400$  pF. 4
- (b) Discuss the various categories of oscillators. 4

### SECTION - III

6. (a) Sketch the graph between voltage gain and frequency in negative voltage feedback. 2
- (b) What do you mean by coupling in amplifiers ? Give its advantages and disadvantages. 2, 4
7. (a) Describe in detail the working and characteristics of an emitter follower by drawing its circuit diagrams. 6
- (b) What do you mean by transistor biasing ? 2

### SECTION - IV

8. (a) What are the characteristics that distinguish laser from ordinary light source. 4

91540- (P-4)(Q-9)(16) (3)

P. T. O.