

⇒ Boolean Algebra :-

(i) When no. of variable are less. (1,2,3)

(ii) It is preferred when output is 0 or 1.

⇒ K-map :-

(i) When no. of variables are 2,3,4,5 (upto 5 variable)

(ii) output is 0,1 or 2.

⇒ Tabulation method.

(i) It is used when no. of variables are more.

Boolean Algebra :-

⇒ A complement $\rightarrow \bar{A}$ or A'

$$\overline{\bar{A}} = A$$

⇒ NOT :-

$$0 = 1$$

$$1 = 0$$

⇒ AND :-

$$0 \cdot 0 = 0$$

$$A \cdot A = A$$

$$0 \cdot 1 = 0$$

$$A \cdot 1 = A$$

$$1 \cdot 0 = 0$$

$$A \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$A \cdot \bar{A} = 0$$

⇒ OR :-

$$0+0 = 0$$

$$A+A = A$$

$$0+1 = 1$$

$$A+1 = 1$$

$$1+0 = 1$$

$$A+0 = A$$

$$1+1 = 1$$

$$A+\bar{A} = 1$$

Problem:- $AB + A\bar{B}$

Sol:- $A(B + \bar{B})$

($\because B + \bar{B} = 1$)

$$= A$$

classmate

Problem:- $AB + A\bar{B}C + A\bar{B}\bar{C}$, find the min. no. of NAND Gate.

option. ✓ (a) 0

(b) 1

(c) 2

(d) 3

Sol:- $AB + A\bar{B}C + A\bar{B}\bar{C}$

$$= AB + A\bar{B}(C + \bar{C})$$


$$= AB + A\bar{B}$$

$$(\because C + \bar{C} = 1)$$

$$= A(\bar{B} + B)$$

$$= A$$

No NAND gate required.

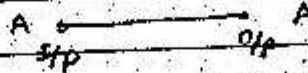

Advantage of Minimization:-

⇒ No. of logic gate ↓

⇒ speed ↑

⇒ Power dissipation ↓

⇒ complexity of circuit less.

⇒ fan in ↓ (no. of input ↓)

⇒ Cost ↓

Problem:- Simplify:-

(a) $A\bar{B} + A\bar{B}C + A\bar{B}\bar{C}D$

Sol:- $A\bar{B}C + A\bar{B}(1 + \bar{C}D)$

$$= A\bar{B}C + A\bar{B}$$

$$(1 + x = 1)$$

$$= A(\bar{B} + \bar{B}C)$$

$$(\because \bar{B} + \bar{B}C = \bar{B} + C)$$

$$= A(\bar{B} + C)$$

$$= A\bar{B} + AC$$

(b) $(A+B)(A+C)$

Sol:- $A \cdot A + AC + AB + BC$

$$= A + A(B+C) + BC$$

$$= A(1+B+C) + BC$$

$$= A + BC$$

Transposition Theorem

$$(A+B)(A+C) = A + BC$$

Similarly :

$$(\bar{x} + y)(\bar{x} + z) = \bar{x} + yz$$

(c) $(A+B+C)(A+\bar{B}+C)(A+B+\bar{C})$

Sol:- take $A+B = X$

$$= (X+C)(A+\bar{B}+C)(X+\bar{C})$$

$$= (X+C\bar{C})(A+\bar{B}+C)$$

$$= X(A+\bar{B}+C)$$

$$= (A+B)(A+\bar{B}+C)$$

$$= A + B(\bar{B}+C)$$

$$= A + B\bar{B} + BC$$

$$= A + BC$$

(d) $(A+B)(A+\bar{B})(\bar{A}+B)(\bar{A}+\bar{B})$

Sol:- $(A+B)(A+\bar{B})(\bar{A}+B)(\bar{A}+\bar{B})$

$$= (A+B\bar{B})(\bar{A}+B\bar{B})$$

$$= (A)(\bar{A})$$

$$= 0$$

$$A + BC = (A+B)(A+C)$$

Distribution theorem

(e) $A + \bar{A}B$

Sol:- $(A+\bar{A})(A+B)$

$$= 1(A+B) = A+B$$

(f) $A + \bar{A}\bar{B}$

Sol:- $(A+\bar{A})(A+\bar{B})$

$$= 1(A+\bar{B}) = A+\bar{B}$$

(g) $AB + \bar{A}\bar{B} + A\bar{B}$

Sol:- $A(B+\bar{B}) + \bar{A}\bar{B}$

$$= A + \bar{A}\bar{B}$$

$$= (A+\bar{A})(A+\bar{B})$$

$$= A + \bar{B} \text{ Ans}$$

classmate

PAGE

$$(h) AB + \bar{A}B + A\bar{B}$$

$$\text{Sol: } B(A + \bar{A}) + A\bar{B}$$

$$= B + A\bar{B}$$

$$= (B + A)(B + \bar{B})$$

$$= A + B \quad \text{Ans.}$$

$$(i) AB\bar{C} + ABC + \bar{A}BC$$

$$\text{Sol: } AB\bar{C} + ABC + ABC + \bar{A}BC$$

$$(\because A + A = A)$$

$$= AB(\bar{C} + C) + (A + \bar{A})BC$$

$$= AB + BC$$

$$= B(A + C)$$

$$(j) AB + \bar{A}C + BC \rightarrow \text{redundant term.}$$

$$\text{Sol: } AB + \bar{A}C + BC(A + \bar{A})$$

$$= AB + \bar{A}C + BCA + \bar{A}BC$$

$$= AB(1 + C) + \bar{A}C(1 + B)$$

$$= AB + \bar{A}C$$

Note: In this case BC is known as redundant term i.e. not used or not compulsory term.

$\Rightarrow AB + \bar{A}C + BC = AB + \bar{A}C$, called consensus theorem or redundancy theorem.

$\Rightarrow$ Shortcut method :-

(a) Three variable

(b) each variable comes twice.

(c) one variable is complemented.

$$(k) AB + B\bar{C} + AC$$

$$\text{Sol: } B\bar{C} + AC$$

The term which is complemented is taken.

$$(l) A\bar{B} + BC + AC$$

$$\text{Sol: } A\bar{B} + BC$$

(m) $(A+B)(\bar{A}+C)(B+C)$

Sol: $(A+B)(\bar{A}+C)$ $\therefore (B+C)$ is redundant term.

(n) $(A+B)(\bar{B}+C)(A+C)$

Sol: $(A+B)(\bar{B}+C)$

(o) $\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C}$

Sol: In this case all the variable are complemented only one are uncomplemented. then.

$$= \bar{A}\bar{B} + \bar{A}\bar{C}$$

("The term which is uncomplemented is taken)

(p) $\bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$

Sol: $\bar{B}\bar{C} + \bar{A}\bar{B} + \bar{A}\bar{C}$

(q) $(\bar{A}+B)(\bar{B}+C)(\bar{A}+C)$

Sol: $(\bar{B}+C)(\bar{A}+C)$

ed.

$$\overline{ABC} = \bar{A} + \bar{B} + \bar{C}$$

Demorgan's theorem.

$$\overline{A+B+C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

m

Boolean Algebra :-

⇒ Minimization

⇒ SOP

→ minimal

→ canonical

⇒ POS

→ minimal

→ canonical

⇒ Dual

⇒ Complement Expression

⇒ Truth table

⇒ Venn Diagram

⇒ Switching circuit

⇒ Statement

classmate

PAGE

--	--	--

(A) Minimization :-

(a) $XY + \bar{X}\bar{Y}WZ$

Sol: $A = XY$ and $B = WZ$

Then,

$$= A + \bar{A}B$$

$$= (A + \bar{A})(A + B)$$

$$= A + B$$

$$= XY + WZ$$

(b) let $f(A, B) = \bar{A} + B$ Then, the value of

$f[f(X+Y, Y), Z]$ is

(a) $XY + Z$

(c) $\bar{X}Y + Z$

Ques:

✓ (b) $X\bar{Y} + Z$

(d) X

Sol: $f[f(X+Y, Y), Z]$

$$= f[X+Y + \bar{B}Y, Z]$$

$$= f[X\bar{Y} + Y, Z]$$

$$= \bar{X}\bar{Y} + Y + Z$$

$$= \bar{X}\bar{Y} + \bar{Y} + Z$$

Sol:

$$= (\bar{X} + \bar{Y})\bar{Y} + Z$$

$$= X\bar{Y} + Y\bar{Y} + Z$$

$$= X\bar{Y} + Z \quad \text{Ans.}$$

(c) let $X * Y = \bar{X} + Y$ and $Z = X * Y$

Then the value of $Z * X$ is

(a) X

(c) 0

Ques

(b) 1

(d) $\bar{X}$

Sol

(b) SOP (Sum of Product Form)

$$ABC + \bar{A}BC + A\bar{B}C$$

↳ minterm

⇒ In SOP form, each product term is known as Minterm or Implicant.

⇒ SOP form is used when o/p of logical expression is 1.
(means $1 \rightarrow A$ and $0 \rightarrow \bar{A}$)

Ex :- $5 \rightarrow 101 \rightarrow A\bar{B}C$

$9 \rightarrow 1001 \rightarrow A\bar{B}\bar{C}D$

Ques: For the given truth table, minimize SOP expression.

	A	B	Y
$\bar{A}\bar{B}$	0	0	1 ✓
	0	1	0
$A\bar{B}$	1	0	1 ✓
	1	1	0

Sol: In SOP form only 1 taken.

$$= \bar{A}\bar{B} + A\bar{B}$$

$$= \bar{B}(\bar{A} + A)$$

$$= \bar{B}$$

⇒ Y can written as :-

$$Y(A, B) = \sum m(0, 2)$$

Ques: Simplified the expression for

$$Y(A, B) = \sum m(0, 2, 3)$$

Sol: to 10 11

logical expression in SOP form :-

$$Y = \bar{A}\bar{B} + A\bar{B} + AB$$

$$= \bar{B}(\bar{A} + A) + AB$$

$$= \bar{B} + AB$$

$$= (\bar{B} + A)(\bar{B} + B)$$

$$= A + \bar{B}$$

$$= A + \bar{B}$$

classmate

PAGE

--	--	--

SOP can be of two form.

- Minimal form
- Canonical form.

$\Rightarrow A + \bar{A}B = A + B$ (It is a minimal form)

$\Rightarrow$ In canonical form, each term must have all variable.

e.g. $A + B = A(B + \bar{B}) + \bar{A}B$

$$= AB + \bar{A}B + \bar{A}\bar{B}B$$

$$= AB + \bar{A}B + \bar{A}\bar{B}$$

Thus each min-term will contain all variable.

IES-2003

Problem:- In canonical SOP form, no. of min term presenting the logical expression $A + \bar{B}C$ is.

- 4
- 5
- 6
- 7

Sol:-

$$A + \bar{B}C = A(B + \bar{B})(C + \bar{C}) + \bar{B}C(A + \bar{A})$$

$$= (AB + \bar{A}B)(C + \bar{C}) + A\bar{B}C + \bar{A}\bar{B}C$$

$$= ABC + AB\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + \bar{A}\bar{B}C$$

$$= ABC + AB\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

i.e. 5 terms.

(c) POS Form (Product of Sum) :-

$$(A+B+\bar{C}) (\bar{A}+B+C) (A+B+C)$$

↳ max term

⇒ POS form are used when o/p is logic '0'.

$$0 \rightarrow A$$

$$1 \rightarrow \bar{A}$$

$$\text{Ex :- } 5 \rightarrow 101 \rightarrow \bar{A} B \bar{C}$$

$$3 \rightarrow 1001 \rightarrow \bar{A} B C \bar{D}$$

Ques: For a given th truth table minimize POS expression.

	A	B	Y
	0	0	1
$A+\bar{B}$	0	1	0 ✓
	1	0	1
$\bar{A}+\bar{B}$		1	0 ✓

Sol: we take only that value at which o/p is '0'.

$$Y = (A+\bar{B}) (\bar{A}+\bar{B})$$

$$= \bar{B} + A\bar{A}$$

$$= \bar{B}$$

⇒ Y can be written in POS form as,

$$Y(A,B) = \Pi M(1,3) = \bar{B}$$

and for sop :-

$$Y(A,B) = \Sigma m(0,2) = \bar{B}$$

i.e.

$$\Sigma m(0,2) = \Pi M(1,3)$$

$$\Rightarrow \text{If } F(A,B,C) = \Sigma m(0,1,4,7)$$

There are 3 variable then 8 combination then max term are, 2,3,5,6.

$$F(A,B,C) = \Sigma m(0,1,4,7) = \Pi M(2,3,5,6)$$

classmate

PAGE

⇒ with 'n' variable, maximum possible minterms or maxterms are 2^n eq.

(i) for, $n = 2$ i.e. (A, B)

∴ Total no. of min or max terms are $2^2 = 4$.

(ii) for, $n = 3$ i.e. (A, B, C)

Total no. of min or max terms are $2^3 = 8$.

⇒ For $n = 2$, (A, B) total 16 logical expression i.e.

1	A	$A\bar{B}$	AB
0	$\bar{A}$	$\bar{A}B$	$A+B$
$\bar{A}B + A\bar{B}$	B	$A+\bar{B}$	$\bar{A}\bar{B}$
$AB + \bar{A}\bar{B}$	$\bar{B}$	$\bar{A}+B$	$\bar{A}+B$

Note:- With n variable maximum possible logical expression are 2^{2^n}

eq. for $n = 2$, logical expression = $2^{2^2} = 16$
for $n = 3$, logical expression = $2^{2^3} = 256$

PES-2004
GATE-2002
JTO-2001
JRO-2002

Problem:- For $n = 4$ what is the total no. of logical expression.

Sol:- logical expression = 2^{2^4}
 $= 2^{16} = 65536$.

(D) Dual Form :-

+ive logic
⇒ +ive logic means higher voltage corresponds to logic '1'.

⇒ logic '0' → 0V
logic '1' → +5V

-ive logic
⇒ -ive logic means higher voltage corresponds to logic '0'.

⇒ logic 0 = +5V
logic 1 = 0V

Ques:- logic 0 → -5V
logic 1 → 0V

Sol:- Higher value of voltage (0V) for logic 1. then +ive logic.

Ques:- ECL :
logic '0' → -1.7V
logic 1 → -0.8V

Sol:- -0.8V is larger value than -1.7V then it is +ive logic.

+ive logic AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

-ive logic AND

A	B	Y
1	1	1
1	0	1
0	1	1
0	0	0

+ive logic OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

-ive logic OR

A	B	Y
1	1	1
1	0	0
0	1	0
0	0	0

⇒ For -ive logic OR gate, convert 1 to 0 and 0 to 1.

⇒ We can say that +ive logic AND gate is equal to -ive logic OR gate and -ive logic AND gate is equal to +ive logic OR gate.

classmate

PAGE

--	--

⇒ Dual expression is used to convert +ive logic into -ive logic or, -ive logic to +ive logic.

⇒ $AB \xrightarrow{\text{Dual}} A+B$

Dual is nothing but -ive logic.

⇒ $\text{AND} \xrightarrow[\text{Dual}]{\text{-ive logic}} \text{OR}$

⇒ $\text{OR} \xrightarrow[\text{Dual}]{\text{-ive logic}} \text{AND}$

(i) $\text{AND} \longleftrightarrow \text{OR}$

(ii) $\cdot \longleftrightarrow +$

(iii) $1 \longleftrightarrow 0$

(iv) keep variable as it is

Dual.

Problem: Find Dual.

$$AB\bar{C} + \bar{A}BC + ABC$$

Sol:- Dual:-

$$(A+B+\bar{C})(\bar{A}+B+C)(A+B+C)$$

If we find again dual then,

$$AB\bar{C} + \bar{A}BC + ABC$$

⇒ For any logical expression, if two times dual is used resulting same expression.

Self Dual:-

$$AB + BC + AC$$

Dual:-

$$= (A+B)(B+C)(A+C)$$

$$= (B+AC)(A+C)$$

$$= BA + BC + AC + AC$$

$$= AB + BC + AC \quad (\text{again same expression})$$

⇒ In some of the logical expression not all its dual gives the same expression.

classmate

⇒ In self dual expression, if one time dual is used result in same expression.

$$n \text{ variable} \rightarrow \text{self dual} = 2^{2^{n-1}}$$

i.e. If there are n variables then total no. of self dual expression is $2^{2^{n-1}}$.

eg :-

(i) For $n=1 \Rightarrow 2^{2^{1-1}} = 2$.

Then 2 dual expression.

$$A \rightarrow \text{Self dual} \rightarrow A$$

$$\bar{A} \rightarrow \bar{A}$$

Total self dual expression are 2.

(ii) For $n=2 \Rightarrow 2^{2^{2-1}} = 4$.

Then 4 dual expression.

$$A \rightarrow A$$

$$B \rightarrow B$$

$$\bar{A} \rightarrow \bar{A}$$

$$\bar{B} \rightarrow \bar{B}$$

(iii) For $n=3 \Rightarrow 2^{2^{3-1}} = 16$.

Then 16 dual expression.

$$A, \bar{A}, B, \bar{B}, C, \bar{C}, \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A}, AB + BC + CA, \dots$$

(E) Complement :-

$$\text{If } Y = ABC + \bar{A}BC + A\bar{B}C$$

complement is,

$$\bar{Y} = (\bar{A} + \bar{B} + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})$$

(i) $\text{AND} \leftrightarrow \text{OR}$

(ii) $\cdot \leftrightarrow +$

(iii) $1 \leftrightarrow 0$


(iv) complement of each variable.

complement.


(F) Venn Diagram :-

Sol :-

For two variable (A, B).

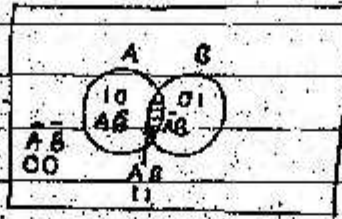

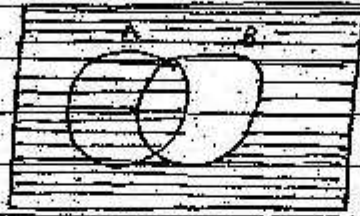Ques :- For a given venn diagram , minimize the SOP expression for shaded region.



Sol :-

$$\begin{aligned}
 Y &= \bar{A}\bar{B} + A\bar{B} + AB \\
 &= \bar{B}(\bar{A} + A) + AB \\
 &= \bar{B} + AB \\
 &= (\bar{B} + A)(\bar{B} + B) \\
 &= A + \bar{B} \\
 &\quad \downarrow \quad \downarrow \\
 &\quad (0 \ 1) \text{ for posform.}
 \end{aligned}$$

Ques :- SOP expression for Shaded region.



Sol :-


$$\begin{aligned}
 Y &= AB + A\bar{B} + \bar{A}B \\
 &= A(B + \bar{B}) + \bar{A}B \\
 &= A + \bar{A}B \\
 &= (A + \bar{A})(A + B) \\
 &= A + B \\
 &\quad \downarrow \quad \downarrow \\
 &\quad (0 \ 0) \longrightarrow \text{(in posform)}
 \end{aligned}$$

Ques :- SOP expression



$$\begin{aligned}
 \text{Sol: } & \bar{A}B + A\bar{B} + AB + \bar{A}\bar{B} \\
 &= B(A + \bar{A}) + \bar{B}(A + \bar{A}) \\
 &= B + \bar{B} \\
 &= 1.
 \end{aligned}$$

⇒ For 3-variable :-

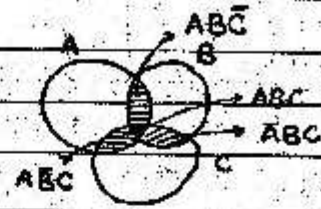

SOP form for shaded portion


$$\begin{aligned}
 &= ABC + \bar{A}BC + A\bar{B}C + A\bar{B}\bar{C} + ABC + ABC \\
 &= BC(A + \bar{A}) + AB(\bar{C} + C) + AC(B + \bar{B}) \quad \rightarrow \text{extracted} \\
 &= AB + BC + CA
 \end{aligned}$$

(G) Switching Circuit :-

For Series :-

Truth table :-

A	Y
0	0
1	1

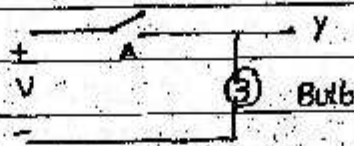

For Parallel :-

A	Y
0	1
1	0



⇒ In place of bulb if there is resistor then answer remains the same but some drop.


Truth table :-

A	Y
0	1
1	0




⇒ In place of switch if there is a transistor.

A	Y
0	1
1	0

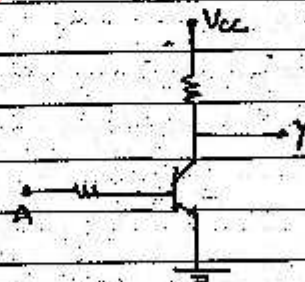

(i) For A=1 transistor becomes short circuit.

For two switch A and B :-

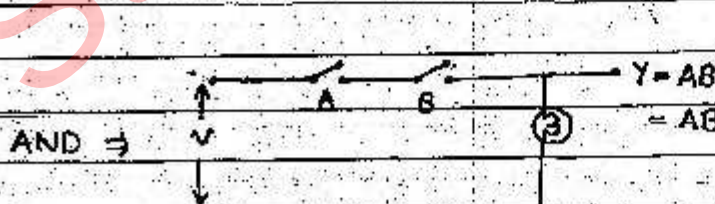

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND ⇒



A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Ques:-



Sol:- $Y = A \cdot (B+C) \cdot D$

$$= (AB+AC) D$$

$$= ABD + ACD$$

(H) STATEMENT :-

(I)

Ques:- A logic circuit have 3 input A, B, C and o/p is Y.

o/p Y is 1 for the following combination.

(i) B and C are true $= BC$ (ii) A and C are false $= \bar{A}\bar{C}$ (iii) A, B and C are true $= ABC$ (iv) A, B and C are false $= \bar{A}\bar{B}\bar{C}$

then minimize the o/p for Y.

Sol:- o/p Y = 1. (take min term = SOP form)

$$Y = BC + \bar{A}\bar{C} + ABC + \bar{A}\bar{B}\bar{C}$$

$$= BC(1+A) + \bar{A}\bar{C}(1+B)$$

$$= BC + \bar{A}\bar{C}$$

If o/p Y = 0, then take max term (POS form).

Ques:- A logic ckt have 3 input A, B, C and o/p is F = 1 when majority no. of I/p's are logic 1.

* in minimizing expression F

(i) Implement logic ckt

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

$$= \bar{A}BC + ABC + A\bar{B}C + A\bar{B}\bar{C} + ABC + ABC$$

$$= BC(A+\bar{A}) + AC(B+\bar{B}) + AB(\bar{C}+C)$$

$$= AB + BC + CA$$

(I) LOGIC GATES :-

→ Basic Building Blocks

NOT
AND
OR

→ Basic gate

NAND
NOR

→ universal gate

EXOR → Arithmetic opt.

EXNOR → comparator, parity generator/checker, code converters
(Binary to gray, Gray to Binary)

NOT :-

A → NOT → $\bar{A} = Y$


A → NOT → $A = Y$

A	Y
0	1
1	0

IES-2010
GATE-2010

Ques: Circuit shown in the fig are

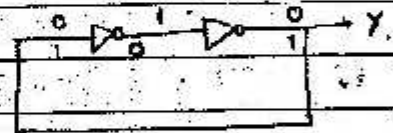- Buffer
- Astable MV.
- Bistable MV.
- square wave generator.



Sol: If there is no feedback then it is buffer. In Buffer if we apply 0 then get 0

" 1 " " 1.


" no I/p " " no I/p.

Buffer means whatever the I/p is, the o/p.

→ But there is a feedback and the o/p is stable if we give 1 as I/p, o/p is also 1 and if gives 0 then o/p is 0 then two stable state.

→ Hence it is Bistable multivibrator.


Ques:- Ckt shown is

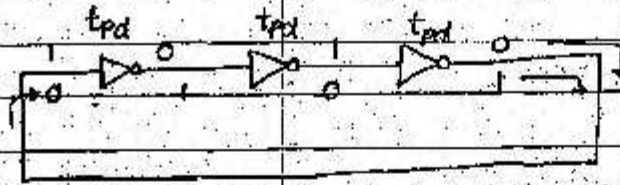

Sol:- t_{pd} = Propagation delay.

'0' for = $3t_{pd}$

'1' for = $3t_{pd}$

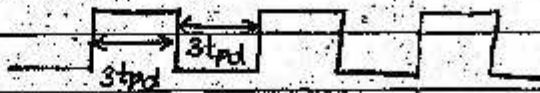

It is called

(i) Square wave generator.

(ii) As o/p is not stable sometime 1 and sometime 0
Hence it is also called astable multivibrator.

(iii) clock generator

(iv) Ring oscillator.


Total time period (T) = $6t_{pd}$

then,

$$T = 2N t_{pd}$$

N = no. of inverters in feedback.

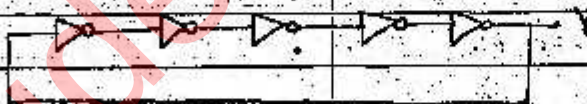Ques:- In a ckt shown in fig. the propagation delay of each NOT gate is 100 Psec. Then frequency of generator square wave is



(a) 10 GHz

(b) 1 GHz

(c) 100 MHz

(d) 10 kHz


Sol:- $T = 2N t_{pd}$

$$= 2 \times 5 \times 100 \text{ Psec} = 1000 \text{ Psec}$$

$$f = \frac{1}{T} = \frac{1}{1000 \times 10^{-12} \text{ sec}} = 10^9 \text{ Hz}$$

$$\text{alternately} = 1 \text{ GHz}$$

Ques:-

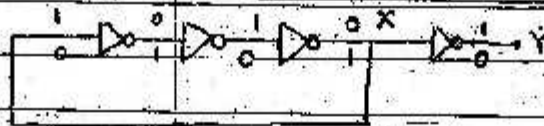

Sol:- The ckt shown in the fig the propagation delay of each NOT gate is 2 nsec. Then time period of generated square wave is.

(a) 6 ns

(b) 14 ns


(c) 12 ns

(d) 18 ns

Sol:- Astable Multivibrator, square wave generator.


$$T = 2 N t_{pd}$$
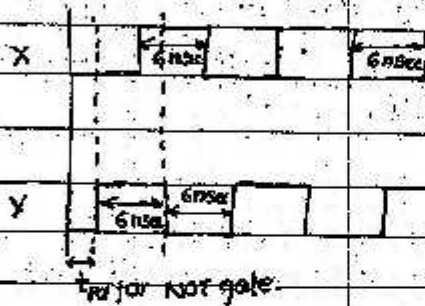
$$= 2 \times 3 \times 2 \text{ nsec} = 12 \text{ nsec}$$



Thus time period of x and y is same.

AND GATE :-

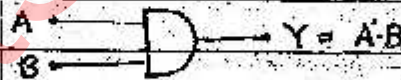


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

⇒ o/p is low if any of the i/p is low i.e logic '0'.


⇒ AND gate follow both commutative law and associative law.

$$(i) AB = BA$$

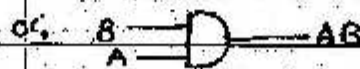


classmate


$$(i) ABC = (AB) \cdot C = A(BC)$$

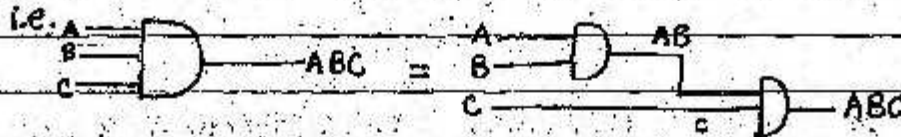

⇒ Disable & Enables :-

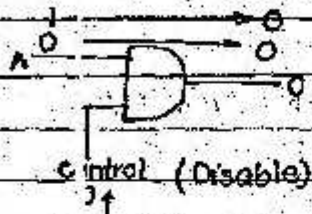

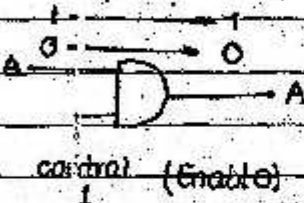⇒ Thus o/p remains in '0' due to control i/p disable. AND gate is not in working state.




⇒ AND gate is in working state, o/p is changing in Enabled state.

Note


⇒ In TTL logic family, If any i/p is open and float then it will act as '1'.

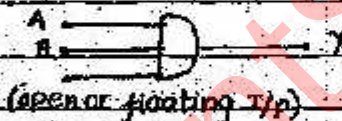⇒ In ECL logic family, floating input will act as logic '0'.



* Question occurs mostly from ECL and TTL in Exam.



Unused I/p's :-

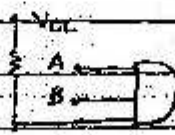

⇒ In Multipin (I/p) AND gate unused i/p can be connected to logic 1. or "pull up".

⇒ unused i/p can be connected to logic '0' or "pull down".

inaccurate

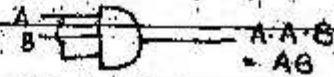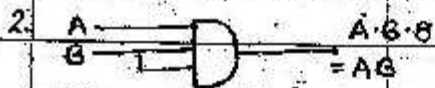


⇒ unused I/p can be connected to one of the used I/p.



⇒ If it is TTL logic family, then unused I/p can be open or floated. (unconnected).


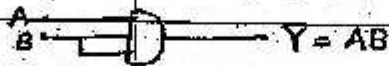
Note:- Because of unnecessary I/p attached to B, fan in will be down.



⇒ Best way to connecting unused pin (I/p) in AND gate is connecting to logic '1'.



OR Gate :- (Inclusive OR)

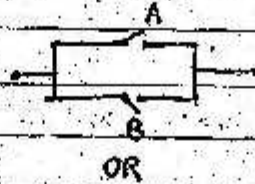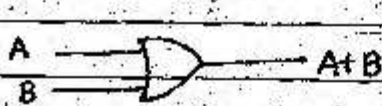


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

⇒ When any of the I/P is High in OR gate then o/p is High.

⇒ OR gate follows both commutative and Associative law.

(i) Commutative law :-

$$A+B = B+A$$

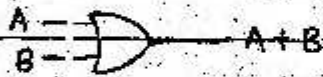


(ii) Associative law :-


$$A+B+C = (A+B)+C = A+(B+C)$$



⇒ Enable and Disable :-

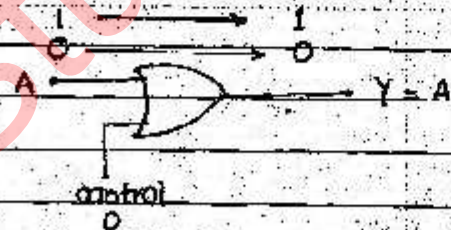

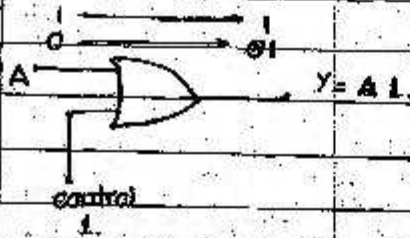⇒ o/p is changing as I/P is changing or we say the gate is enabled.



⇒ o/p is fixed or not changed.
it is said to be disable.


Unused I/p's :-

1. In OR gate, unused I/p is connected to logic '0'. "pull down."
 2. Connect to one of the used I/p.
 3. If it is ECL then unused I/p can be open or floated.
- ⇒ In OR gate, Best way of connecting the unused I/p is to connect to logic '0'.



Gate-2024.

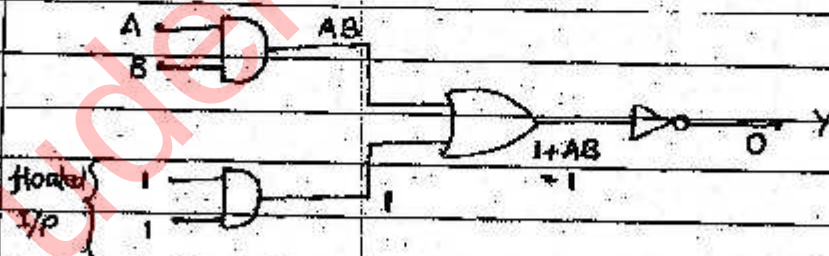Problem:- In the CKT shown in fig. in TTL, AND, OR, INVERTER CKT for the given I/p o/p is.



- I/P
- Q
- (a) 0
 - (b) 1
 - (c) AB
 - (d) $\overline{AB}$


Sol:- In TTL, all I/p's are float then it is logic 1

classmate

DATE

--	--	--	--	--	--


Problem: For ECL AND, OR, INVERTER.

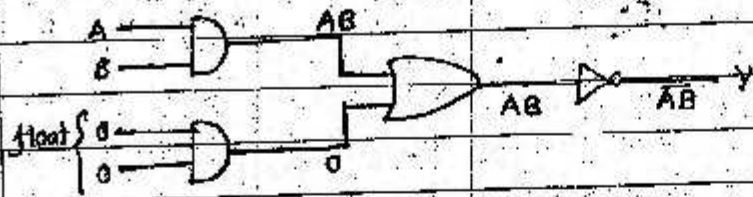

- (A) 0
- (B) 1
- (C) AB
- (D) $\overline{AB}$


Sol: If all i/p are floating in ECL then it is '0'
and o/p $Y = \overline{AB}$ Ans.

NAND GATE :- (Bubbled OR)

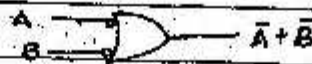


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

⇒ When both I/p high the o/p is low.

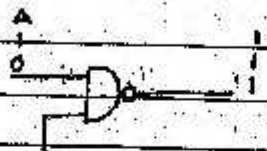


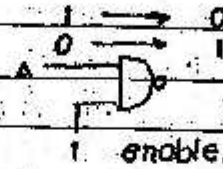0 disable (not changing if one I/p is zero)



1 enable.

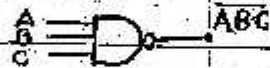⇒ NAND gate follow commutative law but not follow associative law



≠



$$(AB)C = AB + C$$



⇒ The only two gate not follow associative law i.e universal gate NAND or NOR gate.

⇒ Unused I/p in NAND gate can be connected similar to unused I/p in AND gate.



NOR GATE :- (Bubbled AND)

⇒ OR gate followed by NOT gate.

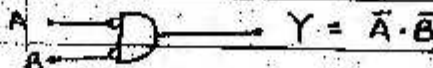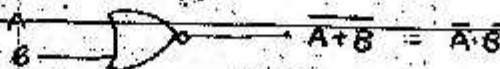

classmate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

⇒ When both I/p is low the o/p is High.



⇒

⇒ enable and disable both are same as OR gate.

⇒ NOR gate follow commutative law and not follow associative law.

i.e. (i) $A+B = B+A$


(ii) $A+B+C \neq A+B \cdot C$

⇒ unused I/p in NOR gate can be connected similar to OR gate.

EXOR or, XOR :-

⇒ Exclusive OR gate.

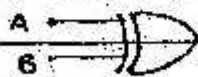⇒ OR gate is also called as inclusive OR gate.




$Y = A \oplus B$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

⇒ When $A=B$, o/p is low i.e. '0'.

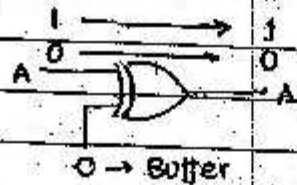⇒ When $A \neq B$, o/p is High i.e. logic '1'.



⇒ It is also called controlled inverter.

Note:-

$$A \oplus A = 0$$

$$A \oplus A = 1$$

$$A \oplus 0 = A$$

$$A \oplus 1 = \bar{A}$$

⇒ If $A \oplus B = 0$ then

(i) $A \oplus C = B$

(ii) $B \oplus C = A$

(iii) $A \oplus B \oplus C = 0$

⇒ Since, $A \oplus A = 0$

$$A \oplus A \oplus A = A$$

$$A \oplus A \oplus A \oplus A = 0$$

and so on...

Then we say,

odd no. of same I/p gives same o/p.

and even no. same I/p gives zero as o/p.

⇒ $B \oplus B \oplus B \oplus \dots \oplus B = B$ if n is odd
 $= 0$ if n is even.


Problem:- The ckt shown in fig. contains cascading of 20 EXOR gate.
 If X is the I/p then o/p is.

(a) 0

(b) 1

(c) X


(d) $\bar{X}$

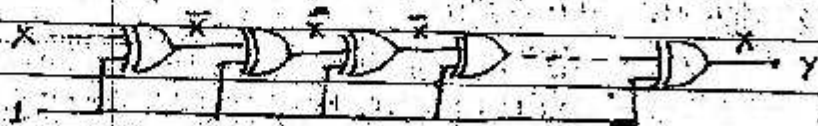


Sol: o/p of even EXOR gate have same o/p.

= X Ans.

Internal Diagram of EXOR gate :-

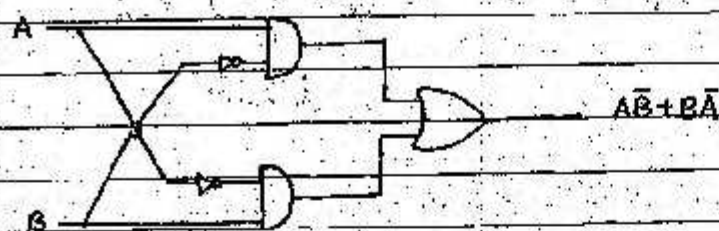

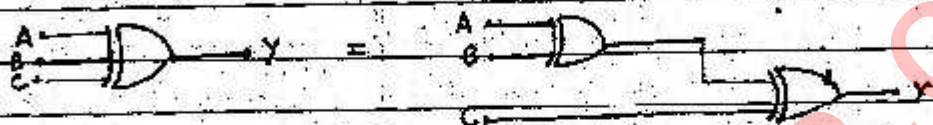- ⇒ EXOR gate follow both commutative and associative law.
- ⇒ EXOR gate is follow available with two I/P's only.



Truth table :-

	A	B	C	Y (A ⊕ B ⊕ C)
	0	0	0	0
→	0	0	1	1
→	0	1	0	1
	0	1	1	0
→	1	0	0	1
	1	0	1	0
	1	1	0	0
→	1	1	1	1

- ⇒ The o/p of EXOR gate is 1, when no. of 1's at the I/P is odd no.

⇒ logical expression :-

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$
$$= 001 + 010 + 100 + 111 \rightarrow \text{odd no. of 1's}$$


$$Y = \sum m(1, 2, 4, 7)$$

- ⇒ The reduced form of this expression is,

$$A \oplus B \oplus C$$

classmate

EXNOR or XNOR :-

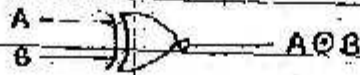

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

⇒ Whenever the I/p is same o/p is High.

SOP expression = $\bar{A}\bar{B} + AB$


POS expression = $(A + \bar{B})(\bar{A} + B)$

EXOR :-	$\bar{A}B + A\bar{B}$	← SOP →	EXNOR :-	$\bar{A}\bar{B} + AB$
	$(A + B)(\bar{A} + \bar{B})$	← POS →		$(A + \bar{B})(\bar{A} + B)$

⇒ When $A = B$, then o/p is High.
therefore coincidence logicckt and also called as equivalent detector.

⇒ When $A \neq B$, The o/p is low.

⇒ Enable and Disable:-

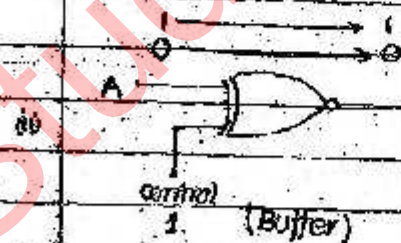

classmate

PAGE

$$A \oplus A = 1$$

$$A \oplus \bar{A} = 0$$

$$A \oplus 0 = \bar{A}$$

$$A \oplus 1 = A$$

Since, $A \oplus A = 1$

$$A \oplus A \oplus A = A$$

$$A \oplus A \oplus A \oplus A = 1$$

and so on.

$$B \oplus B \oplus B \oplus \dots \oplus B = \begin{cases} 1 & \text{if } n = \text{even} \\ B & \text{if } n = \text{odd} \end{cases}$$

$\Rightarrow$ EXOR and EXNOR is not always complement, it is complement only when the no. of i/p is even and if i/p is odd then EXOR and EXNOR are same.

i.e. $A \oplus B \oplus C = A \oplus B \oplus C \Rightarrow$ same

and, $A \oplus B \oplus C \oplus D = A \oplus B \oplus C \oplus D \Rightarrow$ complement

Ques: Find expression of $A \oplus B \oplus C$.

Sol:

$$A \oplus B \oplus C$$

$$= (\bar{A}\bar{B} + AB) \oplus C$$

$$= (\bar{A}\bar{B} + AB)\bar{C} + (\bar{A}\bar{B} + AB)C$$

$$= (\bar{A}\bar{B} \cdot \bar{A}\bar{B})\bar{C} + (\bar{A}\bar{B} + AB)C$$

Since,

$$(\bar{A}\bar{B} + AB) = (\bar{A} \oplus B) = A \oplus B = \bar{A}\bar{B} + AB$$

$$= (\bar{A}\bar{B} + AB)\bar{C} + (\bar{A}\bar{B} + AB)C$$

$$= \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}C + ABC$$

$$= A \oplus B \oplus C$$

classmate

PAGE

Ques- Minimize

	A	B	C	Y	
→	0	0	0	1	(A) $A \oplus B \oplus C$
	0	0	1	0	(B) $A \oplus B \oplus C$
	0	1	0	0	✓(C) $A \oplus B \oplus C$
→	0	1	1	1	(D) $AB + BC + AC$
	1	0	0	0	
→	1	0	1	1	
→	1	1	0	1	
	1	1	1	0	

Sol: for EXOR → O/P is 1 when odd no. of 1's at I/P.

In this case,

$$Y = A \oplus B \oplus C$$

$$= A \oplus B \oplus C \quad \text{Ans.}$$

⇒ EXOR and EXNOR are never always complemented, It is complement only when even variable occurs.

⇒ EXNOR gate is even no. of 1's detector when no. of I/P's are even.

⇒ EXNOR gate is odd no. of 1's detector when no. of I/P's are odd.

Problem:- $\bar{A} \oplus B = A \oplus B$

Sol:- Put $x = \bar{A}$, $y = B$

$$x \oplus y$$

$$= A \cdot \bar{x} \bar{y} + \bar{A} \cdot x \bar{y}$$

$$= A \bar{B} + \bar{A} B = A \oplus B$$

Problem:- $\bar{A} \oplus \bar{B}$

Sol:- Put $x = A$, $y = \bar{B}$

$$= x \oplus y$$

$$= x \bar{y} + \bar{x} y$$

$$= A \bar{B} + \bar{A} B$$

$$= A \oplus B$$

classmate

PAGE 11

Problem: $A \oplus B \oplus AB$

Sol:- $(A\bar{B} + \bar{A}B) \oplus AB$

$$= (A\bar{B} + \bar{A}B)\bar{A}B + (A\bar{B} + \bar{A}B)AB$$

$$= A\bar{B}(\bar{A} + B) + \bar{A}B(\bar{A} + B) + (\bar{A}\bar{B} \cdot \bar{A}B)AB$$

$$= A\bar{B} + \bar{A}B + [(\bar{A} + B)(A + \bar{B})]AB$$

$$= A\bar{B} + \bar{A}B + [\bar{A}B + AB]AB$$


$$= A\bar{B} + \bar{A}B + AB$$

$$= A(\bar{B} + B) + \bar{A}B = A + \bar{A}B$$

$$= (A + \bar{A})(A + B) = A + B \text{ Ans.}$$

$$A \oplus B \oplus AB = A + B$$

Problem:

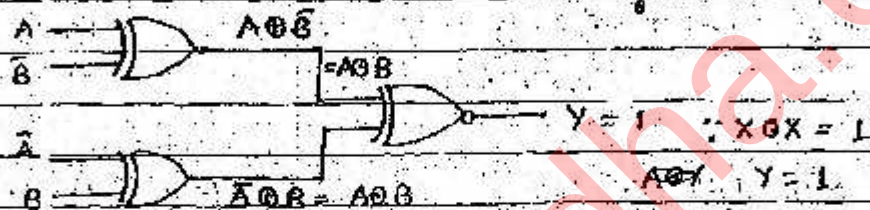

(a) 0


(b) 1

(c) $A \oplus B$


(d) $A \oplus B$

Sol:- $Y = 1 \text{ Ans.}$

SYMBOLS :-

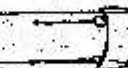
NAND $\Rightarrow$  $\Rightarrow$  Bubbled OR


NOR $\Rightarrow$  $\Rightarrow$  Bubbled AND

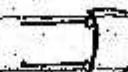
AND $\Rightarrow$  $\Rightarrow$ 


OR $\Rightarrow$  $\Rightarrow$ 

NAND as Universal :-

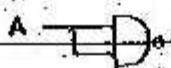
(i) NOT :-  $\Rightarrow$ 1 gate required

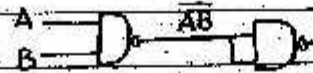(ii) AND :-  $\Rightarrow$ 2 gate

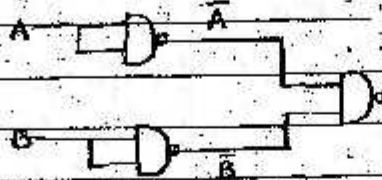(iii) OR :-  $\Rightarrow$ 3 gate.

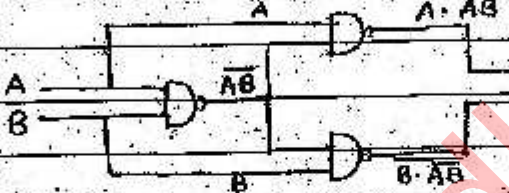(iv) EXOR :-  $\Rightarrow$ 4 Gate.

$$\begin{aligned} Y &= (A \cdot \bar{A} \bar{B} + B \cdot \bar{A} \bar{B}) \\ &= (A \cdot \bar{A} \bar{B} + B \cdot \bar{A} \bar{B}) \\ &= (A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})) \\ &= \bar{A} \bar{B} + \bar{B} A = A \oplus B \end{aligned}$$

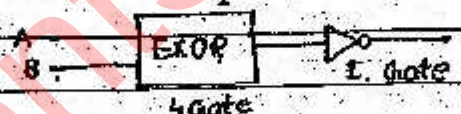(v) EXNOR :-  $\Rightarrow$ 5 Gate.

(vi) NOR :-  $\Rightarrow$ 4 Gate


classmate

PAGE


NOR AS universal :-

Note


(i) NOT :-

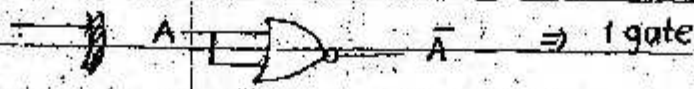


(ii) AND :-

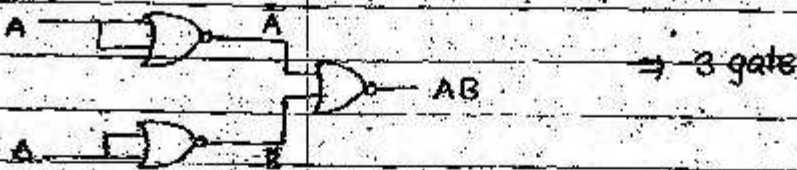

(iii) OR :-

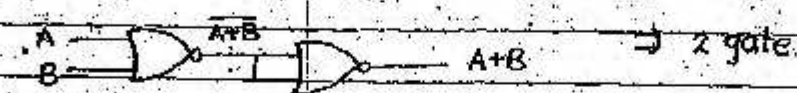

(iv) EXNOR :-

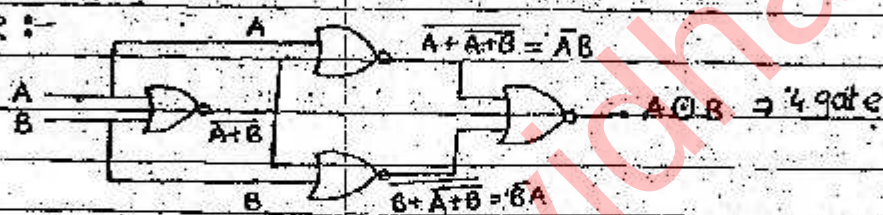


$$Y = \overline{(\bar{A} + A + B) + (B + A + \bar{B})} = \overline{\bar{A}(A + B) + B(A + \bar{B})}$$


$$= \overline{(\bar{A} + \bar{A}B)(B + A + \bar{B})} = \overline{AB + \bar{B}A} = \overline{AB + BA} = \overline{A \oplus B}$$

$$AB + A(\bar{A}B) + B(\bar{A}B) + AB = A \oplus B$$

(v) EXOR :-

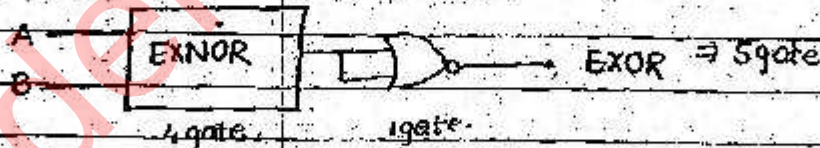

(vi) NAND

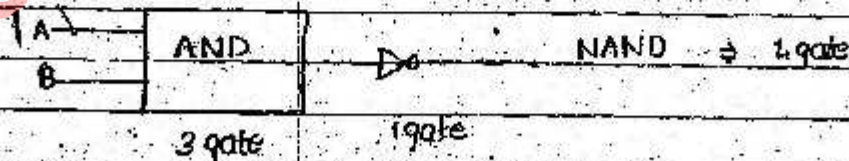

classmate

PAGE

Note:-	Logic gate	No. of NAND	No. of NOR
	NOT	1	1
	AND	2	3
	OR	3	2
	EXOR	4	5
	EXNOR	5	4

Problem:- To implement $\bar{X}YZ$. The min no. of two I/p NAND gate required.


Sol:-



Total no. of NAND gate = $2 + 2 + 1 = 5$ Ans.

Problem:- To implement $XY + WZ$, the min no. of 2 input NAND gate required.

Sol:-

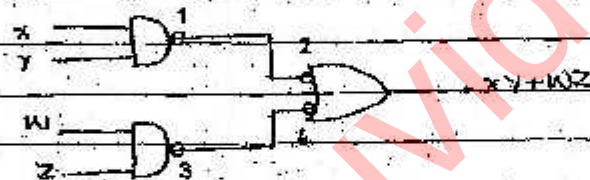

⇒ 1st inverter cancelled 2nd and 3rd cancelled 4th

⇒ Now the total no. of NAND gate is.

= 2 + Bubbled OR (= NAND)

= 2 + 1 = 3

= 3 NAND gate required.

Note:-



Two level AND-OR = Two level NAND-NAND

AND-OR = NAND-NAND

classmate


PAGE

⇒ To implement SOP form, only NAND gate alone.


⇒ To implement POS form, only NOR gate alone.

Q:- if $(A+B)(C+D)$, then min no. of gate.

Sol:-

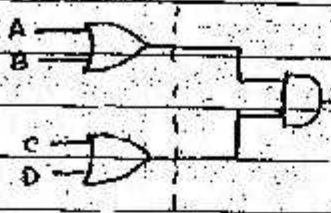

Twolevel OR-AND

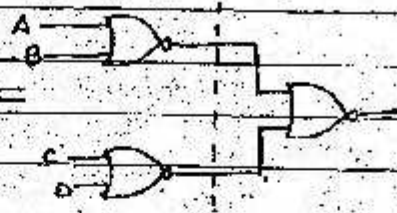

Twolevel NOR-NOR

⇒

OR-AND = NOR-NOR