 


☆ COUNTERS :-

⇒ counters are basically used to count no of clock pulse applied. it can also be used for frequency divider, time measurement, frequency measurement, Range measurement, pulse width.

pulse.  $16 \times \text{pulse width} = \text{Total width}$

⇒ Also used for waveform generator.

⇒ With n ff, max. possible stage in the counter is 2^n

$$N \leq 2^n$$

$$\text{or, } n \geq \log_2 N$$

where N = no. of stage


n = no. of FF.

Depending on clock pulse applied counters of two type:

- (i) Asynchronous
- (ii) Synchronous

Asynchronous	Synchronous
1. Different FF are applied with different clock.	1. All FF are applied same clock.
2. It is slower.	2. It is faster.
3. Fixed count sequence i.e. up or down.	3. Any count sequence is possible.
4. Decoding errors will present.	4. No decoding error will present.
5. Ripple counter	5. Ring counter

 
⇒ No. of stage use in counter mean modulus of counter.
 i.e. if MOD 5 counter = 5 stage.
 MOD n counter = n stage



Q. A decade counter is applied with frequency of 10MHz then o/p frequency is.

So: $f_{out} = \frac{f_{in}}{10} = \frac{10 \text{ MHz}}{10} = 1 \text{ MHz}$

 ⇒ Let MOD M and MOD N are cascaded then it will act as MOD MN counter.



content :-

Basic

Ripple counter

- Non binary ripple counter

Ring counter

Johnson counter

Synchronous series carry

Synchronous parallel carry

Synchronous counter design and Analysis.

(A) Ripple counter :-

⇒ It is a Asynchronous counter.

⇒ Different FF used different clock pulse.

⇒ Toggle mode.

⇒ Only one FF is applied with external clk and other FF's are clk is from previous ff o/p. (whether Q or $\bar{Q}$).


⇒ The FF applied with external clk will acts as LSB bit.

L₁

classmate

PAGE

3 bit ripple counter :- (up counter)

 

(i) Explanation :-

- The ckt shown in fig. Q_0 toggle for every clk pulse
- Q_n change when Q_{n-1} change from 1-0. i.e. Q_1 changes when Q_0 changes from 1-0.


(ii) Truth table :-

CLK	Q_2	Q_1	Q_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

→ This is up counter.

→ It is also called MOD 8 ripple counter.

(iii) Timing Diagram :-

 

classmate

PAGE

⇒ In n bit ripple counter propagation delay of each ff is t_{pdff} . then time period of clk is,

$$t_{clk} \geq n t_{pdff}$$

$$t_{clk} \leq \frac{1}{n t_{pdff}}$$

$$f_{max} = \frac{1}{n t_{pdff}}$$

Note:-

- (i) -ive edge trigger → Q as clock → up counter
- (ii) +ive " " → $\bar{Q}$ as clock → up counter
- (iii) -ive " " → $\bar{Q}$ as clock → down counter
- (iv) +ive " " → Q as clock → down counter

3-Bit Ripple counter (Down counter):-



(i) Explanation:-

- ⇒ The ckt shown in fig. Q_0 toggles for every clock pulse.
- ⇒ Q_1 toggles when Q_0 changes from 0 to 1.
- ⇒ Q_2 toggles when Q_1 changes from 0 to 1.

(ii) Truth table:-

Clock	Q_2	Q_1	Q_0
0	0	0	0
1	1	1	1
2	0	1	0
3	1	0	1
4	1	0	0
5	0	1	1
6	0	1	0
7	0	0	1

PAGE


⇒ This is called ripple counter, because the input clock is the o/p of previous FF output. this is just like ripple, then called ripple counter.

⇒ if the o/p is (000) and clock is applied then t_{pd} is delay

$t_{pd} \rightarrow \begin{cases} 001 \\ 011 \end{cases}$ unwanted or decoding error,
 also called transient state.

⇒ Decoding errors or transient state present in ripple counter due to propagation delay.

 ⇒ To avoid decoding error strobe signal is used.



⇒ i.e. strobe signal is zero for $n t_{pd}$ and after that it is one for next clock. then all the o/p. is zero for the transient time therefore due to strobe signal we can remove decoding error.


$$T_{clk} \geq n t_{pd} + T_s$$

⇒ In ripple counter with n ff, max. possible state is 2^n .

⇒ frequency after n SFF in the ripple counter is $f/2^n$ (i.e. for 3 FF o/p is $f/8$)

clock
like
is delay

 
⇒ Clear and preset are known as Asynchronous I/p.
 S, R, J, K, D, T are Synchronous I/p.
 Clear :- clear is use to reset our FF or counter.
 Preset :- preset is use to set our FF or counter.



(B) Non Binary Ripple counter :-

(B1) BCD counter :- (Decade counter)


⇒ 4 flip flop used.

 


CLK	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
0	0	0	0	0

decade

 (1010)
 $Q_3 \bar{Q}_2 \bar{Q}_1 \bar{Q}_0$



 if we use only Q_3 and Q_1 , we also use this as clear ckt.



⇒ All BCD counter is decade counter but reverse is not true.

⇒ BCD counter is Asymmetric o/p time diagram.

⇒ o/p frequency of BCD counter is $f/10$.

⇒ low for 8 clock and high for 2 clock in Q_3 .

⇒ duty cycle is 20%.

Imp ⇒ In Asynchronous counter follow steps:-

1. Trigger $\begin{cases} \rightarrow +ive \\ \rightarrow -ive \end{cases}$

2. clock $\begin{cases} \rightarrow Q \\ \rightarrow \bar{Q} \end{cases}$


3. counter $\begin{cases} \rightarrow UP \\ \rightarrow Down \end{cases}$

4. Preset/clear $\begin{cases} \text{clear} \rightarrow 000 \\ \text{Preset} \rightarrow 111 \end{cases}$

5. Decoding logic (terminating logic).

 (i) Ring Counter :- (Synchronous counter)

⇒ The last ff o/p is connected to first ff I/P.



(ii) Explanation:-

⇒ Only one ff o/p is high and remaining FF are low.

⇒ In 4 bit ring counter 4 states are there. (i.e. For n FF there is n states).


(iii) Truth table :-

CLK	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	1	0	0	0

4-state

⇒ In synchronous counter the +ive edge or -ive edge, the o/p remains same.

(iv) Time Diagram:-

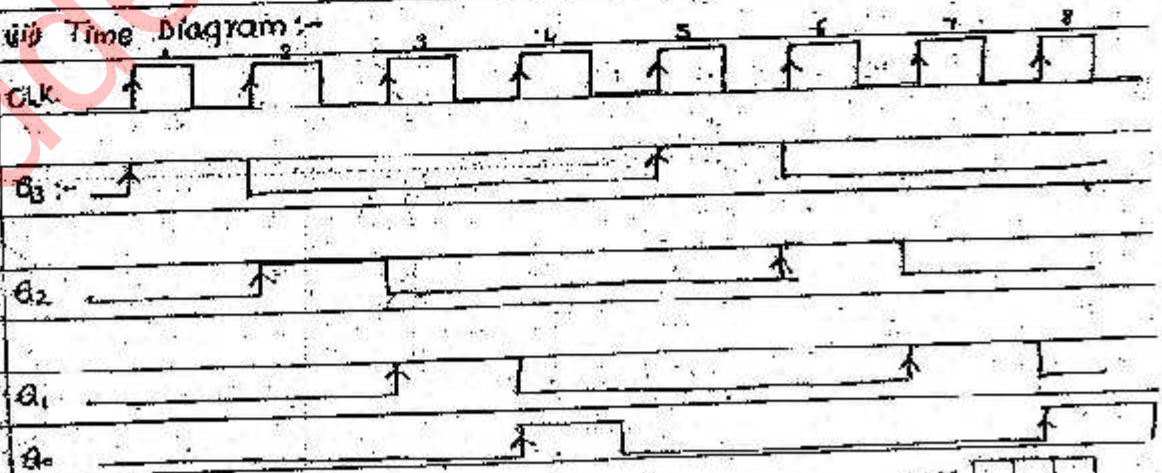

classmate

$$\Rightarrow \begin{array}{l} n \text{ bit} \Rightarrow n \text{ state} \\ \Rightarrow t_0 = \frac{t}{n} \end{array}$$

$\Rightarrow$ Phase shift b/w generated waveform is $360/n$.

$$\phi = \frac{360}{n}$$


Application :-

$\Rightarrow$ used in stepper motor control.


$\Rightarrow$ in Analog to Digital converter

$\Rightarrow$ No. of unused state in ring counter is $2^n - n$.

ring counter using J-K :-

 

* self starting Ring counter :-


 


$\Rightarrow$ Advantage of Ring counter is decoding is simple. to decode no logic gate are required.

$\Rightarrow$ last o/p can not be connected in the i/p of self start ring counter.

  (D) Johnson Counter :-

- ⇒ Symmetric o/p waveform.
- ⇒ 8-stages are there for 4 bit counter.
- ⇒ phase shift = $\frac{360}{4} = 90^\circ$
- ⇒ It is just like SISO register.



iii) Truth Table :-

CLK	Q ₃	Q ₂	Q ₁	Q ₀
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	0	1
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1
8	0	0	0	0

8 state

- ⇒ Total no. of used state = 8
- ⇒ Total no. of unused state = $2^n - 8 = 2^4 - 8 = 8$ state.
- ⇒ Also called Twisted^{ring} counter, Mobius counter or, creeping counter or, walking counter or, switch tail counter.

CLOCK	Q_3	Q_2	Q_1	Q_0	
0	0	0	0	0	$\rightarrow \bar{Q}_3 \bar{Q}_0$
1	1	0	0	0	$\rightarrow Q_3 \bar{Q}_1$
2	1	1	0	0	$\rightarrow Q_3 \bar{Q}_1$
3	1	1	1	0	$\rightarrow Q_3 \bar{Q}_0$
4	0	1	1	0	$\rightarrow Q_3 Q_0$
5	0	1	1	1	$\rightarrow \bar{Q}_3 Q_2$
6	0	0	1	1	$\rightarrow \bar{Q}_3 Q_1$
7	0	0	0	1	$\rightarrow \bar{Q}_1 Q_0$
8	0	0	0	0	

⇒ In Johnson counter to decode each state one two I/p. AND/NOR gate used.

Disadvantage:

⇒ lock out may occur. (when counter enter into unused state)

Note:- In synchronous counter propagation delay of each counter is t_{pdff} . then,


$$T_{clk} \geq t_{pdff}$$

$$t_{clk} \leq \frac{1}{t_{pdff}}$$

$$f_{max} = \frac{1}{t_{pdff}}$$

In synchronous counter.

(A) Synchronous Series carry counter :-

 

ii) Explanation :-

- ⇒ ckt shown in fig. is Synchronous series carry up counter.
- ⇒ In this counter Q_0 toggles for every clock pulse.
- ⇒ Q_1 toggles when $Q_0 = 1$ and clock is applied.
- ⇒ Q_2 toggles when $Q_1 = Q_0 = 1$ and clock applied.
- ⇒ Q_3 will toggle when $Q_2 = Q_1 = Q_0 = 1$ and clock applied.
- ⇒ This ckt may be down counter when $\bar{Q}$ is connected to T.

iii) Truth table :-

clock	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1


⇒ To provide down counter used $\bar{Q}$ a/p to provide next stage

S/p.

classmate

Stat.

5013

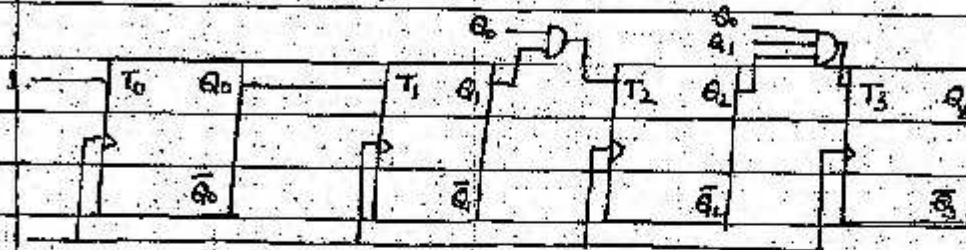


⇒ Disadvantage is increased I/p pin of AND Gate.

$$T_{CLK} \geq t_{ADFF} + t_{PQAND}$$

⇒ Ripple counter < Synchronous serial carry < Synchronous parallel carry counter for faster logic.

Synchronous counter design for the given sequence:-

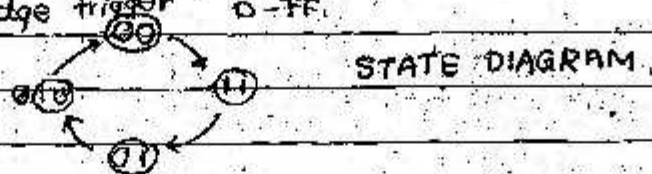
Problem: Design a Synchronous counter for the count sequence $0 \rightarrow 3 \rightarrow 1 \rightarrow 2 \rightarrow 0$
 Sol: Using +ive edge trigger D-FF.



Sol: Procedure :-

- (i) Identify no. of FF and I/p and o/p.
- (ii) construct state table.
- (iii) logical expression for I/p.
- (iv) Minimize.
- (v) Implement the ckt.

Now,

 

(ii) state table :-


Present state	Next state		
Q_1, Q_0	Q_1, Q_0	D_1	D_0
0 0	1 1	1	0 1
1 1	0 1	0	1
0 1	1 0	1	0
1 0	0 0	0	0

(iii) logical expression :-

$$D_1 = \bar{Q}_1 \bar{Q}_0 + \bar{Q}_1 Q_0 = \bar{Q}_1 (Q_0 + \bar{Q}_0) = \bar{Q}_1$$

$$D_0 = \bar{Q}_1 \bar{Q}_0 + Q_1 Q_0 = Q_1 \oplus Q_0 = Q_1 \oplus Q_0$$

iv Implementation :-


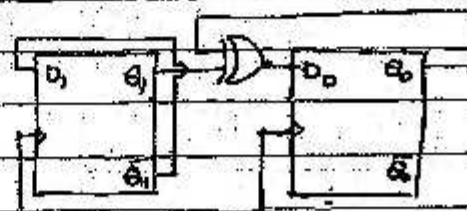


CLK

PAGE

Q: Design using T-FF 0-3-21-2-0

Sol: (i)

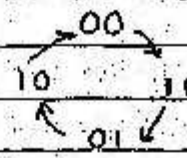 

(ii) state table


Q_1, Q_0	Q_{1+}, Q_{0+}	T_1	T_0
0 0	1 1	1	1
1 1	0 1	1	0
0 1	1 0	1	1
1 0	0 0	1	0

(iii) logical expression

$$T_1 = 1$$

$$T_0 = \bar{Q}_1 Q_0 + Q_1 \bar{Q}_0 = \bar{Q}_1$$

(iv) Implementation:-

 

Content:-

- ⇒ Various no. system.
- ⇒ Arithmetic operation.
 - complement
 - Add, sub.
- ⇒ Various codes.
- ⇒ Data representation.
 - unsigned
 - signed
 - signed magnitude
 - 1's
 - 2's

Number system and codes:-

↓
Weighted

- ⇒ Positional weighted
- e.g. Binary, octal
- Decimal, Hexadecimal
- BOD code.

↓
Unweighted

- ⇒ No weighted
- e.g. gray code, Excess-3 code

- ⇒ A number system with base or radix r contains r different digit and they are from $(0 - r-1)$.

e.g. $(101)_r$ $r =$ Base or radix.

Base

Different Digit

2

0, 1

8

0, ..., 7

10

0, ..., 9

12

0, ..., 9, A, B

16

0, ..., 9, A, B, C, D, E, F

4

0, ..., 3

6

0, 1, 2, 3, 4, 5

classmate.

PAGE

--	--	--

★ Conversion (Various number System):-

1. Decimal to others:-

⇒ To convert decimal no. into any other base r divide integer part multiply fractional part with r .

e.g.

Q:- Convert $(25.625)_{10} \rightarrow (-)_{2}$

Sol:-

$$\begin{array}{r|l} 2 & 25 \\ \hline 2 & 12 - 1 \uparrow \\ 2 & 6 - 0 \\ 2 & 3 - 0 \\ 2 & 1 - 1 \\ 2 & 0 - 1 \end{array}$$

$$0.625 \times 2 = 1.25 = 1$$

$$0.25 \times 2 = 0.50 = 0$$

$$0.5 \times 2 = 1.0 = 1 \downarrow$$

Ans:- $(11001.101)_2$

Q:- Convert $(25.625) \rightarrow (-)_8$

Sol:-

$$\begin{array}{r|l} 8 & 25 \\ \hline 8 & 3 - 1 \uparrow \\ 8 & 0 - 3 \end{array}$$

$$0.625 \times 8 = 5$$

Ans:- $(31.5)_8$

⇒ When we go from higher to lower base the no. is increased.

Q:- Convert $(25.625)_{10} \rightarrow (-)_{16}$

Sol:-

$$\begin{array}{r|l} 16 & 25 \\ \hline 16 & 1 - 9 \uparrow \\ 16 & 0 - 1 \end{array}$$

$$0.625 \times 16 = 10 = A$$

Ans:- $(19.A)_{16}$

Q:- Convert $(254)_{16} \rightarrow (-)_{16}$

Sol:-

$$\begin{array}{r|l} 16 & 254 \\ \hline 16 & 15 - 14 = E \uparrow \\ 16 & 0 - 15 = F \end{array}$$

= $(FE)_{16}$

Q1. Convert $(27.4)_{10} = (-)_{4}$

Sol.

$$\begin{array}{r} 4 \overline{) 27} \\ 4 \overline{) 8-3} \\ 5 \overline{) 1-2} \\ 0-1 \end{array}$$

$$\begin{array}{l} 0.4 \times 4 = 1.6 = 1 \\ 0.6 \times 4 = 2.4 = 2 \\ 0.4 \times 4 = 1.6 = 1 \end{array}$$

Ans:- $(123.123)_4$

2. Others to Decimal :-

$$(X_1 X_2 X_3 \dots Y_1 Y_2)_r = (-)_{10}$$

⇒ To convert any other base r to decimal multiply each digit with positional weighted then add.

then,

$$(-)_{10} = X_1 r^2 + X_2 r^1 + X_3 r^0 + Y_1 r^{-1} + Y_2 r^{-2}$$

Q1. Convert $(10101.11)_2 = (-)_{10}$

Sol.

$$1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 1 \times 2^{-2}$$

$$= 16 + 4 + 1 + \frac{1}{2} + \frac{1}{4}$$

$$= \frac{64 + 16 + 4 + 2 + 1}{4} = \frac{87}{4} = (21.75)_{10}$$

Q2. Convert $(57.4)_8 = (-)_{10}$

Sol.

$$5 \times 8^1 + 7 \times 8^0 + 4 \times 8^{-1}$$

$$= 40 + 7 + \frac{4}{8} = \frac{320 + 56 + 4}{8} = \frac{380}{8}$$

$$= 47.5 = (47.5)_{810}$$

Q3. Convert $(57.4)_{16} = (-)_{10}$

Sol.

$$5 \times 16 + 7 + \frac{4}{16} = 87 + 0.25 = (87.25)_{10}$$

Q4. Convert $(BAD)_{16} = (-)_{10}$

Sol.

$$11 \times 16^2 + 10 \times 16 + 13$$

$$= 256 \times 11 + 160 + 13$$

$$= 2816 + 160 + 13 = (2989)_{10}$$

Q:- convert $(35)_6 = (-)_{10}$
 Sol:- $3 \times 6 + 5 \times 1 = 18 + 5 = (23)_{10}$

3. Octal to Binary & Binary to Octal:-

$(xyz)_8 = (-)_2$

→ each no. is represent by its 3 bit binary formate.

Ques:- convert $(37.45)_8 = (-)_2$

Sol:- $(011111.100101)_2$

Binary to octal:-

Ques:- convert $(10110.11)_2$

Sol:- $(010110.110)_2$
 $= (26.6)_8$

4. Hexadecimal to Binary and Binary to Hexadecimal:-


→ Each digit is represent by 4 bit binary.

Ques:- convert $(259A)_{16} = (-)_2$

Sol:- $(0010010110011010)_2$

 5. Hexadecimal to octal or octal to Hexa:-

for Hexa $\longleftrightarrow$ Octadecimal



Q:- convert $(CAD)_{16} = (-)_8$

Sol:- $(CAD)_{16}$
 $= (110010101101)_2$
 $= (6255)_8$