

Roll No. ....

**24004**

**B. Tech 1st Semester  
(Common for All Branches)  
Examination – December, 2017**

**BASICS OF ELECTRONICS**

**Paper : ECE-101-F**

**Time : Three Hours ]**

**[ Maximum Marks : 100**

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** Attempt five questions in all, selecting at least *one* question from each Section. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (a) What is barkhausen criteria for oscillations?  
 $5 \times 4 = 20$
- (b) Why LED's emit light of different colours ?
- (c) What is ideal diode ? Write down diode equation.
- (d) What is flip-flop ?
- (e) Give truth table of OR gate.

24004-7050-(P-3)(Q-9)(17)

P. T. O.

**SECTION - A**

2. What is semiconductor ? Explain with its types. Why we prefer Si instead of Ge ? 20
3. Explain the terminal characteristics of PN Junction diode and compare it with ideal diode characteristics. 20

**SECTION - B**

4. (a) Write short note on SMPS. 10  
(b) Explain working of Wein Bridge oscillators. 10
5. (a) Discuss characteristics of an ideal op-amp. 10  
(b) Explain block diagram of op-amp. 10

**SECTION - C**

6. Explain function Generator with the help of block diagram. 20

7. (a) Differentiate combinational and sequential circuit. 10

- (b) What are Universal Gates ? Explain. 10

**SECTION - D**

8. (a) Explain different types of segment displays. 10  
(b) What is LED ? Discuss its construction and working. Give its advantages and disadvantages. 10

24004-7050-(P-3)(Q-9)(17) ( 2 )

9. Write short notes on :

- (a) SR flip-flop  
(b) Voltage Regulator

10 × 2 = 20

24004-7050-(P-3)(Q-9)(17) ( 3 )