

**SECTION – D**

6. Define voltage regulation. Derive the equation for voltage regulation of 1- $\phi$  transformer at inductive load. 20
7. Derive the equation for power in 3- $\phi$  star connected system. 20

**SECTION – E**

8. Draw and explain the constructional features of 3- $\phi$  induction motors. 20
9. Explain the construction and working principle of electro-dynamometer type Wattmeter. 20

24007-14250-(P-4)(Q-9)(17) (4)

Roll No. ....

**24007**

**B. Tech. 2nd Semester (Common for all Branches) Examination – May, 2017**

**ELECTRICAL TECHNOLOGY**

Paper : EE-101-F

*Time : Three Hours ]*

*[ Maximum Marks : 100*

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** (i) Attempt *five* questions in total.

(ii) Question No. 1 is *compulsory*.

(iii) Attempt *four* more questions from remaining *four* Sections (B, C, D & E) by selecting at least *one* question from each Section.

**SECTION – A**

1. (a) Describe how the direction of induced e. m. f. can be determined. 5

24007-14250-(P-4)(Q-9)(17)

P. T. O.

(b) Define :

- (i) Periodic function
  - (ii) cycle
  - (iii) time period of a sinusoidal signal
- (c) Derive e.m.f. equation of 1- $\phi$  transformer. 5
- (d) Derive e.m.f. equation of D. C. generator. 5

**SECTION - B**

2. Solve the circuit given below by using Nodal analysis :




and find the value of current flowing through  $4\Omega$  resistance.

24007-14250-(P-4)(Q-9)(17) (2)

20

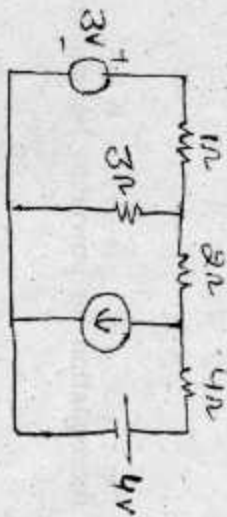3. State and explain super position theorem. Find the value of current flowing through  $3\Omega$  resistance in the given circuit by using Norton's theorem : 20



**SECTION - C**

4. A  $10\Omega$  resistor is connected in series with a  $100\ \mu\text{F}$  capacitor to a  $230\ \text{V}$ ,  $50\ \text{Hz}$  supply. Find : 20

- (a) Impedance
- (b) Current
- (c) Power factor
- (d) Phase angle
- (e) voltage across the resistor and capacitor

5. State and explain Resonance in RLC series circuit. Differentiate between Acceptor and Rejctor circuits. 20

24007-14250-(P-4)(Q-9)(17) (3)

P. T. O.