

Roll No.

06/01/11

Total No. of Page : 4

EEE- DEC 2010- 1

BT-1/DX: 8022

EL-101-E: Elements of Electronics Engineering

Time : Three Hours

Maximum Marks : 75

Note:- Attempt any FOUR questions, with at least ONE from each section A, B, C and D. Section E is compulsory.

SECTION-A

- Q.1. a) Explain the mechanisms of breakdown in p-n diodes. Describe the use of Zener diode as a voltage regulator. 7.5
- b) A specimen of intrinsic Germanium at 300 °K, having a concentration of carriers of $2.5 \times 10^{13} \text{ cm}^{-3}$ is doped with impurity atoms of one for every million germanium atoms. Assuming that all the impurity atoms are ionized and that the concentration of Ge atoms is $4.4 \times 10^{22} \text{ cm}^{-3}$, find the resistivity of doped material.

(μ_n for Ge is 3600 cm²/volt-sec). 7.5

- Q.2. a) Draw the circuit of a Full wave and bridge rectifier and centre tap transformer rectifiers, with the help of waveforms explain their operation.

Also discuss their diodes PIV values. 7.5


- b) What value of series resistance is required when 10W, 10V, 1000mA zener diodes are connected in series to obtain 20 V regulated output from a 35 V dc source? 7.5

SECTION-B

- Q.3. a) Define α of a transistor. Show that it is always less than unity. 7.5

Show that
$$\beta = \frac{\alpha}{1-\alpha}$$

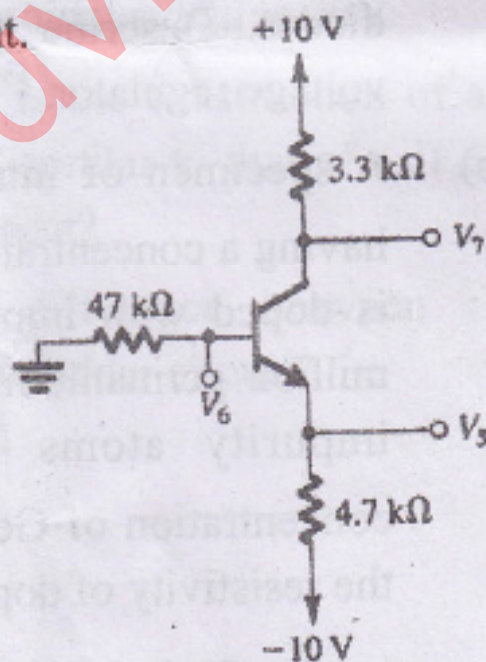- b) The transistor in the circuit of figure 1 has $\beta = 80$ exhibits a V_{BE} of 0.7V. Find all the terminal voltage and current. 7.5



- Q.4. a) Explain the working of a transistor as a switch. 5
- b) Draw the various basing circuits and explain their operations. Calculate the stability factor in each case. Why emitter divider bias is better than the two other techniques. 7.5

SECTION-C

- Q.5. a) An amplifier with open loop voltage gain $A_v = 1000 \pm 100$ is available. It is necessary to have an amplifier whose voltage gain varies by no more than 0.1%. Find the reverse transmission factor β of the feedback network used. 7.5
- b) Discuss IC741 with its complete pin diagram. 7.5
- Q.6. a) Draw the circuit of OPAMP as following and derive its output in case of its use as
- Scale changer
 - Differentiator
 - Draw the inverting and non-inverting amplifier circuits of an Opamp in closed loop configurations. Obtain an expression for closed loop gain in these circuits.

SECTION-D

- Q.7. a) Prove that the transconductance g_m of a JFET is given by

$$g_m = \frac{2}{|V_P|} \sqrt{I_{DS} I_{DSS}}$$

Where V_P = Pinch off voltage, I_{DS} = Drain current
 I_{DSS} = Maximum value of I_{DS} corresponding to $V_{GS} = 0$ volts. 7.5

- b) Discuss how JFET acts as a voltage amplifier. Draw the waveforms. 10

- Q.8. a) Explain the working relaxation oscillator using UJT. 5
- b) Explain the working of a digital CRO with the help of a block diagram. 10

SECTION-E

6. Draw Energy band diagram of p-n junction at equilibrium, forward bias condition and reverse bias condition. 3
7. How can you check the polarity of the diode, if the mark on its body is rubbed off or not visible? 3
8. Sketch a circuit that will clip all levels of a sinusoidal signal above-5V. The peak to peak voltage of sinusoidal signal is 20V 3
9. IN what ways is the construction of a depletion-type MOSFET similar to that of a JFET? In what ways is it different? 3
10. What is the difference between a summing amplifier and an adder circuit? 3