

**BT-1/D11**

**7520**

**Elements of Electronics Engineering (New)**

**Paper : EL-101 E**

Time : Three Hours]

[Maximum Marks : 75

**Note :-** Attempt **FIVE** questions, selecting at least **ONE** from each Unit.  
Question 9 is compulsory.

**UNIT-I**

1. (a) Explain the importance of PIV in rectifiers. 2
- (b) Draw the circuit of Bridge wave rectifier and explain its working with the help of waveforms. What are its advantages over centre tapped Rectifier ? 10
- (c) Discuss the operation of varactor diode. 3
2. (a) Explain the working of Zener diode as voltage regulator. 5
- (b) What do you understand by waveshaping circuits ? Discuss various waveshaping circuits used for clipping of signals ? 8
- (c) Define drift current and diffusion current in p-n junction. 2

**UNIT-II**

3. (a) Explain why transistor action cannot be achieved by connecting two diodes back to back ? 3
- (b) Sketch typical CB input and output characteristics of NPN transistor. Indicate all the operation regions and explain the characteristics qualitatively. 8
- (c) Differentiate between CE, CC and CB configurations in terms

(b) Differentiate between positive and negative feedback. What are the advantages of negative feedback in Amplifier? Explain briefly. 10

### UNIT-III

5. (a) Explain :
- (i) CMRR
  - (ii) Input offset voltage
  - (iii) Slew rate
  - (iv) PSRR. 6
- (b) Draw the equivalent circuit of op-amp. Explain its transfer characteristics. 5
- (c) Write a short note on Transducers. 4
6. (a) Draw the circuit of differential Amplifier. Derive the relation between CMRR and  $V_{out}$  of op-amp. Under what conditions CMRR may be maximized? 10
- (b) Discuss how op-amp acts as differentiator. 5

### UNIT-IV

7. (a) Explain the working of JFET as an amplifier in CS configuration. 6
- (b) How UJT acts as relaxation Oscillator? 5
- (c) Define following with reference to JFET-
- (i) Depletion region
  - (ii) Pinch off voltage
  - (iv) Drain. 4

8. (a) Explain with help of Block Diagram, various functions of CRO.  
Also discuss its various applications. 7½

(b) Explain construction, working and characteristics of TRIAC. 7½

**(Compulsory Question)**

9. (i) Define current controlled and voltage controlled device.  
(ii) Differentiate between Zener and Advalanche breakdown.  
(iii) Draw Transfer Characteristics of MOSFET.  
(iv) Why FET is unipolar device ?  
(v) Define early effect.  
(vi) What are active and passive components ? Give few examples.  
(vii) Draw frequency response of RC coupled Amplifier.  
(viii) What is Barkhausen criterion in Oscillator ?  
(ix) Draw pin diagram of 741.  
(x) How does (LED) emit light ? 1.5×10=15