

Time Allowed: 3 Hours]

[Maximum Marks: 100

**Note:** Attempt **five** questions in all, selecting at least **one** question from each Section.

**SECTION-I**

1. (a) Differentiate between :
- (i) Digital Signal and Analog Signal
  - (ii) XOR gate and XNOR gate. 6
- (b) Convert  $(0.65625)_{10}$  to binary. 4
- (c) What are the important characteristics of Gray code? 4
- (d) Express the following BCD numbers in
- (i) Straight binary form and (ii) Excess-3 code.
- 10010011, 01100111. 6
2. (a) Realize or implement the following Boolean expression using basic gates:
- $$Y = \overline{AC} + \overline{BC} + BC + AC$$
- 6
- (b) Minimize the following Logic function and realize using NOR gates:
- $$F(A, B, C, D) = \pi M(1, 2, 3, 8, 9, 10, 11, 14) \cdot d(7, 15).$$
- 8
- (c) How is QM method of simplification different from K-map method? 6

**SECTION-II**

3. (a) Realize full subtractor using NAND gates only, if  $I/P$ 's A, B and  $b_i$  are available in complemented. 6
- (b) Implement the following Boolean function using 8 : 1 multiplexer :
- $$F(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + \sum d(3, 8, 14)$$
- 8
- (c) Draw common anode and common cathode circuits of LED seven segment display and bring out the difference between them. 6
4. (a) Draw and explain working of a positive edge triggered J-K flip flop. Also explain the race around problem. 7
- (b) Discuss the application of Shift registers. 5
- (c) Design a synchronous counter with the following sequence:
- $$0001 \rightarrow 0011 \rightarrow 0101 \rightarrow 0111 \rightarrow 1001 \rightarrow 1011 \rightarrow 1101 \rightarrow 1111 \rightarrow 0001 \dots\dots$$
- 8

### SECTION-III

5. (a) Discuss the switching mode operation of p-n junction. 7  
(b) Explain the parameters used to characterize logic families. 7  
(c) How fan out is increased in DTL? Justify your answer. 6
6. (a) What is interfacing? What are the different schemes for CMOS and TTL interface? Explain one of them. 10  
(b) Compare CMOS and TTL families. 5  
(c) What are the applications of open collector output? 5

### SECTION-IV

7. (a) What are the disadvantages of weighted register DAC? 6  
(b) Explain the important specifications of DAC. 6  
(c) An 8 bit ADC accepts an input voltage 0 to 10 V  
(i) What I/P voltage will cause all 1's at the ADC output?  
(ii) What is the digital output code, if the applied I/P voltage is 5.2V? 8
8. (a) What is meant by the term 'architecture of PLD' ? Give some suitable examples. 8  
(b) Discuss the applications of PLAs. 5  
(c) What is programmable array logic? How does it differ from ROM? 7