# EMI-2010-1

Roll No. .....

Total No. of Pages: 3

### BT-4/JX

8314

## **Electronics Instrumentation and Measurements**

Paper: ECE-202E

Time: Three Hours]

[Maximum Marks: 100

Note: Attempt any FIVE questions, selecting at least ONE question from each Unit.

#### UNIT-I

- (a) Distinguish between static and dynamic characteristics of a measuring system. Define these characteristics and state the relevance of each in a measuring process.
  - (b) Compute the maximum percentage errors in the sum and difference of two voltage measurements when  $V_1 = 100$  V  $\pm$  1% and  $V_2 = 80$  V  $\pm$  5%.
- (a) Draw the circuit of a Kelvin bridge, explain its operation, and derive the equation for unknown resistance.
  - (b) Draw a circuit diagram to show how the insulation resistance of a cable should be measured?

### UNIT-II

(a) Sketch the circuit diagram of Hay inductance bridge. Derive
the equations for the resistive and inductive components of the
measured inductor. Discuss various applications of the Maxwell
and Hay bridges.

## EMI-2010-2

- (b) A Maxwell inductance bridge uses a standard capacitor of  $C_3 = 0.1 \,\mu\text{F}$  and operate at a supply frequency of 100 Hz. Balance is achieved when  $R_1 = 1.26 \, \text{k}\Omega$ ,  $R_3 = 470 \, \Omega$ , and  $R_4 = 500 \, \Omega$ . Calculate the inductance and resistance of measured inductor, and determine its Q factor.
- 4. (a) Sketch the circuit of an ac electronic voltmeter using a voltage-to-current converter with full wave rectification. Explain the operation of the circuit.
  - (b) Sketch the oscilloscope display that occurs with sine wave horizontal and vertical inputs that (i) are in phase, (ii) are in antiphase, (iii) have a phase difference of 90°, and (iv) have a phase difference greater than zero but less than 90°.

#### UNIT-III

- (a) Sketch the block diagram for a swept super-heterodyne spectrum analyzer. Explain the system operation.
  - (b) A 20 V dc voltage is measured by analog and digital multimeters. The analog instrument is on its 25 V range, and its specified accuracy is ±2%. The digital-meter has a 3½ digit display and an accuracy of ±(0.6+1). Determine the measurement accuracy in each case.
- Define dual slope integrator and zero-crossing detector. Sketch the block diagram and system waveforms for a digital voltmeter that uses a dual-slope integrator. Explain how it operates, and discuss the advantages of the dual-slope system.

### UNIT-IV

 (a) What are the transducer selection parameters? Describe the operation of piezoelectric transducer for pressure measurement.

# EMI-2010-3

- (b) For a certain thermistor,  $\beta = 3140$  K and the resistance at 27°C is known to be 1050  $\Omega$ . The thermistor is used for temperature measurement and the resistance measured is as 2330  $\Omega$ . Find the measured temperature.
- (a) Describe the various stages of a FDM system and a TDM system, by means of block diagrams and explain the function of each stage.
  - (b) What are the important characteristics of a telemetry system and distinguish the criteria on which the telemetry and communication systems are based?