



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**BTECH**  
**(SEM I) THEORY EXAMINATION 2021-22**  
**BASIC ELECTRICAL ENGG**

**Time: 3 Hours****Total Marks: 70****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 7 = 14**

a.	Compare active and passive elements with examples.	BL-2
b.	Determine the form factor and peak factor of pure sine wave voltage of 220 Volt.	BL-3
c.	Why series resonant circuit is known as acceptor circuit & parallel resonant circuit as rejecter circuit?	BL-1
d.	What the relationship between line and phase, voltage and current for a 3- $\Phi$ star connected balanced system?	BL-2
e.	What is the condition of maximum efficiency of single transformer?	BL-1
f.	Write the applications of split ring and brush in DC machines.	BL-1
g.	A 3-phase 440 V, 50 Hz induction motor has a 4% slip. What will be the frequency of the rotor current?	BL-3

**SECTION B****2. Attempt any three of the following:****7 x 3 = 21**

a.	Find the current in $8\Omega$ resistance using nodal analysis.	BL-3
b.	Explain series resonance in R-L-C circuit. A series R-L-C circuit has $R=10\Omega$ , $L=0.1\text{H}$ and $C=8\mu\text{F}$ . Determine (i) resonant frequency (ii) Q factor of the circuit at resonance (iii) the half power frequencies.	BL-4
c.	Find the relationship between line and phase, voltage and current for a 3- $\Phi$ delta connected balanced system. A balanced 3-Phase star connected load takes 30KW at a leading current of 48A from a 3- $\phi$ source of 500V, 50Hz. Find the circuit parameters per phase.	BL-4
d.	Establish the analogy between electric circuit and magnetic circuit.	BL-5
e.	Draw and explain the torque-slip characteristics of a 3- $\Phi$ induction motor indicating the starting torque, the maximum torque and operating region.	BL-4

**SECTION C****3. Attempt any one part of the following:****7 x 1 = 7**


(a)	Formulate the average value, rms value & form factor and peak factor of half wave rectified alternating current having maximum value of 100 A.	BL-5
(b)	Using mesh analysis, find the current through $6\Omega$ resistances in the following circuit.	BL-3



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--


**BTECH**  
**(SEM I) THEORY EXAMINATION 2021-22**  
**BASIC ELECTRICAL ENGG**

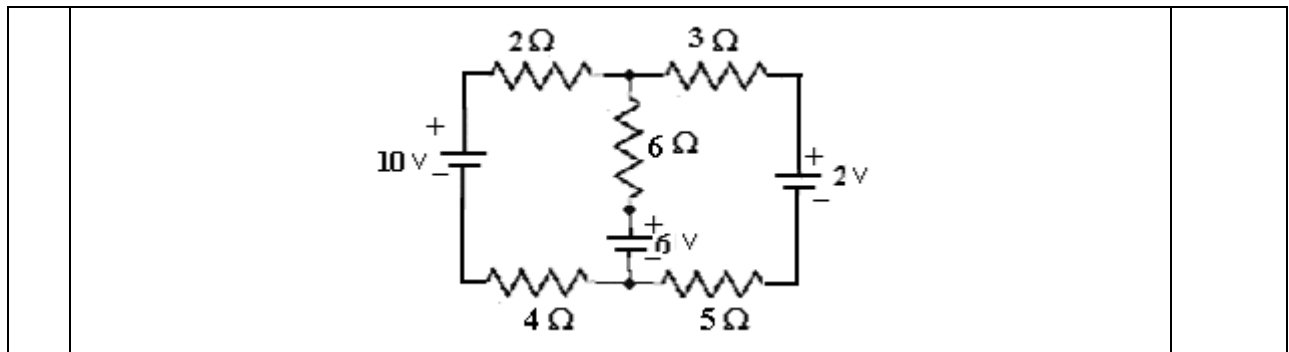

4. Attempt any one part of the following:

7 x 1 = 7

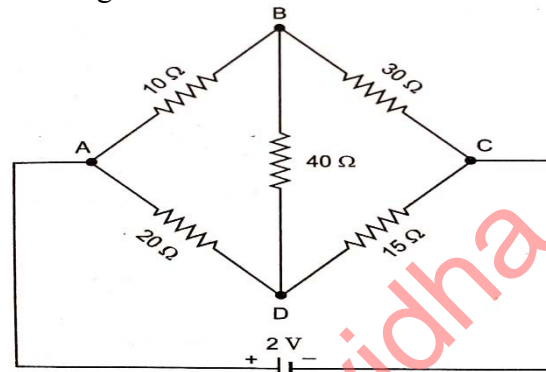- (a) State and Explain Thevenin's theorem and find the current in 40 Ω resistance in the following network using Thevenin's theorem.



BL-4

- (b) Explain the causes of low power factor. What are the disadvantages of low power factor? Explain any two methods to improve the power factor.

BL-2

5. Attempt any one part of the following:

7 x 1 = 7

- (a) A balanced star connected load of  $(8 + j6) \Omega$  per phase is connected to a balanced 3-phase, 400 V supply. Find the line current, phase current, power factor, power and total volt-amperes.

BL-3

- (b) Explain the construction details and working of a Permanent magnet moving coil PMMC instruments along with the deflecting torque and controlling torque.

BL-2

6. Attempt any one part of the following:

7 x 1 = 7

- (a) Explain the working principle and emf equation of transformer. A 40 KVA transformer has iron loss of 450W and full load copper loss of 850W. if the power factor of the load is 0.8 lagging, calculate:
- Full load efficiency
  - The load at which the maximum efficiency occurs and
  - The maximum efficiency.

BL-4

- (b) Explain single phase auto transformer and give its advantages over two winding transformers. Mention the various applications of auto transformer.

BL-2

7. Attempt any one part of the following:

7 x 1 = 7

- (a) Why synchronous motor is not self-starting? Discuss any two methods to start the synchronous motor. What are the various applications of synchronous motor?

BL-5

- (b) (i) Why 1- $\Phi$  induction motor is not self-starting? Discuss any one method of starting.  
(ii) A 250 V dc shunt motor takes 41 A at full load. Armature resistance and shunt field winding resistances are 0.1  $\Omega$  and 250  $\Omega$  respectively. Find the back emf on full load.

BL-3