



Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2021-22
ELECTRONICS ENGINEERING

Time: 3 Hours**Total Marks: 100****Note: 1.** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A****1. Attempt all questions in brief.****2 x 10 = 20**

Q no.	Question	Marks	CO
a.	What you mean by Doping. Describe its need.	2	CO-1
b.	Why Si is preferred as compared to Ge in Semiconductor Electronics.	2	CO-1
c.	Differentiate between Clipper and Clamper circuit.	2	CO-2
d.	Compare LED and photo diode.	2	CO-2
e.	State two Difference between BJT and FET.	2	CO-3
f.	Define Threshold Voltage for an E-MOSFET. Also define V_{th} for an JFET.	2	CO-3
g.	What is unity gain amplifier(buffer)?	2	CO-4
h.	What is SLEW RATE explain briefly?	2	CO-4
i.	Compare analog and digital instruments.	2	CO-5
j.	Write the applications of CRO.	2	CO-5

SECTION B**2. Attempt any three of the following:**

Q no.	Question	Marks	CO
a.	Explain Avalanche and Zener Breakdown Mechanism.	10	CO-1
b.	Write a short note on Tunnel and Varactor Diode.	10	CO-2
c.	Draw the basic structure of Common Base BJT and explain its principle of operation with neat diagram with its input and output characteristics.	10	CO-3
d.	Define Op-Amp with the help of block diagram. List the 10 ideal characteristic of an Op-Amp. Explain working of Op-Amp as a Adder.	10	CO-4
e.	Draw and explain the block diagram of Digital Storage Oscilloscope (DSO) also compare it with analog oscilloscope.	10	CO-5

SECTION C**3. Attempt any one part of the following:**

Q no.	Question	Marks	CO
a.	Draw the V-I characteristics of an ideal & practical diode and explain. Also write the diode equation in support of your answer	10	CO-1
b.	What do you mean by diode resistances? Draw and explain the characteristics of transition and diffusion capacitance v/s applied voltage.	10	CO-1

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2021-22
ELECTRONICS ENGINEERING**4. Attempt any one part of the following:**

Q no.	Question	Mark s	CO
a.	Determine I_Z , I_L , I_R and V_L for the network shown in given fig. <div style="text-align: center; margin-top: 10px;"> </div>	10	CO-2
b.	Determine the output waveform for a given input waveform <div style="display: flex; justify-content: space-around; align-items: center; margin-top: 10px;"> <div style="text-align: center;"> </div> <div style="text-align: center;"> </div> </div>	10	CO-3

5. Attempt any one part of the following:

Q no.	Question	Marks	CO
a.	Distinguish between enhancement type and depletion type MOSFETs. Draw the cross-section of N-channel enhancement MOSFET. Explain and draw the transfer characteristics.	10	CO-4
b.	Describe the construction of a NPN transistor. Define α and β with respect to BJT and derive the relationship between them.	10	CO-4

6. Attempt any one part of the following:


Q no.	Question	Marks	CO
a.	Explain the concept of Virtual ground. Explain working of Op-Amp as a differentiator.	10	CO-5
b.	Determine the output of following Circuits (i)	10	CO-5



Roll No:

--	--	--	--	--	--	--	--	--	--	--

BTECH
(SEM III) THEORY EXAMINATION 2021-22
ELECTRONICS ENGINEERING

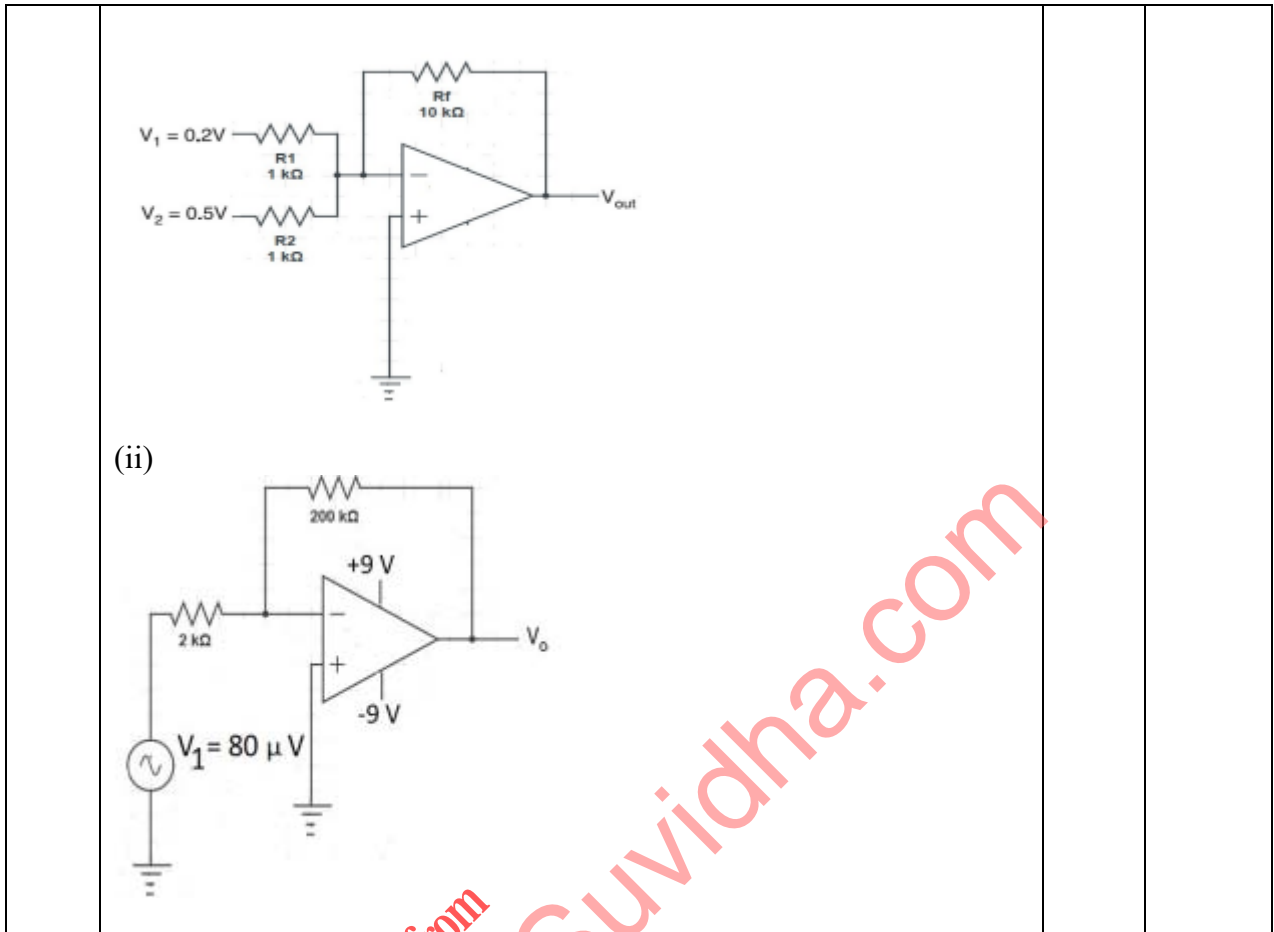

7. Attempt any *one* part of the following:

Q no.	Question	Marks	CO
a.	Describe measurement of Voltage, Frequency & Phase using CRO.	10	CO-1
b.	Describe the working of Digital Multimeter with their block diagram.	10	CO-1