

**B.TECH****(SEM IV) THEORY EXAMINATION 2022-23  
ELECTRONICS ENGINEERING****Time: 3 Hours****Total Marks: 100****Note:** Attempt all Sections. If require any missing data; then choose suitably.**SECTION A**

- 1. Attempt all questions in brief. 2 x 10 = 20**
- Breakdown voltage of a zener diode is 10V. It can dissipate a maximum power of 350 mW. Determine the maximum current the diode can handle?
  - What you mean by Doping.
  - Explain the principle of operation of LED.
  - What is meant by voltage multiplier?
  - Define Threshold Voltage for an E-MOSFET.
  - Define transconductance of JFET.
  - Explain the concept of Virtual ground in an OPAMP.
  - Draw the structure of Integrator using OP-AMP.
  - What are the applications of CRO?
  - For what purpose, digital multimeter are used?

**SECTION B**


- 2. Attempt any three of the following: 10 x 3 = 30**
- Draw & explain the V-I characteristic of a P-N junction diode. Also describe the effect of Temperature on the V-I characteristic of a P-N junction diode.
  - Explain principle of operation and construction of Varacter diode. Draw its V-I characteristic.
  - With help of a well labeled diagram, discuss input and output characteristics of a bipolar junction transistor in common base configuration. Also indicate all the regions of operation
  - Explain unity gain OPAMP. With suitable circuit diagram obtain the expression for integrator and differentiator OPAMP.
  - Draw and explain the block diagram of Ramp type digital voltmeter. Also draw related voltage to time conversion waveforms

**SECTION C**

- 3. Attempt any one part of the following: 10 x 1 = 10**
- Explain how a barrier potential is developed at the P-N junction
  - Draw and explain the circuit diagram for negative and positive clamper circuits with input and output waveforms.
- 4. Attempt any one part of the following: 10 x 1 = 10**
- Explain principle of operation and construction of Tunnel diode. Draw its V-I characteristic.
  - Draw the circuit and discuss the working of full wave bridge rectifier with suitable input -output waveforms. What is PIV of bridge rectifier?

5. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) Draw the circuit of transistor in the CE configuration. Sketch the output characteristic. Indicate the Active, saturation region and cut-off region. Explain each region in detail.
  - (b) Draw and explain the construction and working of p-channel depletion type MOSFET. Also draw the characteristics of p-channel depletion type MOSFET.

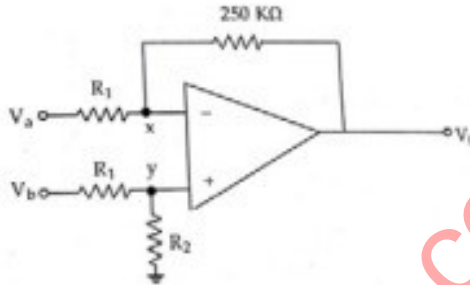6. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) For the op-amp shown in figure , find the values of  $R_1$  and  $R_2$  for the output to be  $V_0 = -5V_a + 3V_b$



- (b) Explain the non-inverting summing amplifier with circuit diagram.

7. **Attempt any one part of the following:** **10 x 1 = 10**
- (a) Describe the operation of CRT with neat block diagram. How unknown frequency is measured using CRO?
  - (b) Compare DSO with analog oscilloscope.