

**M.TECH
(SEM I) THEORY EXAMINATION 2022-23
RF CIRCUIT DESIGN**

Time: 3 Hours

Total Marks: 70

Note: Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt *all* questions in brief. 2 x 7 = 14
- What is SOC
 - What are mm range of frequency
 - What is insertion loss in RF circuit
 - What is SWR
 - What is condition for sustained oscillation
 - What is low noise amplifier
 - What is coupling and isolation

SECTION B

2. Attempt any *three* of the following: 7 x 3 = 21
- Explain sensitivity and dynamic range with respect to RF receiver
 - What is significance of Scattering parameters
 - Explain Multistage large signal amplifier design
 - Explain one diode mixer? Illustrate with an example
 - How impedance matching is achieved through Quarter Wave transformer $\lambda/4$

SECTION C

3. Attempt any *one* part of the following: 7 x 1 = 7
- Explain tuned resonant circuit?
 - Find the high frequency impedance behavior of a 500 Ω with 2.5cm copper wire construction of AWG 26 and a stray capacitances $C_a=5\text{pF}$
4. Attempt any *one* part of the following: 7 x 1 = 7
- Design of a 18dB single stage MESFET amplifier operated at 5.7GHZ
 - Explain how signal distortion can be overcome through amplifier design
5. Attempt any *one* part of the following: 7 x 1 = 7
- For a 200Mhz a Colpitts BJT oscillator in CE configuration. For the bias point of $V_{CE}=3\text{V}$ and $I_C=3\text{mA}$, $C_{BC}=0.1\text{fF}$, $r_{BE}=2\text{k}$, $r_{CE}=10\text{k}\Omega$, $C_{BE}=100\text{fF}$. Inductance should not exceed 50nH. Find the value of capacitance in feedback loop
 - Explain Dielectric Resonant oscillator?
6. Attempt any *one* part of the following: 7 x 1 = 7
- What is mixer in RF networks? Design a mixer for conversion loss for SSB mixers
 - What is smith chart? What is its practical implementation in RF design
7. Attempt any *one* part of the following: 7 x 1 = 7
- Explain design rules for a matching using L networks? Why matching is so important in RF circuit design
 - Explain what is four port network? What is a circulator