

[This question paper contains 4 printed pages]

Your Roll No. :

Sl. No. of Q. Paper : **2444** IC

Unique Paper Code : 32223903

Name of the Course : **B.Sc. (Prog.) : SEC**

Name of the Paper : Electrical Circuits and
Network Skills

Semester : VI

Time : 3 Hours

Maximum Marks : 50

Instructions for Candidates :

- (a) Write your Roll No. on the top immediately on receipt of this question paper.
- (b) Attempt **five** questions in **all**.
- (c) Question **NO. 1** is compulsory.
- (d) **All** questions carry equal marks.

1. Attempt any **five** :

2,2,2,2,2

- (i) Explain Ohm's law with examples.
- (ii) Discuss about different type of conductors.

P.T.O.

- (iii) Draw the circuit diagram of a practical current source.
- (iv) Discuss about the phase reversal.
- (v) Draw the phasor diagram and waveform of voltage and current for a pure inductive circuit.
- (vi) Explain about the overload devices.
- (vii) The current through a $100\mu\text{F}$ capacitor is given below. Find the sinusoidal expression for voltage across the capacitor.

$$i = 40 \sin (500t + 60^\circ)$$

2. (a) Discuss in details about a digital multimeter. 5
- (b) Explain in details about single phase and three phase ac sources. 5
3. (a) Describe the construction and working of a transformer. 5

- (b) Describe the construction and working of an ac generator. Support your answer with relevant diagrams. 5
4. (a) State Thevenin's Theorem. 2
- (b) Mention the steps to Thevenize an electrical circuit. 2
- (c) In an electrical circuit with V_{th} as Thevenin equivalent voltage, R_{th} as Thevenin equivalent resistance, calculate the value of load resistance (R_L) to get the maximum power. Explain with circuit diagram. 2
- (d) In case of electrical symbols, show the symbols for phase shifter (3-wire), bridge rectifier, dc current source, and zener diode. 4
5. (a) Discuss the basic design and working of a three phase motor with relevant diagram. 6
- (b) Discuss the basic design and working of a dc motor with relevant diagram. 4

2444

6. Describe the construction and working of half-wave and full-wave rectifiers in details.

4,6

7. Write short notes on any **two** of the following :

5,5

(i) Solid and Stranded Cables.

(ii) Cable Trays.

(iii) Extension board.

(iv) Losses across cables and conductors