

Dr. Babasaheb Ambedkar Open University
Term End Examination July – 2021

Course	: BCA/DCA	Date	: 29-July-2021
Subject Code	: BCAN-203(NEW)/DCA-203	Time	: 01:00pm to 03:00pm
Subject Name	: Digital Electronics & Computer Organization	Duration	: 02 Hours
		Max. Marks	: 50

Section A

Answer the following (Attempt any two) (20)

1. Explain 9's complement and 10's complement
2. Explain 'binary coded decimal'.
3. Describe a working of ALU 74181
4. Describe a circuit diagram of DE Multiplexer

Section B

Answer the following (Attempt any three) (15)

1. Explain Binary Number System in detail.
2. $11001_2 = ?_{10}$
3. Explain Theorems governing Boolean Algebra
4. Explain 'Full Adder'.
5. Draw a circuit diagram for 'CLOCKED SET-RESET FLIP-FLOP'

Section C

Part – A (Multiple Choice Questions)

(10)

1. In Boolean algebra, the OR operation is performed by which properties?
A Associative properties B Commutative properties
C Distributive properties D All of the Mentioned
2. The representation of octal number $(532.2)_8$ in decimal is _____
A $(346.25)_{10}$ B $(532.864)_{10}$
C $(340.67)_{10}$ D $(531.668)_{10}$
3. According to Boolean law: $A + 1 = ?$
A 1 B A
C 0 D A'
4. The ALU gives the output of the operations and the output is stored in the _____
A Memory Devices B Registers
C Flags D Output Unit
5. The quantity of double word is _____
A 16 bits B 32 bits
C 4 bits D 8 bits
6. The weights used in Binary coded decimal code are:
A 2,1 B 6,4,2,1
C 8,4,2,1 D 4,2,1

- 7 Which of the following can be represented for decoder?
A Combinational circuit B Sequential circuit
C Logical circuit D None of the mentioned
- 8 The truth table for an S-R flip-flop has how many VALID entries?
A 1 B 2
C 3 D 4
- 9 Invalid BCD can be made to valid BCD by adding with _____
A 0101 B 0111
C 0110 D 1001
- 10 Which of the following is correct for a gated D-type flip-flop?
A The Q output is either SET or B The output complement follows the
RESET as soon as the D input goes input when enabled
HIGH or LOW
C Only one of the inputs can be D The output toggles if one of the
HIGH at a time inputs is held HIGH

Part – B (Do as Directed)

(05)

State whether the following statement are True or False

- 1 A ripple counter is an asynchronous counter.
- 2 Bidirectional shift registers can shift data either right or left.
- 3 BCD arithmetic is performed using base 10 numbers.
- 4 The S-R flip-flop has no invalid or unused state.
- 5 Edge-triggered J-K flip-flops make it hard for design engineers to know when to accept input data.
