

**GUJARAT TECHNOLOGICAL UNIVERSITY****BE - SEMESTER– III (New) EXAMINATION – WINTER 2019****Subject Code: 2131004****Date: 3/12/2019****Subject Name: Digital Electronics****Time: 02:30 PM TO 05:00 PM****Total Marks: 70****Instructions:**


1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.

**MARKS**

- Q.1 (a) Answer the following Questions: 03**
1. Find 2's Complement Representation of  $(-52)_{10}$ .
  2. Convert the binary number  $(1101110.0110)_2$  to decimal.
  3. For a given logic circuit, if  $A=B=1$ , and  $C=D=0$ . Find output Y.
- 
- (b) Minimize the following Boolean expression using Karnaugh Map (K-MAP) and Draw the draw the simplified logic circuit diagram. 04**
- $$Y = \sum m(0,1,5,9,13,14,15) + d(3,4,7,10,11)$$
- (c) Explain full subtractor and construct full subtractor using half subtractors. 07**
- Q.2 (a) Define Following Terms. 03**
1. Nibble
  2. Negative Logic
  3. Even Parity
- (b) Implement 16 X 1 multiplexer using 2 X 1 multiplexer. 04**
- (c) With a neat block diagram explain the function of encoder. Explain priority encoder? 07**
- OR**
- (c) Design a combinational logic circuit such that output is high, when four bit binary number is greater than  $(0110)_2$ . 07**
- Q.3 (a) Design 3-bit Binary to Gray code Converter. 03**
- (b) Explain 3-bit synchronous Binary Up counter with timing diagram. 04**
- (c) Explain T Flipflop with Excitation Table. Implement T flip flop using SR flip flop. 07**
- OR**
- Q.3 (a) Distinguish between combinational and Sequential logic circuits. 03**
- (b) Draw and Explain 4-bit bidirectional Shift Register. 04**
- (c) Differentiate the Asynchronous counter and Synchronous counter. Explain 3- bit up/down Asynchronous counter in detail. 07**
- Q.4 (a) State the advantages of Finite State Machine. 03**
- (b) Which are the various problems of Asynchronous Circuits? 04**

(c) Realize the sequential circuit for the state diagram shown in figure

07

 

OR

- Q.4** (a) Define State Table and State Diagram. 03  
(b) Describe General State Machine Architecture with suitable diagrams. 04  
(c) Explain the Fundamental Mode Model of ASM with Suitable example. 07

- Q.5** (a) Compare the Following in every aspect: TTL and CMOS 03  
(b) Explain oscillation problem of an asynchronous state machines with the help of one example. 04  
(c) Write short note on Programmable Logic Arrays. . 07

OR

- Q.5** (a) Define following terms with respect to Finite State Machine. 03  
1. Melay machine 2. Moore machine.  
(b) Draw and explain the working operation of 2- INPUT TTL NAND gate. 04  
(c) Compare ROM, PLA and PAL. 07

\*\*\*\*\*

downloaded from  
StudentSuvidha.com