

(T)

Roll No. ....

PAPER ID—14530

B.C.A. EXAMINATION, 2023

(First Semester)

LOGICAL ORGANIZATION OF  
COMPUTER-I

Code : SCA-104

Time : 3 Hours

Maximum Marks : 80

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

**Note :** Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. 1 is compulsory. All questions carry equal marks.

(023-3-09/23) T-14530

P.T.O.

1. Explain the following briefly :  $8 \times 2 = 16$

(i) EBCDIC codes

(ii) Venn Diagrams

(iii) Combinational circuits

(iv) Self-complementing codes

(v) Half adder

(vi) Encoder circuits

(vii) XOR gate

(viii) Canonical form of Boolean Expressions. . .

### Unit I

2. Solve the following number system conversions

(Attempt any *four*) :

$4 \times 4 = 16$

(i)  $(B2E)_{16} = (?)_2$

(ii)  $(5456)_8 = (?)_{16}$

(iii)  $(1110101101101)_2 = (?)_{10}$

(iv)  $(1527.362)_8 = (?)_2$

(v)  $(1046.25)_{10} = (?)_{16}$

(vi)  $(1011001110011.00110)_8 = (?)_8$

T-14530

2

3. Explain the following : 4×4=16
- (i) Error detecting codes
  - (ii) Hamming codes
  - (iii) Floating point representation
  - (iv) Binary subtraction using 2's Complement method.

### Unit II

4. (a) State and prove the following Boolean Algebra laws using examples : 4×2=8
- (i) Distributive Law
  - (ii) De Morgan's Law
- (b) Prove the following Boolean expressions using truth table : 4×2=8
- (i)  $AB + A'C + BC = AB + A'C$
  - (ii)  $ABC + AB'C + ABC' + AB'C' = A$ .

5. (a) Solve the following Boolean Expression using K-map : 6  
 $F(A, B, C, D) = \Sigma(0, 2, 3, 6, 7, 12, 13, 14) + \Sigma d(1, 4, 11, 15)$
- (b) Simplify the following expression using Boolean Algebra laws and also draw a circuit diagram for the minimized expression : 5  
 $X'Y'Z + XY'Z' + XY'Z + XYZ' + XYZ$
- (c) Explain SOP and POS forms of expression using example. 5

### Unit III

6. What are logic gates ? Explain the types of Logic Gates with their truth table as well as diagrams. 16
7. (a) Define Universal gates. Prove that NAND and NOR gates are universal gates. 8
- (b) Multilevel NAND and NOR Circuits. 4
- (c) Explain Combinational circuits and their characteristics. 4

#### Unit IV

8. Design and implement following digital circuits :
- (a) BCD to 7 Segment Display 8
  - (b) 5X32 decoder using 3X8 decoder. 8
9. (a) Design and implement a full adder circuit. 8
- (b) Define multiplexer circuits and its advantages. Also design a 4X1 MUX with block diagram and circuit. 8