

(T)

Roll No.

PAPER ID—13650

B. Sc. EXAMINATION, 2023

(First Semester)

COMPUTER SCIENCE

Code : 1.2

Computer Architecture

Time : 3 Hours

Maximum Marks : 40

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. 1 is compulsory. All questions carry equal marks.

1. (a) Write a short note on Multiplexers. 2
(b) What is a shift register ? 2

(S-D23-09/6) T-13650

P.T.O.

- (c) What is race around condition ? 2
(d) What is D flip-flop with truth table ? 2

Unit I

2. (a) Discuss Karnaugh simplification in detail. 4
(b) Obtain the minimal POS expression for the function given below using a four variable K-map $F(A, B, C, D) = \pi(2, 4, 6, 7, 10, 11, 13, 14, 15)$. 4
3. (a) State and prove De Morgan law. 4
(b) Simplify the following Boolean expression :
 $AB\bar{C}\bar{D} + ABCD + A\bar{B}\bar{C}D + A\bar{B}CD$. 4

Unit II

4. Define and design Half Subtractor and full Subtractor. 8
5. What are Encoders and Decoders ? Draw and explain an Octal to Binary encoder. 8

T-13650

2

Unit III

6. What do you mean by flip-flops ? Draw and explain the working of S-R flip-flop and D flip-flop. 8
7. Draw and explain the working of Ring and Modulo counter. 8

Unit IV

8. (a) What are the types of micro-operations ? Discuss shift micro operations in detail. 4
- (b) Write a short note on register transfer language. 4
9. What is an instruction, instruction code and instruction cycle ? Explain various phases of instruction cycle. 8