

PAPER ID—10703

B.Tech. (Civil Engg.)

EXAMINATION, 2023

(Second Semester)

BASICS OF ELECTRICAL AND  
ELECTRONICS ENGINEERING

Time : 3 Hours

Maximum Marks : 70

Before answering the question-paper candidates  
should ensure that they have been supplied to correct

- (b) What are independent and dependent sources ?
- (c) What is meant by Complex power ?
- (d) What is resonance in an electric circuit ?
- (e) Draw the V-I characteristics of a practical  $p-n$  diode.
- (f) What is meant by thermal stability ?
- (g) What is pinch off voltage ?  $2 \times 7 = 14$

2. (a) Describe the concept of electric field and electric charge. Derive expression for electric field due to a point charge.
- (b) Three resistors  $30 \Omega$ ,  $25 \Omega$ ,  $45 \Omega$  are connected in series across 200V.  
Calculate :
- (i) Total resistance
  - (ii) Current
  - (iii) Potential difference across each element.  $7 \times 2 = 14$

3. (a) State and explain Thevenin's theorem and discuss its applications and limitations.

(b) Draw the power triangle and discuss real power, reactive power, and apparent power.  $7 \times 2 = 14$

4. (a) Draw the circuit diagram and phasor diagram of a RLC series circuit and explain each component.

(b) Find the instantaneous value of alternating voltage for the given equation  $v = 10 \sin(3\pi \times 10^4 t)$  volt at :

(i) 0 s

(ii) 50  $\mu$ s

(iii) 75  $\mu$ s.  $7 \times 2 = 14$

5. (a) What is  $p$ - $n$  junction diode ? Explain its forward mode of operation.

(b) Draw and explain the circuit diagram of half wave and full wave rectifier.  $7 \times 2 = 14$

6. (a) Draw and explain CB characteristics of BJT.

(b) Explain Transconductance ( $g_m$ ) parameter of JFET.  $7 \times 2 = 14$

7. (a) What is depletion and enhancement type MOSFET ?

(b) Explain three regions of operation of a MOS transistor.  $7 \times 2 = 14$