

Code No: 153AB

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, March - 2022

ANALOG AND DIGITAL ELECTRONICS

(Common to CSE, IT, ECM, ITE, CSE(SE), CSE(CS), CSE(N))

Time: 3 Hours

Max. Marks: 75

Answer any five questions
Each Carries Equal Marks

- 1.a) Explain the operation of PN junction under forward bias condition with its characteristics.
- b) Describe the operation of Half Wave Rectifier with and without filters. [7+8]
- 2.a) Explain about RC coupled amplifier and sketch the frequency response plot of an RC coupled amplifier
- b) A transistor operating in CB configuration has $I_C = 2.98\text{mA}$, $I_E = 3.00\text{ mA}$ and $I_{CO} = 0.01\text{ mA}$. What current will flow in the collector circuit of this transistor when connected in CE configuration with a base current of $30\mu\text{A}$. [10+5]
- 3.a) What is thermal runaway? What is the condition for thermal stability in CE configuration?
- b) Derive the expression for stability factor S in self-bias circuit. [8+7]
- 4.a) Explain the operation of JFET and draw the drain and transfer characteristics.
- b) Explain about 2 input TTL NAND Gate. [10+5]
- 5.a) Convert the decimal number $(128.25)_{10}$ into binary, octal, hexadecimal number system.
- b) Build basic gates AND, NOT, OR using NAND and NOR gates. [6+9]
- 6.a) Simplify the following Boolean expression into one literal. $W'X(Z'+YZ) + X(W+Y'Z)$.
- b) What is multiplexer? Draw circuit diagram of 8:1 multiplexer. Explain its working in brief. [6+9]
- 7.a) Design a full subtractor circuit by using K-map method and draw the logic diagram.
- b) Explain 4-bit ring counter with circuit diagram and waveforms. [8+7]
- 8.a) Draw the logic diagram of clocked RS flip-flop using NAND gates and explain its working.
- b) With a neat diagram, explain 3-bit parallel in serial out shift register. [7+8]

---ooOoo---