

Code No: 153AC

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**B. Tech II Year I Semester Examinations, March - 2022****ANALOG ELECTRONICS****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

--

- 1.a) How does the reverse saturation current of a diode and voltage varies with temperature? Explain.
- b) Derive the expressions for the following parameters of the half wave rectifier circuit:
i) Average DC current ii) RMS value of current iii) Rectifier efficiency. [6+9]
- 2.a) Discuss the self bias circuit and derive the expression for S ?
- b) Explain the drain characteristics of depletion MOSFET. [7+8]
- 3.a) Explain the small signal model of CS MOSFET amplifier. Also derive the expression for amplification factor.
- b) Write short note on MOSFET as a resistor. [10+5]
- 4.a) Explain the working of common emitter direct coupled amplifier.
- b) Prove that class B push pull amplifier efficiency is 78.5%. [7+8]
- 5.a) Derive the voltage gain for unbalanced output differential amplifier.
- b) Explain the operation of direct coupled class-A power amplifier. [7+8]
- 6.a) Draw the circuit of current series feedback amplifier and derive the expressions for input and output resistances.
- b) Why are RC oscillators preferred for the generation of low frequencies? [10+5]
- 7.a) Calculate the gain, input impedance and output impedance of voltage series feedback amplifier having $A = -300$, $R_i = 50K\Omega$ and $\alpha = -1/20$.
- b) Explain non inverting op-amp circuit. [7+8]
- 8.a) Construct an op-amp integrator circuit to and explain.
- b) Explain differential amplifier using one op-amp. [8+7]

---ooOoo---