

Code No: 133AM

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, March - 2021

ELECTRICAL MACHINES – I

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

---

- 1.a) Explain the different methods of excitation of DC generators with suitable diagrams.  
b) A long shunt d.c. compound generator has an armature, series field and shunt field resistances of  $0.04\Omega$ ,  $0.03\Omega$  and  $200\Omega$  respectively. It supplies a load current of 180A at 400V. Calculate the generated emf. Assume contact drop/brush = 1.2V. [8+7]
- 2.a) Explain the following methods of improving commutation:  
i) Resistance commutation ii) E.m.f. commutation  
b) A 6 pole lap connected 230V dc shunt motor has 410 armature conductors. It takes 42 A on full load. The flux per pole is 0.05 weber. The armature and field resistances are  $0.1\Omega$  and  $230\Omega$  respectively. Contact drop per brush = 1.2V. Determine the speed of motor at full load. [8+7]
- 3.a) Derive the torque developed in a DC Motor.  
b) A 220 V DC Shunt motor draws a no – load armature current of 3 A when running at 1400 rpm. Determine its speed when taking an armature current of 65A, if armature reaction weakens the flux by 3.2%. Take armature resistance as  $0.25\Omega$ . [8+7]
- 4.a) Explain the working of a three point starter with a neat connection diagram.  
b) Derive the condition for maximum efficiency for a DC generator or DC Motor. [8+7]
- 5.a) Explain how the efficiency can be predetermined by using Swinburne's Test on a DC Shunt machine .  
b) The voltage per turn of a single phase transformer is 1.1 V. When the primary winding is connected to a 230V, 50Hz AC supply, the secondary voltage is found to be 550V. Find:  
i) the primary and secondary turns, ii) Core area if the maximum flux density is 1.2 Tesla. [8+7]
- 6.a) Distinguish between a core type and Shell type transformer.  
b) Derive the condition for maximum efficiency of a Single Phase transformer. [8+7]
7. The number of turns on the primary and secondary windings of a transformer are 1200 and 300 respectively. When the load current on the secondary is 120A at 0.85 power factor lagging, the primary current is 32 A at 0.72 power factor lagging. Determine the no-load current of the transformer and its phase with respect to the voltage. [15]
- 8.a) Explain the concept of parallel operation of a Single – phase transformers.  
b) The primary and secondary resistances of a 1100/220V transformer are  $0.32\Omega$  and  $0.0198\Omega$  respectively. If iron loss amounts to 300W, determine the secondary current at which maximum efficiency occurs and find the maximum efficiency at 0.82 power factor. [7+8]

---ooOoo---