

Code No:53012

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B.Tech II Year I Semester Examinations, March - 2022****ELECTRICAL MACHINES-I****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75****Answer any five questions****All questions carry equal marks**

---

- 1.a) Derive the expression for force in a singly excited Magnetic system.  
b) Explain the Co-Energy. For a linear magnetic circuit, derive the relation between stored magnetic energy and co-energy. [8+7]
- 2.a) Explain the constructional features of DC machine.  
b) Calculate the voltage induced in the armature winding of a 4-pole, lap wound DC machine having 728 active conductors and running at 1800 rpm. The flux per pole is 30 mwb. [8+7]
- 3.a) Develop an expression for the demagnetizing and cross magnetizing ampere turns in a DC generator.  
b) Explain the importance of compensating windings in DC machines. [8+7]
- 4.a) Describe the process of voltage build up in a DC shunt generator.  
b) Explain the classification of the DC Generators. [8+7]
- 5.a) What are the conditions for parallel operation of DC series generators? Explain.  
b) Two DC shunt generators are connected in parallel to supply a load of 5000A. Each machine has an armature resistance of  $0.03\Omega$  and field resistance of  $60\Omega$  but emf of one machine is 600V and that of the other machine is 640V. What power does each machines supply? [8+7]
- 6.a) Draw and explain the performance characteristics of DC Shunt motor.  
b) A 230 volts d.c series motor is taking 50A. Resistance of armature and series field winding is  $0.2\Omega$  and  $0.1\Omega$  respectively. Calculate i) Brush voltage, ii) Back EMF iii) Mechanical power developed. [8+7]
- 7.a) Write short notes on Ward-Leonard method of speed control in dc motors.  
b) A 250 V dc shunt motor has an armature resistance of  $0.5\Omega$  and a field resistance of  $250\Omega$ . When driving a constant torque load at 600 rpm, the motor draws of 21A. What will be the new speed of the motor if an additional  $250\Omega$  resistance is inserted in the field circuit? [8+7]
8. Explain the Swinburne's test on DC machine and give the procedure to calculate the efficiency of both generator and motor. [15]

---ooOoo---