

II B. Tech I Semester Supplementary Examinations, May/June - 2017
DIGITAL LOGIC DESIGN
 (Com. to CSE, IT)

Time: 3 hours

Max. Marks: 70

- Note: 1. Question Paper consists of two parts (**Part-A** and **Part-B**)
 2. Answer **ALL** the question in **Part-A**
 3. Answer any **THREE** Questions from **Part-B**

PART -A

1. a) Write first 20 numbers in radix-5 (3M)
- b) Convert the following to the other canonical form: $F(x, y, z) = \sum(1, 3, 5)$ (4M)
- c) Implement function $f = A\bar{B} + \bar{A}B$ using 2X1 MUX (4M)
- d) What is sequential circuit? (3M)
- e) Write the between register and counter (4M)
- f) Draw the block diagram of PLA (4M)

PART -B

2. a) Obtain the 1's and 2's complement of the following binary numbers 1010101 , (8M)
 0111000 , 0000001 , 10000 , 00000 Also obtain 9's and 10's complement of the
 following decimal numbers 09900 , 10000 , 00000
- b) What is a reflected code? Write about reflected codes by giving examples. (8M)
3. a) Show that the dual of the exclusive-OR is equal to its complement (8M)
- b) Draw a NAND logic diagram that implements the complement of the following (8M)
 function: $F(A, B, C, D) = \sum(0, 1, 2, 3, 6, 10, 11, 14)$
4. a) Implement a 5-to-32-line decoder with four 3-to-8-line decoders with enable and a (8M)
 2-to- 4-line decoder
- b) Design 4 bit Magnitude Comparator and explain in detail (8M)
5. a) What is difference between latch and flip flop? Explain about clocked RS flip flop (8M)
 using NAND gates
- b) Conversion of SR Flip Flop to JK Flip Flop (8M)
6. a) Design a shift register with parallel load operations according to the following (8M)
 function table:

shift	load	Register operation
0	0	No change
0	1	Load parallel data
1	X	Shift right

- b) Construct and explain a Johnson counter for ten timing signals (8M)
7. a) Write the difference between PROM, PLA and PAL (8M)
- b) A Combinational circuit defined by functions (8M)
 $F_1(A, B, C) = \sum(3, 5, 6, 7)$ $F_2(A, B, C) = \sum(0, 2, 4, 7)$
 Implement circuit with PLA