

Code No: 154AN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, November/December - 2020

DIGITAL ELECTRONICS

(Electrical and Electronics Engineering)

Time: 2 hours

Max. Marks: 75

Answer any five questions

All questions carry equal marks

- 1.a) Explain various number systems and codes and their conversion with examples for each.
- b) Simplify the following Boolean expressions to a minimum number of literals:
i) $ABC+A'B+ABC'$ (ii) $xy + x(wz+wz')$ [9+6]
- 2.a) Express the following numbers in decimal : $(10110.0101)_2$, $(16.5)_{16}$, $(26.24)_8$.
- b) Demonstrate by means of truth tables the Boolean Associative law and distributive law. Simplify the Boolean expression to minimum number of literals: $(A+B)'(A'+B')$. [8+7]
- 3.a) Simplify the following Boolean functions, using a four variable Karnaugh map method and implement the simplified function using NAND gates.
 $F(A,B,C,D) = \sum(0,2,4,5,6,7,8,10,13,15)$
- b) Show that the dual of the exclusive OR is also its complement. [9+6]
- 4.a) Draw the multiple level NAND circuit for the following expression:
 $(AB'+CD')E + BC(A+B)$
- b) Construct a 4-bit BCD adder-subtractor circuit using BCD adder and 9's complemented. [7+8]
- 5.a) Design 4-bit shift register using D flip-flops.
- b) Design a counter with the following repeated binary sequence: 0, 1, 2, 3, 4, 5, 6, use JK flip-flops. [6+9]
- 6.a) Draw the circuit diagram of a 4-bit binary counter with parallel load and explain its working with its function table.
- b) Design a 4 bit synchronous counter with D flip - flops and explain its working. [8+7]
- 7.a) Explain the working of R-2R ladder DAC with neat circuit diagram and mention its limitations.
- b) Draw and explain the working principle of flash type ADC. [8+7]
- 8.a) Explain the functions and applications of PLAs in memory addressing and implement the following two Boolean functions with a PLA:
 $F_1(A, B, C) = \sum(0, 1, 3, 5)$ and $F_2(A, B, C) = \sum(1, 2, 4, 7)$
- b) What are sequential programmable devices? Draw the sequential programmable logic for a basic microcell logic. [8+7]

---ooOoo---