

Code No: 154AN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year II Semester Examinations, March - 2022

DIGITAL ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 Hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- 1.a) Perform arithmetic operation using 2's complement method.
i) $-70 - 85$ ii) $130 - 65$
b) How to interface CMOS and TTL gates.
c) What are the advantages of Tri-state logic? [7+4+4]
- 2.a) Simplify the Boolean expression using K-map and draw the logic diagram.
 $F(A,B,C,D) = \sum M(0,1,5,12,13,15) + d(1,3,6)$
b) Realise a full adder using the 3×8 decoder. [8+7]
- 3.a) Develop the logic circuit diagram and table for 4-bit ring counter and explain the working.
b) What is a glitch? Design and show the timing diagram for a Mod 6 asynchronous counter showing the glitches in the diagram. [6+9]
- 4.a) With a neat block schematic, describe the working of a successive approximation ADC and illustrate it with a suitable example.
b) Explain the working of Flash type ADC. [10+5]
- 5.a) Bring out the differences between a PAL and PLA.
b) Implement $F = \sum m(2,3,4,5,7)$ using PAL.
c) Compare CPLDs and FPGAs. [5+5+5]
- 6.a) Distinguish between Sequential and combinational circuits.
b) Design a mod-11 asynchronous counter using T flip flops and discuss its disadvantages. [5+10]
- 7.a) What are fast adders? Design a 4 bit, carry look ahead adder, showing the logical diagram.
b) Design a BCD to decimal decoder. [8+7]
- 8.a) Compare the characteristics of TTL and CMOS logic families.
b) Minimize the Boolean expression $F = AB'C' + C'D + BD' + A'C$ using K-map and implement the logic circuit using NAND gates only. [6+9]

---ooOoo---