

Code No: 155CU

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, August - 2022

POWER ELECTRONICS

(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

- - -

- 1.a) Elucidate UJT as trigger source.
b) Explain protection for thyristors. [7+8]
2. Explain working of power MOSFET and power BJT with neat sketches. [15]
3. A Full converter with RLE load is connected to a 240-V, 50-Hz supply. The load current I_a is continuous and its ripple content is negligible. The turns ratio of the transformer is unity.
a) Express the input current in a Fourier series; determine the input power factor.
b) If the delay angle is $\alpha = \pi/3$, calculate V_{dc} , V_n , V_{rms} and PF. [7+8]
- 4.a) The single-phase full converter has a RLE load having $L = 6.5$ mH, $R = 0.5$ Ω , and $E = 10$ V. The input voltage is $V_s = 240$ V at (rms) 50 Hz. Determine
i) The average thyristor current I_A ,
ii) The rms thyristor current I_R .
b) Explain the working of 3-phase dual converter with a schematic diagram and relevant wave forms. [6+9]
5. Explain buck converter power circuit, analysis, waveforms at steady state conditions. [15]
6. Explain boost converter power circuit, analysis, waveforms under steady state conditions. Also obtain the relation between duty ratio and average output voltage. [15]
7. With a neat circuit diagram, explain working of three phase bridge inverter with 120 degrees mode of operation. [15]
8. Explain principle of operation of single phase A. C voltage controller with R-L load and give its applications. [15]

---ooOoo---