

Code No: 155CV

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech III Year I Semester Examinations, September - 2021


POWER SYSTEM – II
(Electrical and Electronics Engineering)

Time: 3 hours

Max. Marks: 75

Answer any five questions
All questions carry equal marks

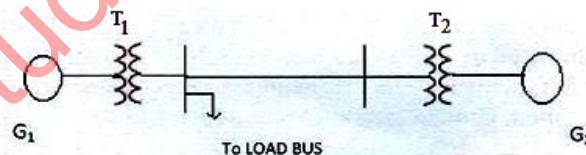- 1.a) Explain the Ferranti effect with a phasor diagram and its causes.
b) Explain the classification of lines based on their length of transmission. [8+7]
- 2.a) What are the factors which govern the performance of a transmission line?
b) What is an equivalent π circuit of long line? Derive expression for parameters of this circuit in terms of line parameters. [6+9]
- 3.a) Describe about shunt and capacitors role in voltage control.
b) Discuss about tap changing transformers used for voltage control. [8+7]
- 4.a) What is difference between compensated and uncompensated transmission line?
b) Describe about radial line with asynchronous load. [8+7]
- 5.a) What is per unit system and list its advantages?
b) Draw the impedance diagram for the electric power system shown in figure showing all impedances in per unit on a 100 MVA base. Choose 12 kV as the voltage base for generator. Three phase power and line ratings are as below:
G1:90MVA, 12kV, X=9%
T1:80MVA, 12/220kV, X=16%
T2:80MVA, 220/7.2kV, X=20%
G2:90MVA, 7.2kV, X=9%
Line:220kV, X=120 Ω
Load Bus:220kV, S=48MW+j64MVAr [6+9]



- 6.a) Determine the equations for the reflection and refraction coefficients for a short circuited line.
b) A surge of 200 KV travelling on a line of surge impedance 400 Ω reaches a junction of the line with two branch lines of surge impedance of 500 Ω and 300 Ω respectively. Find the surge voltage and current transmitted into each branch line. [8+7]
7. What is insulation coordination and describe its significance in selection of protective equipment? Explain with volt-time characteristics. [15]
- 8.a) Find symmetrical components for the given three phase voltages:
 $V_a = 300\angle -120^\circ$, $V_b = 200\angle 90^\circ$ and $V_c = 100\angle -30^\circ$
b) Develop the connection diagram of sequence network when a line to line fault occurs in a power network. [8+7]

---ooOoo---