

Code No: 156CJ**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD****B. Tech III Year II Semester Examinations, August - 2022****POWER SEMICONDUCTOR DRIVES****(Electrical and Electronics Engineering)****Time: 3 Hours****Max. Marks: 75**

Answer any five questions
All questions carry equal marks

1. Analyze the speed torque characteristics of different operating modes of a DC series motor when it is supplied by single phase fully controlled converter. [15]
2. Discuss about three phase semi-controlled converters connected to DC separately excited motor and obtain voltage current wave forms. [15]
3. With necessary diagrams explain the operation of single quadrant chopper feeding to a DC separately excited motor and draw the wave forms for continuous current operation. [15]
4. A 220 V, 30 A, 1200 rpm dc separately excited motor has an armature resistance of 6 W is controlled by a chopper. The frequency is 50 Hz and the input voltage is 240 V. Calculate the duty ratio for a motor torque of 2 times rated torque at 800 rpm. [15]
5. With necessary equations explain variable frequency control of 3-phase induction motor to get the speeds above and below base speed. [15]
6. With neat diagrams explain the operation of a Cyclo-converter fed 3-phase induction motor. [15]
7. Explain the static Kramer Drive operation for an induction motor with a circuit diagram. [15]
8. Explain about load commutated CSI fed synchronous motor with suitable diagrams.[15]

---ooOoo---