

Code No: 123BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, October - 2020

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)


Time: 2 hours

Max. Marks: 75

Answer any five questions

All questions carry equal marks

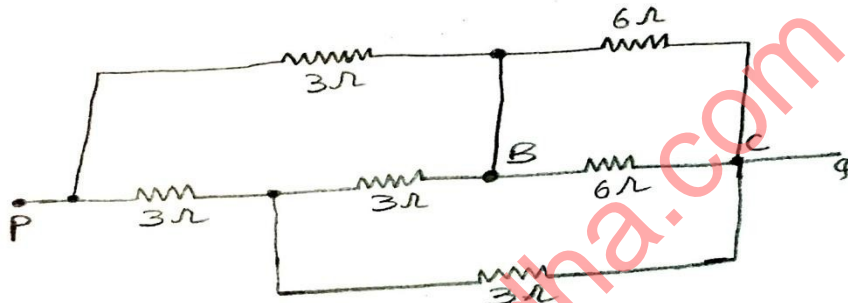- 1.a) What is maximum power transfer theorem? Prove the theorem.
 b) Three resistances of 25Ω , 50Ω and 100Ω are connected in parallel. If the total current drawn is 32 A, calculate the current drawn by each resistor. [9+6]
2. Calculate the equivalent resistance across terminals P and Q for the network shown below. [15]



3. Find the average value, RMS value and the form factor of the sinusoidal waveform. [15]
- 4.a) Prove that the average value of any symmetrical wave over a complete cycle is zero.
 b) In an R-L-C Series circuit, the voltage across R is 160 V, across L is 240 V, and total power consumed is 1000 W. when a voltage of 200 V at 50 Hz is applied across the circuit. Calculate value of the capacitor and the current flowing through the circuit. [7+8]
- 5.a) Draw and explain the equivalent circuit of a transformer under the no – load condition.
 b) Explain the necessary tests that are conducted on transformer to find the efficiency and regulation. [7+8]
- 6.a) Derive the emf equation of a Transformer.
 b) The efficiency of 400 / 200 V, 200 KVA transformer is 98.5% at full load and at 0.8 lagging power factor. At half load, 0.8 power factor lagging the efficiency is 97.5%. Calculate the values of core loss and full load copper loss. [7+8]
- 7.a) Explain the constructional details of a DC Machine with a neat sketch.
 b) A dc machine induces an emf of 240 V at 1500 rpm. Find the developed torque for an armature current of 25 A. [10+5]
8. Explain the following with respect to Instruments:
 a) Indicating b) Recording c) Integrating. [15]

---ooOoo---